

# Computer Organization and Networks

(INB.06000UF, INB.07001UF)

## Chapter 1 - Combinational Circuits

Winter 2021/2022



Stefan Mangard, [www.iaik.tugraz.at](http://www.iaik.tugraz.at)


# **Computation and Physics**

# We Need to Map our Programs to Physics

$$1 + 1 = ?$$

```
include <stdio.h>

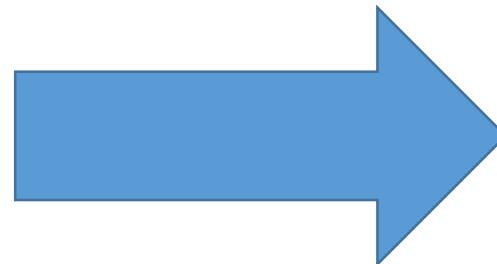int main()
{
    printf("Hello World");
    return 0;
}
```



- Mechanics
- Voltage
- Current
- Quantum Mechanics
- ...

# Examples of Computation Machines

**Enigma**


an electromechanical encryption machine



Museo della Scienza e della Tecnologia "Leonardo da Vinci" CC BY-SA

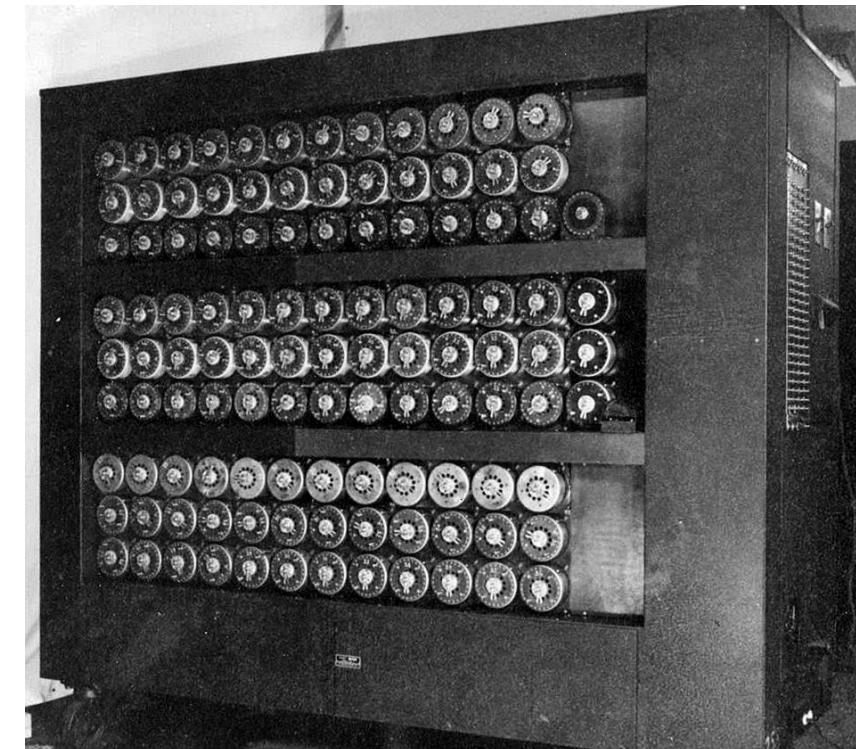
**„British Bombe“ by Alan Turing**

An electromechanical machine to break Enigma




# We Need to Map our Program

$$1 + 1 = ?$$

 

```
include <stdio.h>

 
int main()
{
    printf("Hello World");
    return 0;
}
```



IBM quantum computer  
(Lars Plougmann via flickr CC BY-SA 2.0)



 Zuse Z1 (mechanical)  
ComputerGeek via Wikipedia CC BY-SA 3.0




CMOS Processor  
(<http://asic.ethz.ch>)

# Complementary Metal-Oxide-Semiconductor (CMOS)


- Invented at Bell Labs by Mohamed Atalla and Dawon Kahng in 1959

- CMOS uses PMOS and NMOS transistors

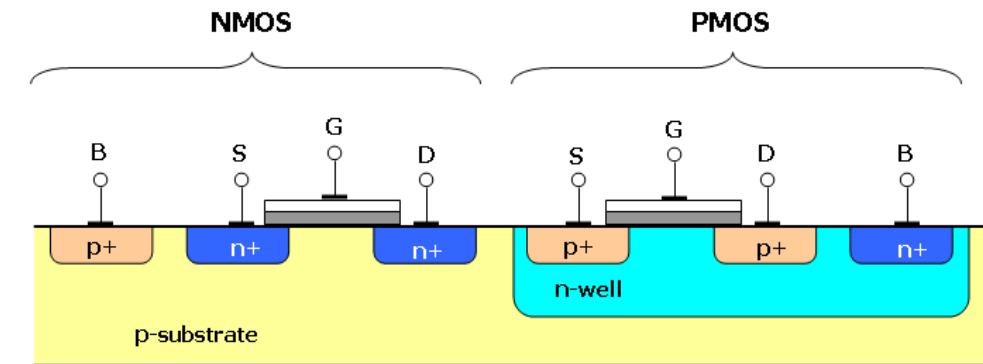


- CMOS is the technology of almost all digital circuits (from contactless RFID chips to server CPUs)

# Two Types of Transistors

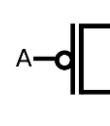

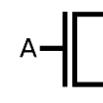PMOS transistor: is conducting, if A is connected to GND



NMOS transistor: is conducting, if A is connected to Vdd


- PMOS and NMOS transistors are essentially switches
  - PMOS:  $A=0 \rightarrow$  switch is open;  $A=1 \rightarrow$  switch is closed
  - NMOS:  $A=0 \rightarrow$  switch is closed;  $A=1 \rightarrow$  switch open
- **How do we build a computer from these two types of transistors?**

# We Need Two Things


- Computation
  - How to apply a function on input data to generate an output?
- Storage
  - How to store data and intermediate results?

# Logic Gates


# The Big Picture

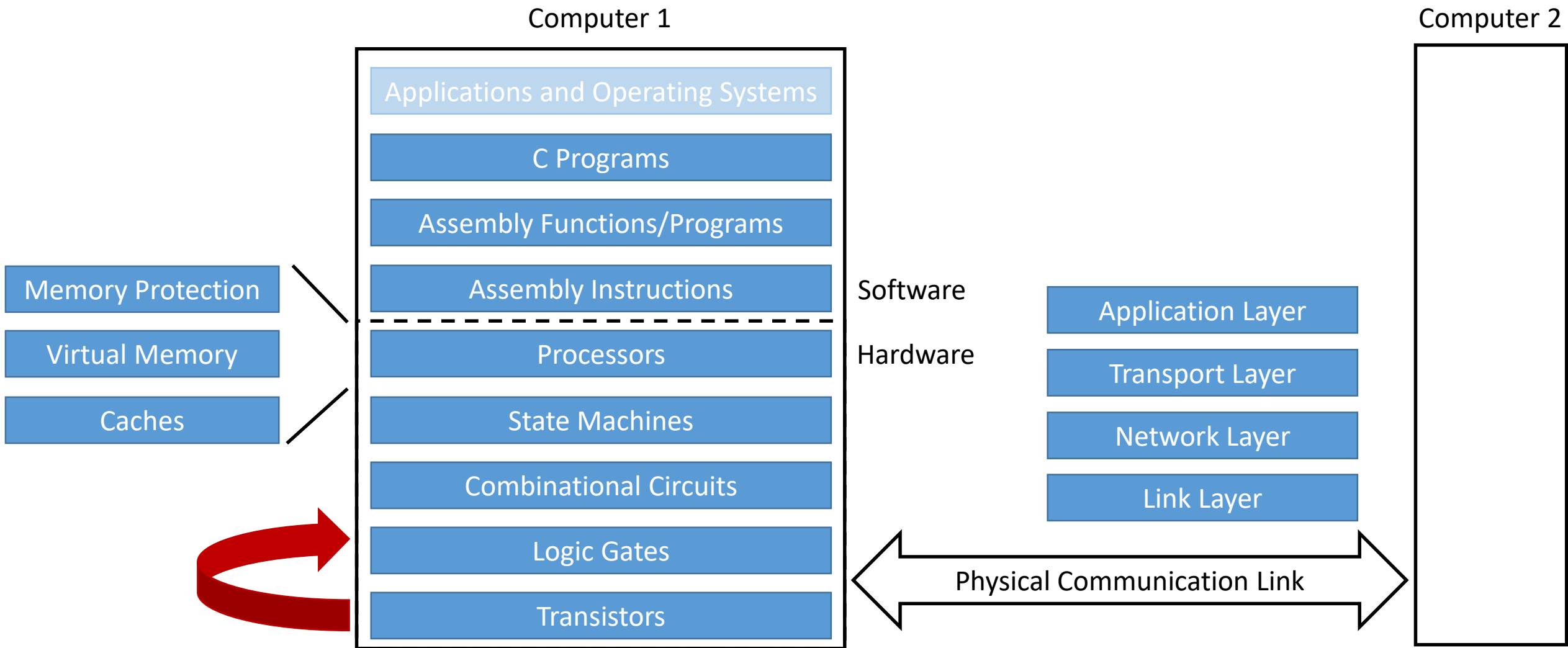

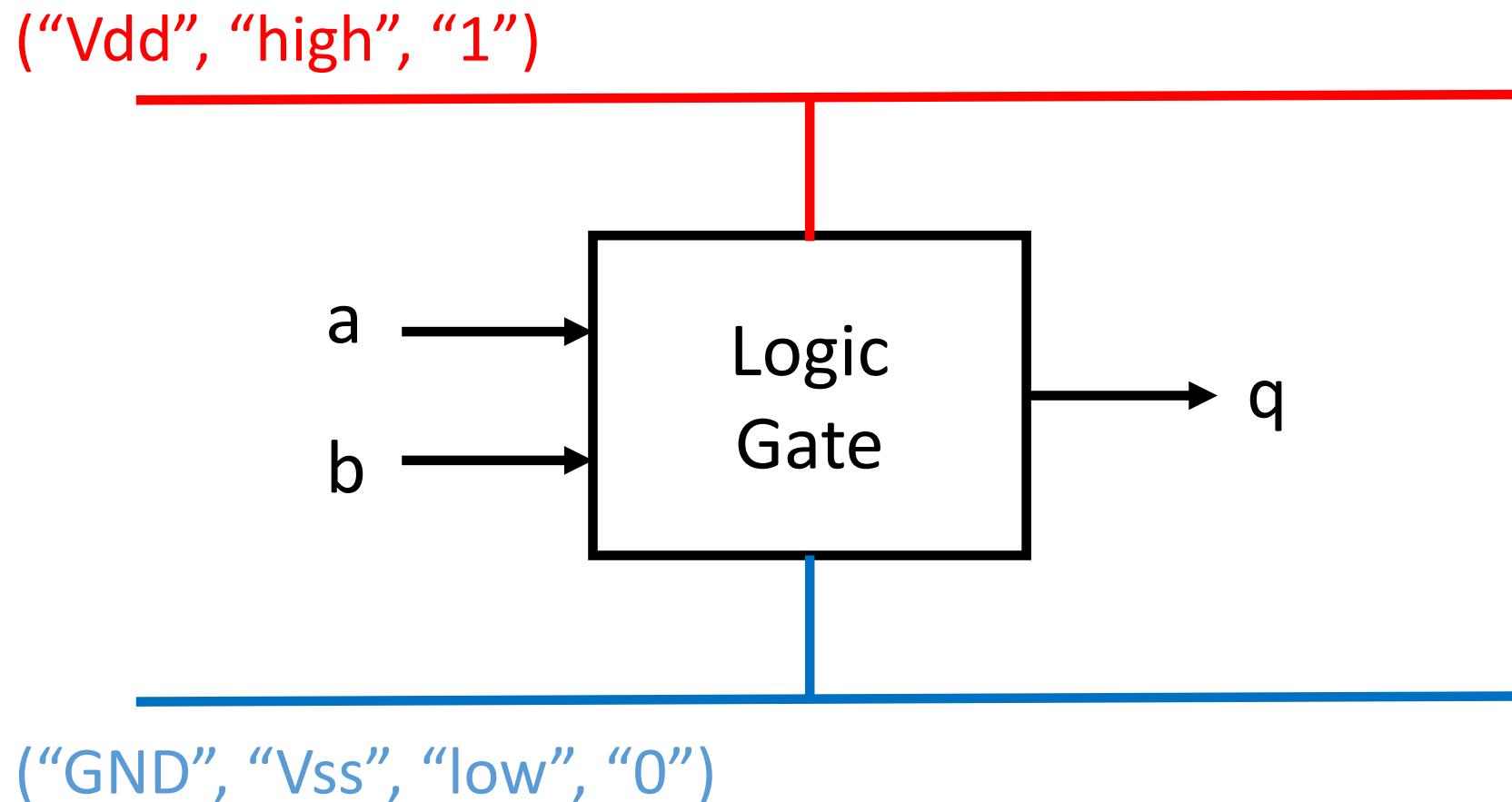
# A Logic Gate – “The Smallest Functional Unit”



# A short look inside – a CMOS Inverter

 


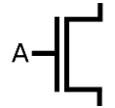PMOS transistor: is conducting, if A is connected to GND




NMOS transistor: is conducting, if A is connected to Vdd

A	Q
High (1)	Low (0)
Low (0)	High (1)

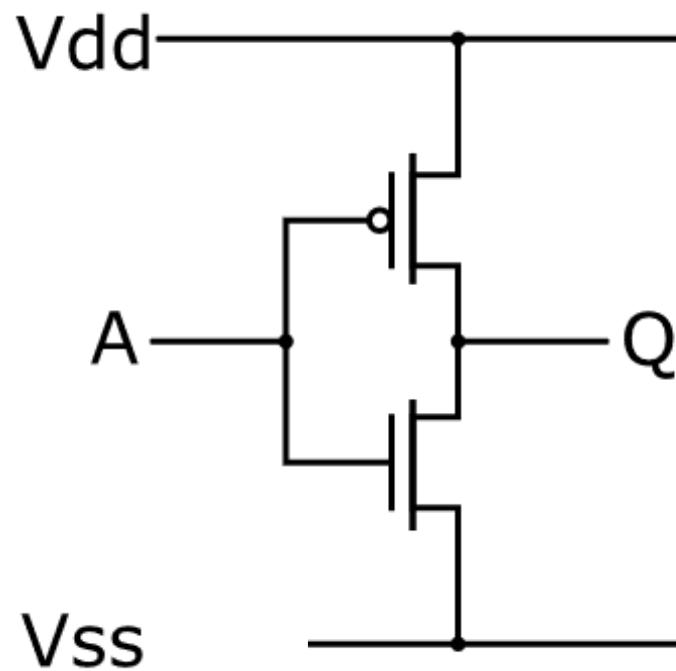


# CMOS NAND gate

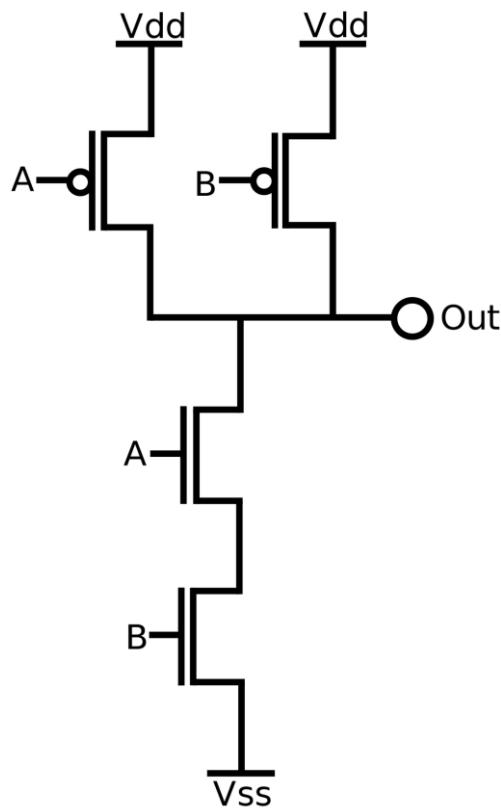

A	B	Out
Low (0)	Low (0)	High (1)
Low (0)	High (1)	High (1)
High (1)	Low (0)	High (1)
High (1)	High (1)	Low (0)

# CMOS Design Principle

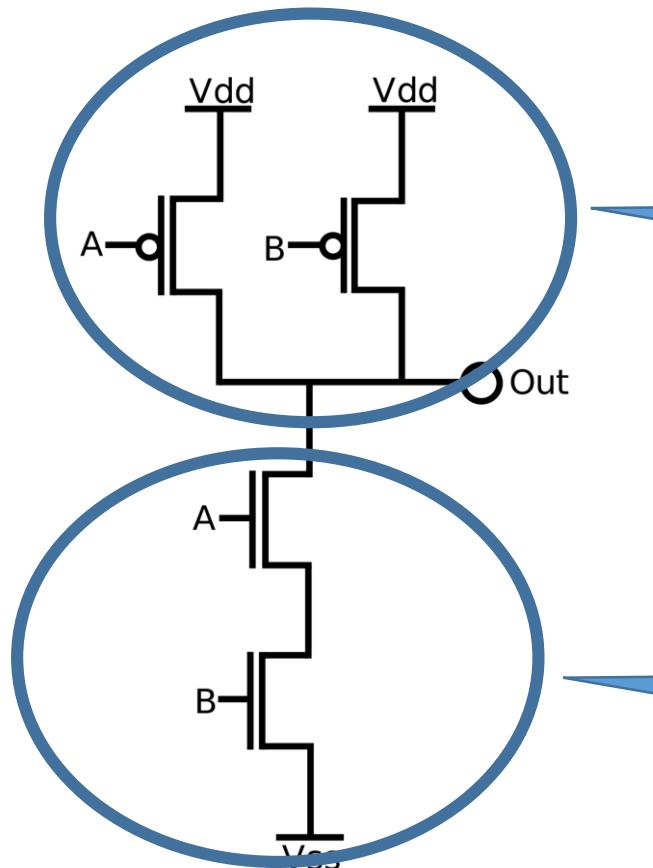

Pull-Up Network with  
PMOS transistors

Pull-Down Network with  
NMOS Transistors

Pull-Up and Pull-Down networks  
are complementary

→ given static inputs, the  
output is either pulled up or  
pulled down

Based on this principle, different  
logic gates can be built


# CMOS NOR gate

A	B	Out
Low (0)	Low (0)	High (1)
Low (0)	High (1)	Low (0)
High (1)	Low (0)	Low (0)
High (1)	High (1)	Low (0)


# Building an AND Gate

- An AND gate cannot be built using a single pull-up/pull-down network
- It is built by a NAND gate followed by an inverter


# AND Gate

 


# AND Gate

 


# AND Gate

 


# Cascading Gates

 

# Combinational Circuit

 

# The Complexity of a Microchip

 

David Carron

- Get an impression

<https://www.youtube.com/watch?v=Fxv3JoS1uY8>

[https://www.youtube.com/watch?v=2z9qme\\_ygRI](https://www.youtube.com/watch?v=2z9qme_ygRI)


- Today's chips contain billions of transistors connected by multiple layers of metal

# Moore's Law: The number of transistors on microchips doubles every two years

Our World  
in Data

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

## Transistor count

 


Data source: Wikipedia ([wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count))

OurWorldInData.org – Research and data to make progress against the world's largest problems.

Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.

# Linear Scaling

 

# The Mathematical View of a Combinational Circuit

- Combinational circuits (physical view) realize logic functions (mathematical view)
- With “function” we mean a **mapping** from a set of inputs to a set of outputs
- In mathematics, there exist many ways to express such a mapping, e.g.:  $y = f(x) = x^2$
- If you choose a value for  $x$ , you get a value for  $y$ . We call  $x$  the independent value and  $y$  the dependent value

# Logic functions (or Boolean functions)

- The “input” of a logic function is a tuple consisting of 0’s and 1’s
- The “output” of a logic function is, depending on the input values, 0 or 1
- Example:  $y = a \& b$  (“logic-AND”)

[http://en.wikipedia.org/wiki/Boolean\\_function](http://en.wikipedia.org/wiki/Boolean_function)

$\mathbf{B}^k \rightarrow \mathbf{B}$ , where  $\mathbf{B} = \{0, 1\}$  is a Boolean domain and

$k$  is a non-negative integer called the arity of the function.

In the case where  $k = 0$ , the "function" is essentially a constant element of  $\mathbf{B}$ .

# Truth Table

- A truth table **uniquely** describes a logic function.
- Example: The logic-AND function with 2 input variables  $x_1$  and  $x_0$

$x_1$	$x_0$	y
0	0	0
0	1	0
1	0	0
1	1	1

# Elements of a truth table

$$y = f(x_1, x_0)$$

Input  
variables

$x_1$	$x_0$	

# Elements of a truth table

$$y = f(x_1, x_0)$$

List all combinations  
of input variables.  
It is convenient to  
list them in sorted order.  
We usually start with  
all zeroes.

Input  
variables

$x_1$	$x_0$
0	0
0	1
1	0
1	1

# Elements of a truth table

$$y = f(x_1, x_0)$$

List all combinations of input variables.  
It is convenient to list them in sorted order.  
We usually start with all zeroes.

Input variables		Output
$x_1$	$x_0$	$y$
0	0	
0	1	
1	0	
1	1	

# Elements of a truth table

$$y = f(x_1, x_0)$$

List all combinations of input variables.  
It is convenient to list them in sorted order.  
We usually start with all zeroes.

Input variables		Output
$x_1$	$x_0$	$y$
0	0	$f(0,0)$
0	1	$f(0,1)$
1	0	$f(1,0)$
1	1	$f(1,1)$

# Size of truth tables

x	f(x)
0	$f(0)$
1	$f(1)$

1 input variable

$2^1$  possible values for x

# Size of truth tables

$n=2$

$2^n$

$x_1$	$x_0$	$f(x_1, x_0)$
0	0	$f(0,0)$
0	1	$f(0,1)$
1	0	$f(1,0)$
1	1	$f(1,1)$

$2$  input variables

$2^2$  possible combinations for  $(x_1, x_0)$

# Size of truth tables

$n=3$

$x_2$	$x_1$	$x_0$	$f(x_2, x_1, x_0)$
0	0	0	$f(0,0,0)$
0	0	1	$f(0,0,1)$
0	1	0	$f(0,1,0)$
0	1	1	$f(0,1,1)$
1	0	0	$f(1,0,0)$
1	0	1	$f(1,0,1)$
1	1	0	$f(1,1,0)$
1	1	1	$f(1,1,1)$

$2^n$

3 input variables  
 $2^3$  possible combinations for  $(x_2, x_1, x_0)$

# Size of truth tables

$n$  input variables

$2^n$  possible combinations

The size of a truth table grows exponentially with  $n$ .

Just to make sure...

 $2^n$ 

exponential

is not

 $n^2$ 

square

# Popular logic functions

- Inversion (1 input variable)

x	f(x)
0	1
1	0

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)

x	f(x)
0	1
1	0

x <sub>1</sub>	x <sub>0</sub>	y
0	0	0
0	1	0
1	0	0
1	1	1

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)

x	f(x)
0	1
1	0

x <sub>1</sub>	x <sub>0</sub>	y
0	0	0
0	1	0
1	0	0
1	1	1

x <sub>1</sub>	x <sub>0</sub>	y
0	0	0
0	1	1
1	0	1
1	1	1

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)
- XOR function (with 2 input variables)

$x_1$	$x_0$	y
0	0	0
0	1	1
1	0	1
1	1	0

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)
- XOR function (with 2 input variables)
- Buffer (double inversion)

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)
- XOR function (with 2 input variables)
- Buffer (double inversion)
- NAND function (AND followed by inversion)

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)
- XOR function (with 2 input variables)
- Buffer (double inversion)
- NAND function (AND followed by inversion)
- NOR function (OR followed by inversion)

# Popular logic functions

- Inversion (1 input variable)
- AND function (with 2 input variables)
- OR function (with 2 input variables)
- XOR function (with 2 input variables)
- Buffer (double inversion)
- NAND function (AND followed by inversion)
- NOR function (OR followed by inversion)
- NXOR function (XOR followed by inversion)

# Boolean Algebra


- Symbol for inversion: ~
- Symbol for AND: &
- Symbol for OR: |
- Example:

$$y = (\sim x_1 \& x_0) \mid (x_2 \& \sim x_0) \mid (x_2 \& x_1)$$

# Logic gates:

## Technical realizations of logic functions

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>


$$q = (\sim a \ \& \ b) \mid c$$

 

# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 


# Logic gates:

## Technical realizations of logic functions

<https://github.com/hneemann/Digital>

$$q = (\sim a \ \& \ b) \mid c$$

 

Inputs are **independent**;  
(can be chosen or  
are defined externally)

Outputs **dependent**  
on the inputs

# Implementing a logic function:

## A design flow

- Start with developing a truth table
- Example: Adding three binary variables u, v and w:  $s = u + v + w$
- With 3 variables we have  $2^3$  possible combinations for input situations.

# Implementing a logic function: A design flow

U	+	V	+	W	
0	+	0	+	0	
0	+	0	+	1	
0	+	1	+	0	
0	+	1	+	1	
1	+	0	+	0	
1	+	0	+	1	
1	+	1	+	0	
1	+	1	+	1	

8 possible combinations;  
sorted from (0, 0, 0) to (1, 1, 1)

# Implementing a logic function: A design flow

u      +      v      +      w      =      s

0	+	0	+	0	=	0
0	+	0	+	1	=	1
0	+	1	+	0	=	1
0	+	1	+	1	=	2
1	+	0	+	0	=	1
1	+	0	+	1	=	2
1	+	1	+	0	=	2
1	+	1	+	1	=	3

The result for each possible case

# Implementing a logic function: A design flow

u	+	v	+	w	=	$s_1$	$s_0$
---	---	---	---	---	---	-------	-------

0	+	0	+	0	=	0	0
0	+	0	+	1	=	0	1
0	+	1	+	0	=	0	1
0	+	1	+	1	=	1	0
1	+	0	+	0	=	0	1
1	+	0	+	1	=	1	0
1	+	1	+	0	=	1	0
1	+	1	+	1	=	1	1

Re-writing the result as a  
binary number

# Implementing a logic function: A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The truth table

# Implementing a logic function: A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The logic function for  $s_0$ :

We only look at lines  
where  $s_0$  gets “true”  
i.e. “1”.

# Implementing a logic function: A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The logic function for  $s_0$ :

$$s_0 = (\sim u \ \& \ \sim v \ \& \ w) \dots$$

# Implementing a logic function: A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The logic function for  $s_0$ :

$$s_0 = (\neg u \ \& \ \neg v \ \& \ w) \ | \\ (\neg u \ \& \ v \ \& \ \neg w) \dots$$

# Implementing a logic function:

## A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The logic function for  $s_0$ :

$$\begin{aligned}
 s_0 = & (\sim u \& \sim v \& w) \mid \\
 & (\sim u \& v \& \sim w) \mid \\
 & (u \& \sim v \& \sim w) ...
 \end{aligned}$$

# Implementing a logic function:

## A design flow

u	v	w	$s_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


The logic function for  $s_0$ :

$$\begin{aligned}
 s_0 = & (\neg u \& \neg v \& w) \mid \\
 & (\neg u \& v \& \neg w) \mid \\
 & (u \& \neg v \& \neg w) \mid \\
 & (u \& v \& w)
 \end{aligned}$$

# Implementing a logic function: With a little help from Digital

<https://github.com/hneemann/Digital>
 
# Implementing a logic function: With a little help from Digital



Start Digital


A screenshot of the 'Table' window. The window title is 'Table'. The menu bar includes 'File', 'New', 'Edit', 'Create', and 'K-Map'. The table has columns labeled A, B, C and a row labeled Y. The data rows are:

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

At the bottom of the window, it says 'Y = 0'.

Goto Analysis → Synthesis
 
# Implementing a logic function: With a little help from Digital



Start Digital

Goto Analysis → Synthesis

Adjust inputs and outputs

# Implementing a logic function: With a little help from Digital

*Table				
A	B	C	Y	X
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

Start Digital

Goto Analysis → Synthesis

Adjust inputs and outputs

Specify the output section of  
the truth table

# Implementing a logic function: With a little help from Digital

*Table				
File	New	Edit	Create	K-Map
A	B	C	Y	X
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Start Digital

Goto Analysis → Synthesis

Adjust inputs and outputs

Specify the output section of  
the truth table

# Implementing a logic function: With a little help from Digital

The screenshot shows the Digital software interface. The main window is titled '\*Table' and contains a truth table with columns A, B, C, Y, and X. The table rows represent the minterms of a logic function. The bottom right cell of the table is highlighted in yellow. The menu bar includes File, New, Edit, Create, and K-Map. The 'Create' menu is open, showing options like 'Open', 'Save', 'Export Plain Text' (which is selected), 'Export LaTeX', 'Export Test Case', 'Export J/K Expressions' (unchecked), and 'Show results dialog'. The export dialog window is titled 'Export' and displays the logic expressions for Y and X. The expression for Y is  $Y = (A \wedge C) \vee (A \wedge B) \vee (B \wedge C)$ . The expression for X is  $X = (\neg A \wedge \neg B \wedge C) \vee (\neg A \wedge B \wedge \neg C) \vee (A \wedge \neg B \wedge \neg C) \vee (A \wedge B \wedge C)$ . There are 'Clipboard' and 'OK' buttons at the bottom of the export dialog.

A	B	C	Y	X
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Start Digital


Goto Analysis → Synthesis

Adjust inputs and outputs

Specify the output section of  
the truth table

Optionally: Check plain text export
 
# Implementing a logic function: With a little help from Digital



# Start Digital

## Goto Analysis → Synthesis


## Adjust inputs and outputs

Specify the output section of  
the truth table

Optionally: Check plain text export

Click “Create” and “Circuit”.
 
# Implementing a logic function: With a little help from Digital






Switch to Simulation Mode:



Simulate circuit with  
all possible input combinations.
   
# Implementing a logic function: With a little help from Digital



Alternative: specify the **expression**

Use “let” to specify outputs.  
Separate formulas by comma.



# Boolean Algebra

- Values of variables are only 0 or 1.
- 3 main operations:
  - Negation, also known as “inversion” ~
  - Conjunctions, also known as “ANDing” &
  - Disjunction, also known as “ORing” |
- 1 other popular operation: “exclusive OR” ^

# Boolean Algebra

$$a \mid 0 = a$$

$$a \mid 1 = 1$$

$$a \& 0 = 0$$

$$a \& 1 = a$$

$$a \wedge 0 = a$$

$$a \wedge 1 = \sim a$$

$$a \mid a = a$$

$$a \mid \sim a = 1$$

$$a \& a = a$$

$$a \& \sim a = 0$$

$$a \wedge a = 0$$

$$a \wedge \sim a = 1$$

$$a \mid (a \& b) = a$$

$$a \& (a \mid b) = a$$

The proof of all these facts is rather easy: Take a truth table and check all possibilities.

# Boolean Algebra

Associative Law:

$$(a \mid b) \mid c = a \mid (b \mid c)$$

$$(a \& b) \& c = a \& (b \& c)$$

$$(a \wedge b) \wedge c = a \wedge (b \wedge c)$$

Commutative Law:

$$a \mid b = b \mid a$$

$$a \& b = b \& a$$

$$a \wedge b = b \wedge a$$

The proof of all these facts is rather easy: Take a truth table and check all possibilities.

# Boolean Algebra

Distributive Law:

$$a \mid (b \& c) = (a \mid b) \& (a \mid c)$$

$$a \& (b \mid c) = (a \& b) \mid (a \& c)$$

$$a \& (b \wedge c) = (a \& b) \wedge (a \& c)$$

The proof of all these facts is rather easy: Take a truth table and check all possibilities.

# Boolean Algebra

De Morgan's Law:

$$\sim(a \ \& \ b) = \sim a \mid \sim b$$

$$\sim(a \mid b) = \sim a \ \& \ \sim b$$


The proof of all these facts is rather easy: Take a truth table and check all possibilities.

# Boolean Algebra

De Morgan's Law:

$$\sim(a \ \& \ b) = \sim a \mid \sim b$$
 
$$\sim(a \mid b) = \sim a \ \& \ \sim b$$





The proof of all these facts is rather easy: Take a truth table and check all possibilities.

# Boolean Algebra

De Morgan's Law:

$$\sim(a \& b) = \sim a \mid \sim b$$

$$\sim(a \mid b) = \sim a \& \sim b$$

  

The proof of all these facts is rather easy: Take a truth table and check all possibilities.

## Incomplete specification: “Don’t Cares”

- Sometimes we are not interested in some input combinations; we “**don’t care**” about the output of the logic function in this case.
- This is the case, when not all input combinations occur in some context.

# Incomplete specification: “Don’t Cares”


- Example: 3 inputs, 2 “don’t cares”.

\*Table

File New Edit Create K-Map

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	x ←
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x ←
1	1	1	0

$Y = A \wedge \bar{B}$

 


# Result after “synthesizing” with Digital

\*Table

File New Edit Create K-Map

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	x ←
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x ←
1	1	1	0

$Y = A \wedge \bar{B}$

 

# How many logic functions are possible?

- Let's start with logic functions with 1 input variable

# How many logic functions are possible?

- Let's start with logic functions with 1 input variable
- There exist 4 possible different truth tables:

x	y
0	0
1	0

x	y
0	1
1	0

x	y
0	0
1	1

x	y
0	1
1	1

# How many logic functions are possible?

- Let's start with logic functions with 1 input variable
- There exist 4 possible different truth tables
- In the y-column we see **all possible combinations**

x	y
0	0
1	0

x	y
0	1
1	0

x	y
0	0
1	1

x	y
0	1
1	1

# How many logic functions are possible?

- Let's start with logic functions with 1 input variable
- There exist 4 possible different truth tables
- In the y-column we see **all possible combinations**

x	y <sub>0</sub>	y <sub>1</sub>	y <sub>2</sub>	y <sub>3</sub>
0	0	1	0	1
1	0	0	1	1

# How many logic functions are possible?

- Two input variables  $x_1$  and  $x_0$

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

# How many logic functions are possible?

- Two input variables  $x_1$  and  $x_0$

$n=2$

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

# How many logic functions are possible?

- Two input variables  $x_1$  and  $x_0$

$n=2$

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$2^n$

# How many logic functions are possible?

- Two input variables  $x_1$  and  $x_0$

$n=2$

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$$2^{2^n} = 2^{2^2} = 16$$

With  $n = 3, 4, \dots$

- $n = 3, 2^3 = 8$  lines,  $2^8 = 256$  functions
- $n = 4, 2^4 = 16$  lines,  $2^{16} = 65536$  functions
- $n = 5, 2^5 = 32$  lines,  $2^{32} = 4294967296$  functions
- $n = 6, 2^6 = 64$  lines,  $2^{64} = 18446744073709551616$  functions

# Back to $n = 2$

- Some functions are “**popular**” and have names:

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

AND



# Popular 2-input functions



# Popular 2-input functions

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$\text{XOR}$        $\text{AND}$        $\text{OR}$



# Popular 2-input functions



NAND

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

XOR      AND      OR


# Popular 2-input functions



		NOR		NAND													
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

XOR      AND      OR

# Popular 2-input functions

 

		NOR		NAND		XNOR											
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

XOR      AND      OR

# Some functions are trivial

		NOR		NAND		XNOR											
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

XOR      AND       $x_1$       OR

# Some functions are trivial

		NOR		NAND				XNOR									
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

XOR      AND       $x_0$        $x_1$       OR

# Some functions are trivial

		NOR		NAND				XNOR									
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0                    XOR                    AND                     $x_0$                      $x_1$                     OR

# Some functions are trivial

		NOR		NAND				XNOR									
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0                    XOR                    AND                     $x_0$                      $x_1$                     OR                    1

# Some functions are “almost trivial”

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	

NOR                    NAND                    XNOR

$0$                      $\sim x_1$                      $XOR$                      $AND$                      $x_0$                      $x_1$                      $OR$                      $1$

# Some functions are “almost trivial”

		NOR		NAND		XNOR											
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	0	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$0$        $\sim x_1$        $\sim x_0$        $XOR$        $AND$        $x_0$        $x_1$        $OR$        $1$

# Some functions are “implications”

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	0	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

NOR                    NAND                    XNOR

$x_1$  implies  $x_0$

↓

$0 \quad \sim x_1 \quad \sim x_0 \quad XOR \quad AND \quad x_0 \quad x_1 \quad OR \quad 1$

# Some functions are “implications”

		NOR				NAND		XNOR									
$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	0	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$0$        $\sim x_1$        $\sim x_0$        $XOR$        $AND$        $x_0$        $x_1$        $OR$        $1$

$x_1$  implies  $x_0$

$x_1$  is implied by  $x_0$

And some functions are “inverse implications”

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	0	0	0	0	0	1	1	1	0	0	0	0	0	1	1	1	
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	

$x_1$  does not imply  $x_0$

NOR

$\sim x_1$

$\sim x_0$

XOR

AND

$x_0$

$x_1$

OR

1

$x_1$  implies  $x_0$

$x_1$  is implied by  $x_0$

And some functions are “inverse implications”

$x_1$	$x_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$y_8$	$y_9$	$y_{10}$	$y_{11}$	$y_{12}$	$y_{13}$	$y_{14}$	$y_{15}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	

$x_1$  does not imply  $x_0$

$x_1$  implies  $x_0$

$x_1$  is not implied by  $x_0$


$x_1$  is implied by  $x_0$

NOR                    NAND                    XNOR

$\sim x_1$        $\sim x_0$       XOR      AND       $x_0$        $x_1$       OR      1

The popular functions can also have more than 2 inputs


- Example: 5-input AND

 

- Only if **all** input values are 1, the output is 1

The popular functions can also have more than 2 inputs

- Example: 3-input OR

 


- If at least **one** input values is 1, the output is 1

# Be careful with XOR function with more than 2 inputs

- Interpretation #1: Output is 1, if an **odd** number of input values is 1
- Interpretation #2: Output is 1, if **exactly 1** input value is 1
- Interpretation #1 is the “common” interpretation! → This is what we use in the lecture

 
# Other Important Gates – Multiplexer (MUX)



- The select signal ( $sel$ ) determines whether  $out$  is equal to  $I_0$  or  $I_1$ :
  - $sel = 0$  means  $out = I_0$
  - $sel = 1$  means  $out = I_1$
 
# Scaling to more inputs

- With each additional select signal, the number of selectable inputs doubles
- 2to1MUX: 1 select signal
- 4to1MUX: 2 select signals
- 8to1MUX: 3 select signals
- ...




4to1MUX
 
# Other Important Gates – Demultiplexer/Decoder

- The select signals (sel) of a demultiplexer determine whether to which output the input is mapped:


- Sel = 0 means  $\text{out}_0 = \text{in}$
- Sel = 1 means  $\text{out}_1 = \text{in}$




1to2 DEMUX

- The select signals (sel) of a decoder determines which output is high

 - Sel = 0 means  $\text{out} = 1$
- Sel = 1 means  $\text{out} = 1$



1to2 Decoder

 

1to4 Decoder


**How many different types of gates are needed to be able to implement any logic function?**

# Functional Completeness


- A functionally complete set of logic gates is a set that allows to build all possible truth tables by combining gates of this set.
- Important sets are:
  - **{NAND}**: Any circuit can be built just by using NAND gates (try it out in Digital!)
  - **{NOR}**: Any circuit can be built just by using NOR gates
  - **{AND, NOT}**: Any circuit can be built just by using AND and NOT gates
  - **{AND, OR, NOT}**: The set we use to map truth tables to equations

# Describing Combinational Circuits


# Describing Combinational Circuits

 


# Describing Combinational Circuits

 


# Describing Combinational Circuits

 


# Describing Combinational Circuits

 

# Describing Combinational Circuits

 

# Describing Combinational Circuits

 


# Example 1

in_a	in_b	in_c	out_q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\text{out}_q = (\sim \text{in}_a \& \text{in}_b) \mid \text{in}_c$$

```
module simple_circuit (
    input in_a,
    input in_b,
    input in_c,
    output out_q
);
    assign out_q = ((~ in_a & in_b) | in_c);
endmodule
```

 

## Truth Table

e 1

in_a	in_b	in_c	out_q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logic equation

$$\text{out}_q = (\neg \text{in}_a \ \& \ \text{in}_b) \mid \text{in}_c$$

module simple\_circuit (

input in\_a,

input in\_b,


input in\_c,

output out\_q

);

assign out\_q = ((~ in\_a &amp; in\_b) | in\_c);

endmodule

 Hardware  
Description  
Language

Circuit Netlist

("connected  
logic gates")


# SystemVerilog – A Hardware Description Language

```
module simple_circuit (
    input in_a,
    input in_b,
    input in_c,
    output out_q
);
    assign out_q = ((~ in_a & in_b) | in_c);
endmodule
```

# Example 2


```
module simple_circuit_with_mux (
    input logic in_a,
    input logic in_b,
    input logic in_c,
    input logic in_x,
    input logic in_y,
    input logic in_z,
    input logic mux_sel,
    output logic out_q
);
```

```
always_comb begin
    if (mux_sel == 0)
        out_q = (~in_a & in_b) | in_c;
    else
        out_q = (in_x ^ in_y) | ~in_z;
end
endmodule
```

 

**I have designed a circuit - how do I  
built a physical device that  
implements this circuit?**

# My Circuit Description

 

**Field Programmable Gate Array  
(FPGA)**

**Application-Specific Integrated Circuit  
(ASIC)**

# ASIC – Application-Specific Integrated Circuit

A chip that physically realizes your circuit

- Basic steps to building your ASIC (very high level view):
  - Select your favorite semiconductor manufacturing plant (see [https://en.wikipedia.org/wiki/List\\_of\\_semiconductor\\_fabrication\\_plants](https://en.wikipedia.org/wiki/List_of_semiconductor_fabrication_plants))
  - Receive the standard cell library from the plant (“the list of logic gates that the plant can build”)
  - Map our circuit to the available cells
  - Place and route the cells
  - Let the plant physically build your circuit



# FPGAs – Field Programmable Gate Arrays

Existing hardware that can be configured to correspond to your circuit (“programmable hardware”)

- Basic concept (very high level view):
  - FPGA vendors build huge arrays of LUTs (Look-Up-Tables) and switches (highly regular repeated physical structure)
  - You can map your design to this hardware (the gates are mapped to LUTs and the wiring is mapped to the switches connecting the LUTs)
  - An FPGA bitfile stores how a given FPGA needs to be configured to realize your circuit (format is vendor-specific)
  - Load the bitfile into the FPGA and the FPGA realizes your circuit


# FPGA boards

- FPGAs are trade-off between hardware and software
  - Less efficient than hardware, but more efficient than software
  - Less expensive than hardware, but more expensive than software
- You can get small FPGA boards already for less than EUR 50.
  - Interested in putting your practical of this semester on physical hardware?
  - Basically any FPGA works for this purpose; ICE40 FGPAs offer an open source toolflow based on the tools we also use in this class (e.g. <https://www.mouser.at/ProductDetail/Lattice/ICE40HX1K-STICK-EVN?qs=hJ2CX3hEdVEyBLaHAEExelA%3D%3D>)

# Mapping a Circuit to the Cells of an FPGA or ASIC

- Logic Synthesis is the process of mapping an abstract description (typically done in a hardware description language) of a circuit to a list of available logic gates
- Synthesis can be parametrized to optimize different properties, like speed or area

# Logic Synthesis

 

# The Toolchain

- iVerilog:
  - Simulator for Verilog code
- SV2V
  - Converts SystemVerilog to Verilog
- Yosys:
  - Synthesis Tool

# The Commands for Our Examples

- Make
  - **build:** Compile code
  - **run:** Run simulation
  - **view:** View simulation result in wave viewer (not relevant yet)
- **syn:** Synthesize code
- **build-syn:** compile synthesized code
- **run-syn:** Run Simulation based on netlist (synthesis result)
- **show:** Show netlist after synthesis

# Let's Try This Out

- See examples con01 available at

<https://extgit.iaik.tugraz.at/con/examples-2021>

# Final remarks

- Every logic function can be **uniquely** specified by its truth table.
- Every truth table can be implemented by an **unlimited** number of logic circuits.
- **Never** talk about optimization without specifying what aspect should be optimized: area, speed, energy consumption, number of gates, security,...?