

Computer Organization and Networks

(INB.06000UF, INB.07001UF)

Chapter 3 – State Machines

Winter 2021/2022




Stefan Mangard, www.iaik.tugraz.at

What About Storage?

- We have so far only considered functions
- We also want to store data and define sequences of computation
- So far, we have not talked about storage or about time


Storage

Storage

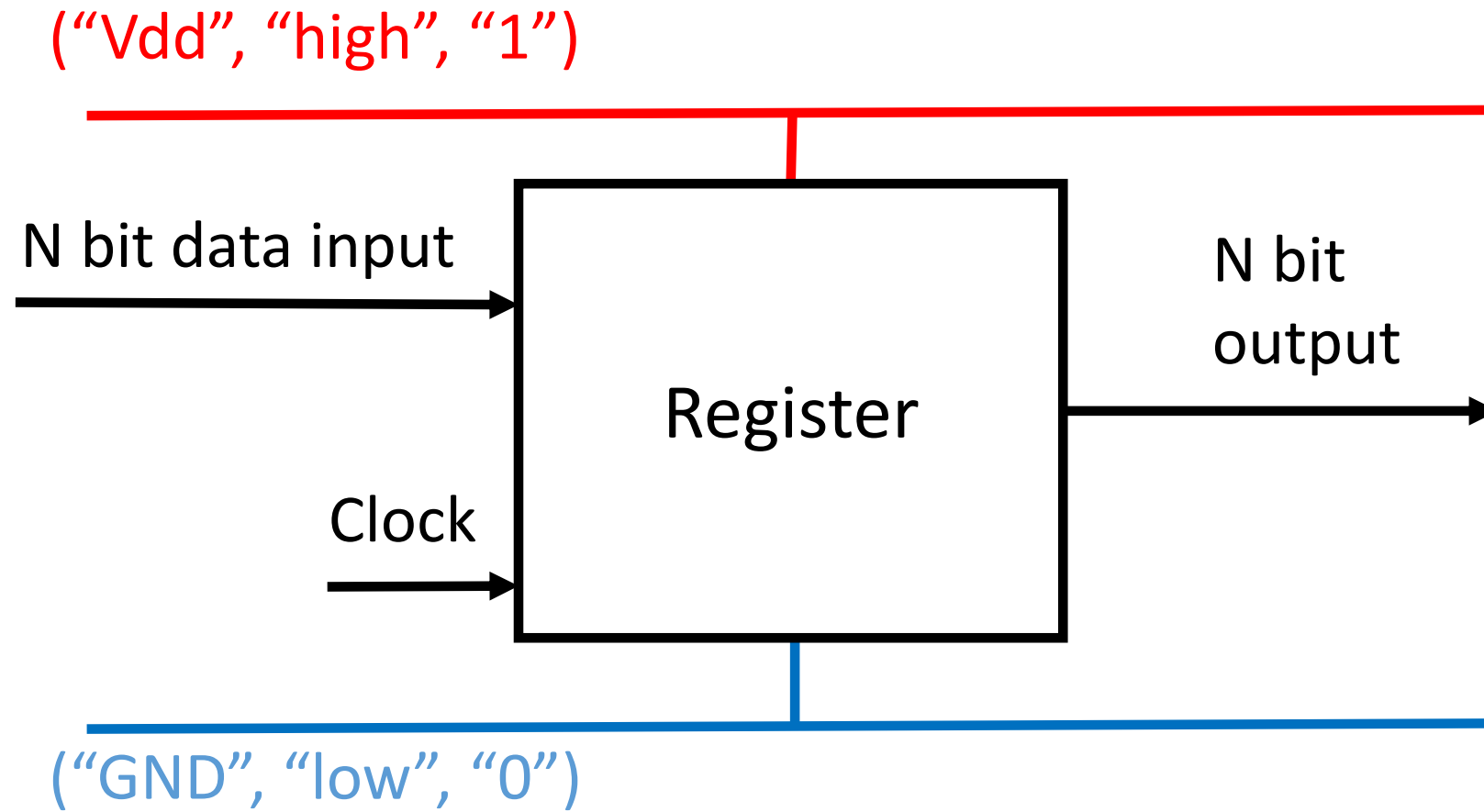

Storage

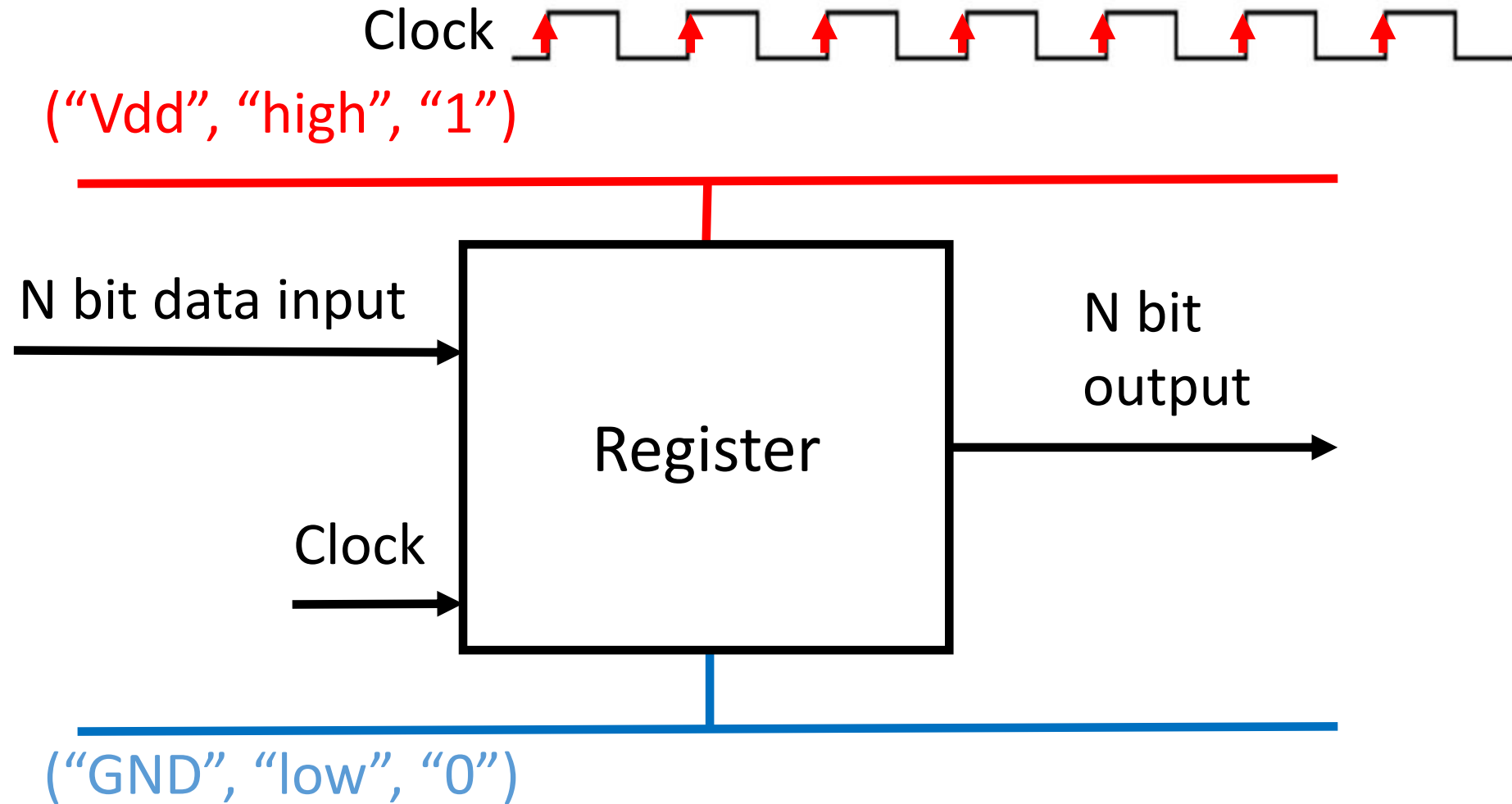
- The registers sets output = input when the clock switches from low to high;
- In all other cases, the input is ignored; the last “sampled” value is kept at the output




Naming Conventions

- Register: An n-bit storage sampling data on the rising clock edge
- Flip Flop: A 1-bit storage sampling data on the rising clock edge


Combining

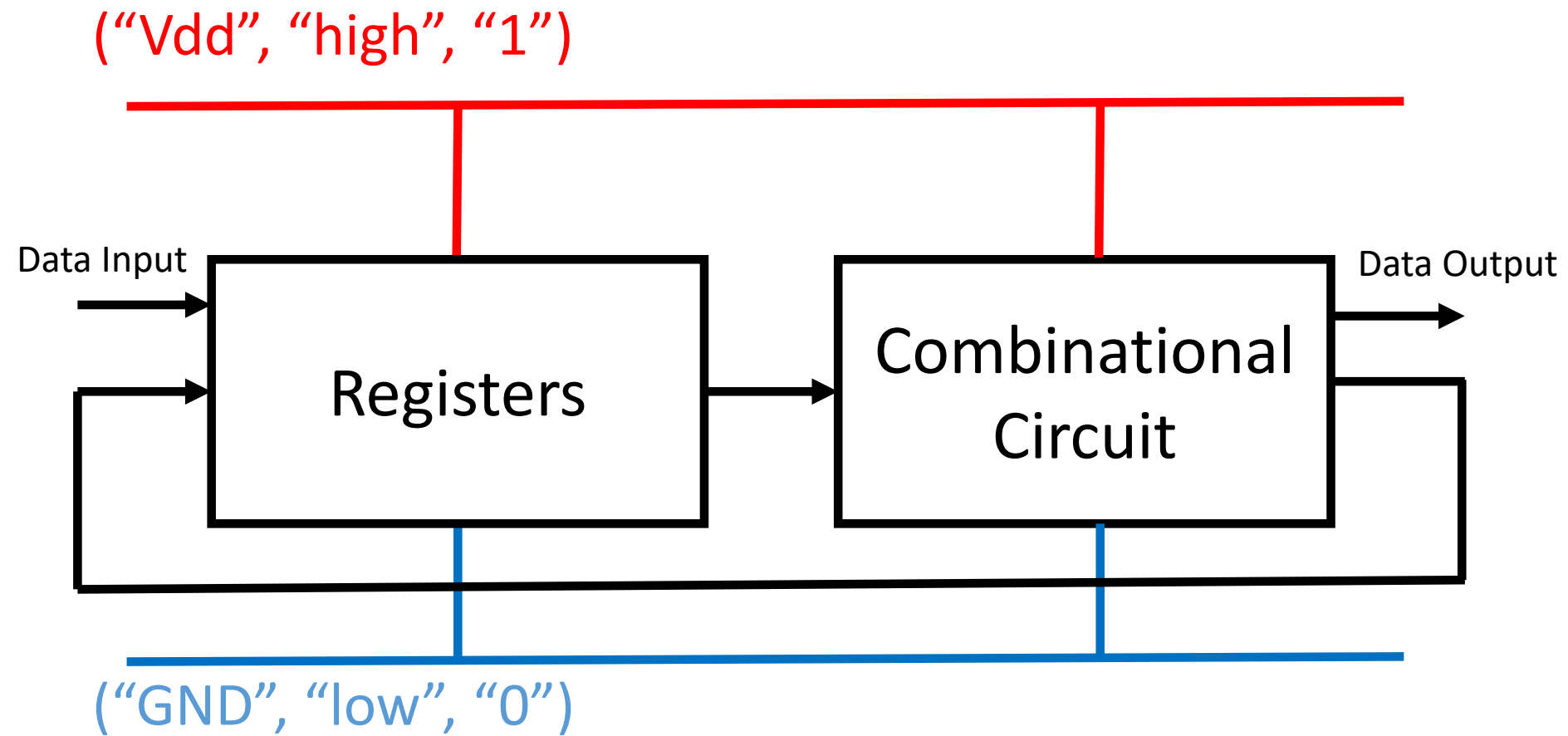

Example Counter

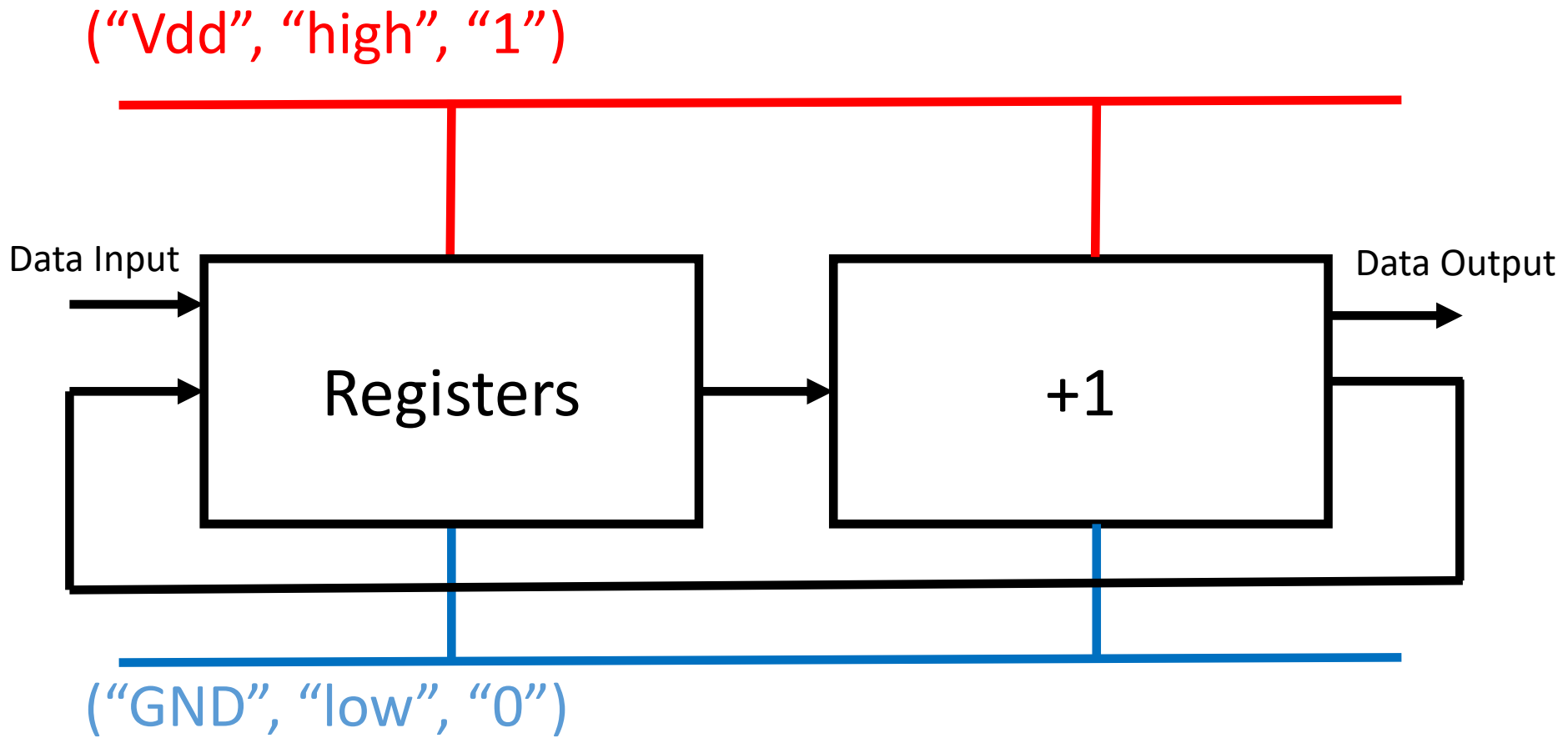

Example Counter

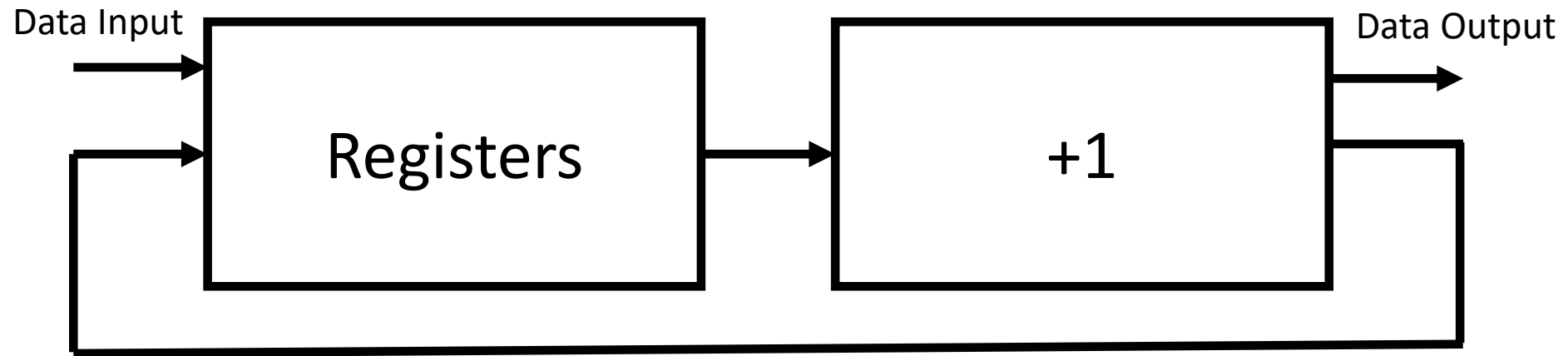

Clock



Register

0 1 2 3 4 5 6 7


Let's Build This in Digital

- See examples con03 available at

<https://extgit.iaik.tugraz.at/con/examples-2021.git>


The Clock Frequency

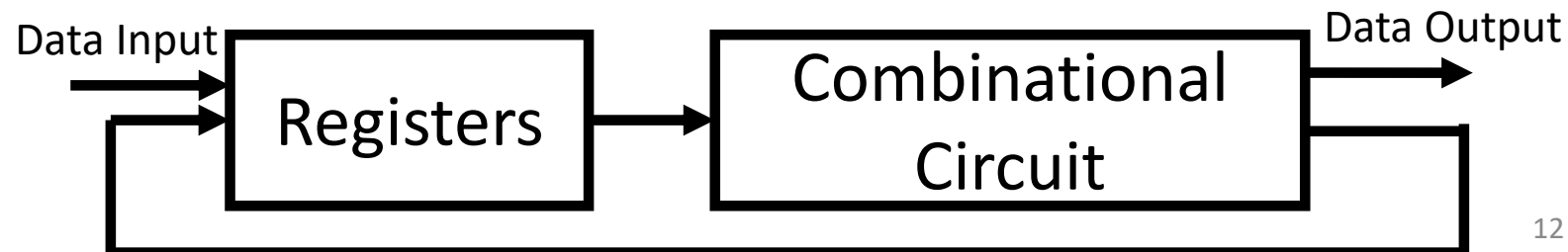- Can we increase the clock frequency arbitrarily?
- The clock frequency is limited by the time the combinational circuit needs to compute its outputs.
- The critical path is the path with the longest propagation delay in the combinational circuit. It defines the maximum clock rate



Temperature, Power Consumption

- The higher the temperature, the slower the transistors become and the lower becomes the maximum clock rate
 - The lower the temperature, the higher clock rates are possible
- Why does a CPU produce heat?
 - Every time a logic gate switches, NMOS and PMOS transistors are open at the same time → there is a short current.
 - Upon a switch, there is also current flowing to charge and discharge parasitics
 - The more transistors are switching, the more heat is produced

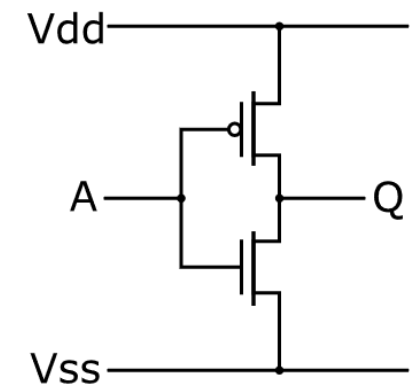

Clock Frequency Too High

What happens, if the clock frequency is too high?

- The circuit stores an intermediate state of the combinational circuit in the registers.
- The intermediate state depends on the physical layout, the temperature, fabrication details, ... → hard to predict; overclocking a processor too much typically leads to a crash

State Machines


Finite State Machines (FSMs)

- FSMs are the “work horse” in **digital systems**.
- FSMs can be implemented with **hardware**.
- We look at “**synchronous**” FSMs only:
 - The “clock signal” controls the action over time
- FSMs can be described with three main “views”:
 - The **functional** view with the “state diagram”
 - The **timing** view with the “timing diagram”
 - The **structural** view with the “logic circuit diagram”


Time flows continuously




We cut time into slices

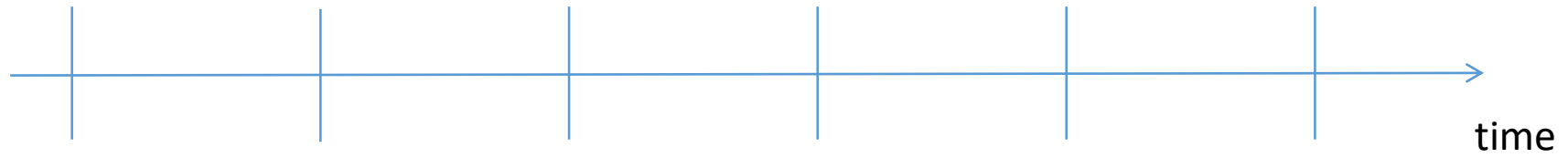

Time slices are strictly ordered

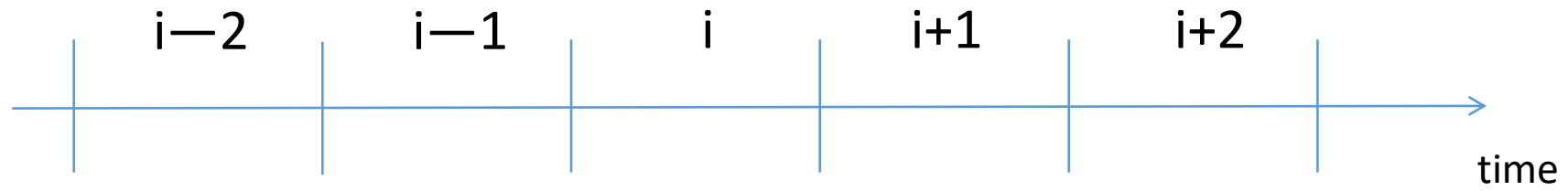


Clock signal

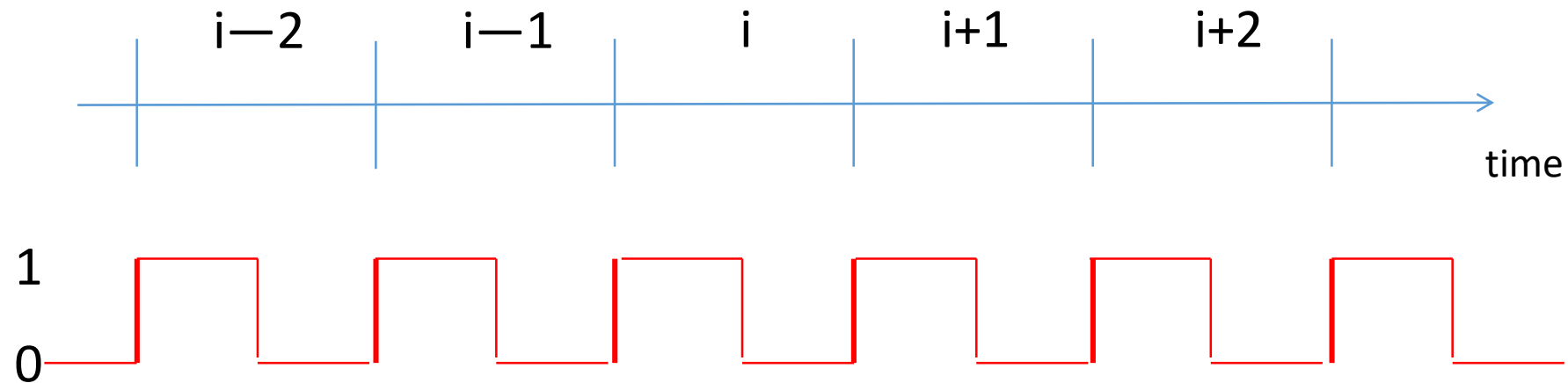

We use the **clock signal ("clk")** in order to advance time from slice to slice.


Rising clock edge

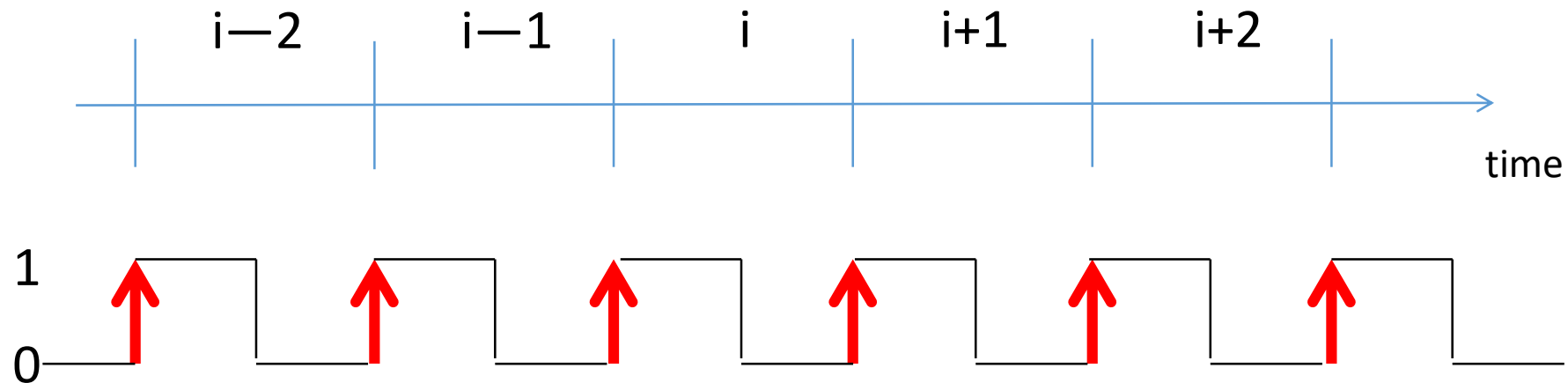

With **rising clock edges** we define the transition between neighboring time slices.

The negative clock edges have no importance.


Clock period

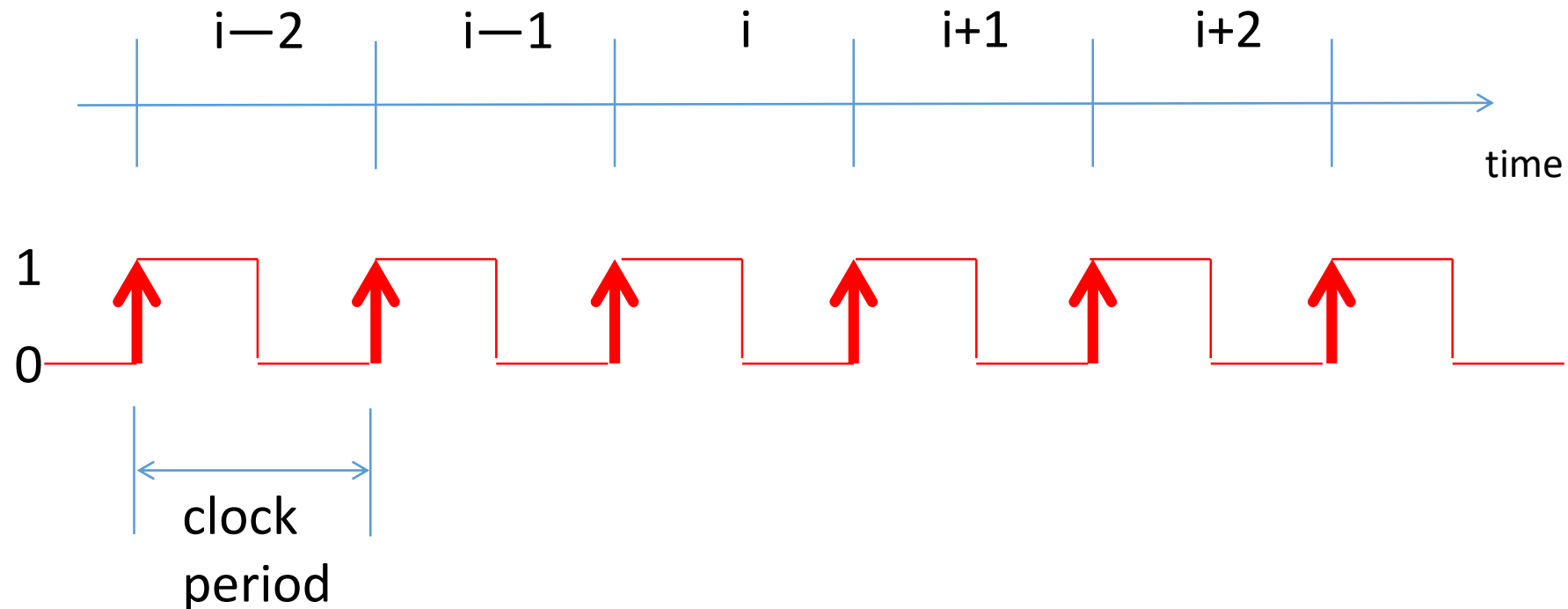

We call the time between two rising clock edges also “clock period”.

Most often, clock periods have the same length. But this is not necessarily the case.

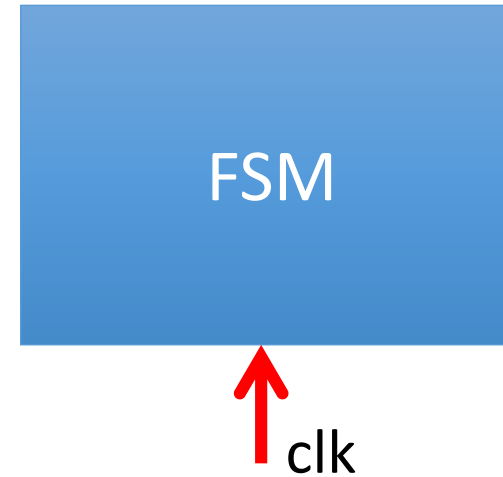
Synchronous finite state machine (= automaton)



A **synchronous FSM** is clocked by a clock signal (“clk”).
In each clock period, the machine is in a defined (current) **state**.
With each rising edge of the clock signal, the machine advances
to a defined next state.


We are interested in “**finite state machines**” (FSMs).
FSMs have only a finite number of states.

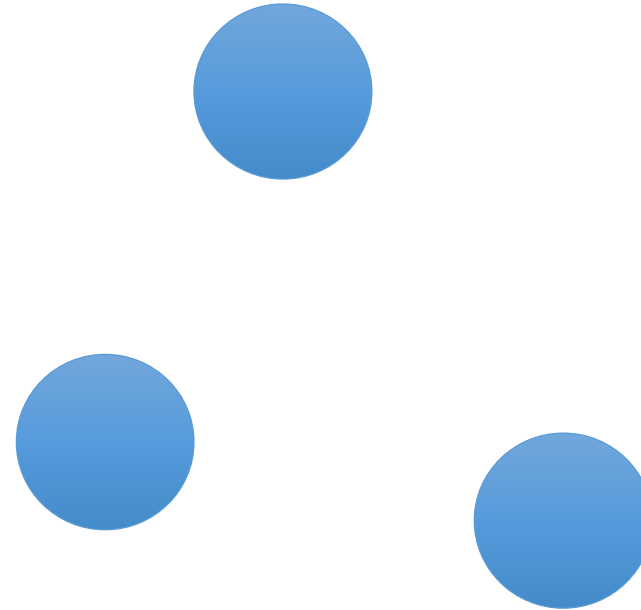The sequence of states can be defined in a **state diagram**.




State diagram:

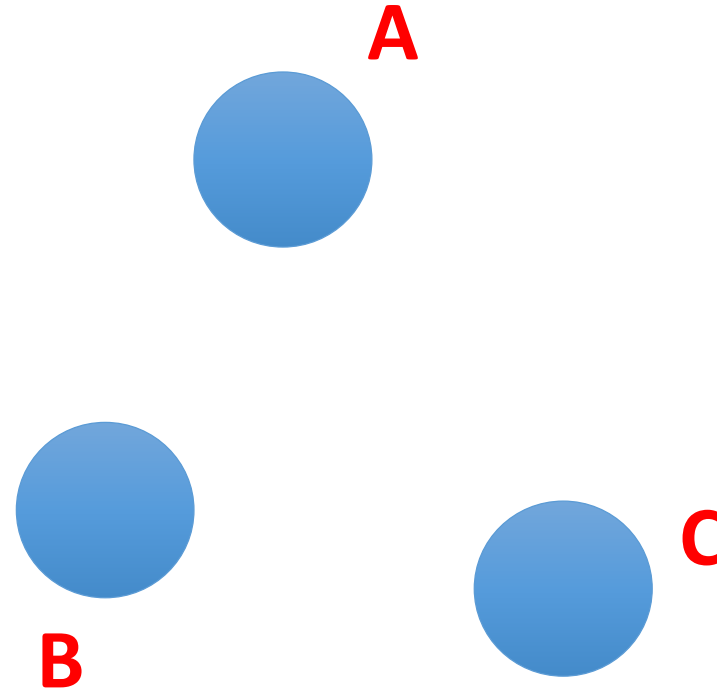We denote the states with circles and give them **symbolic names**, e.g. A, B, and C.




State diagram:

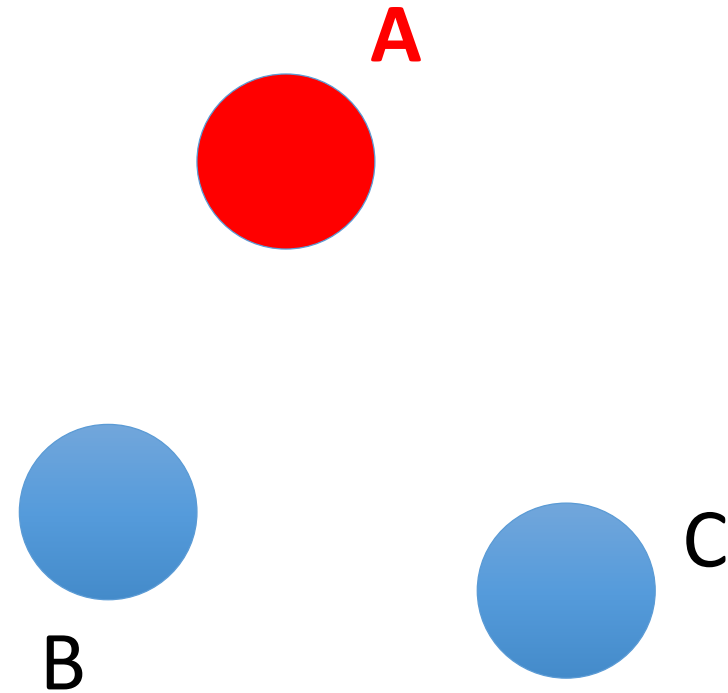


We define one of the states as the **initial state**.

In the beginning...

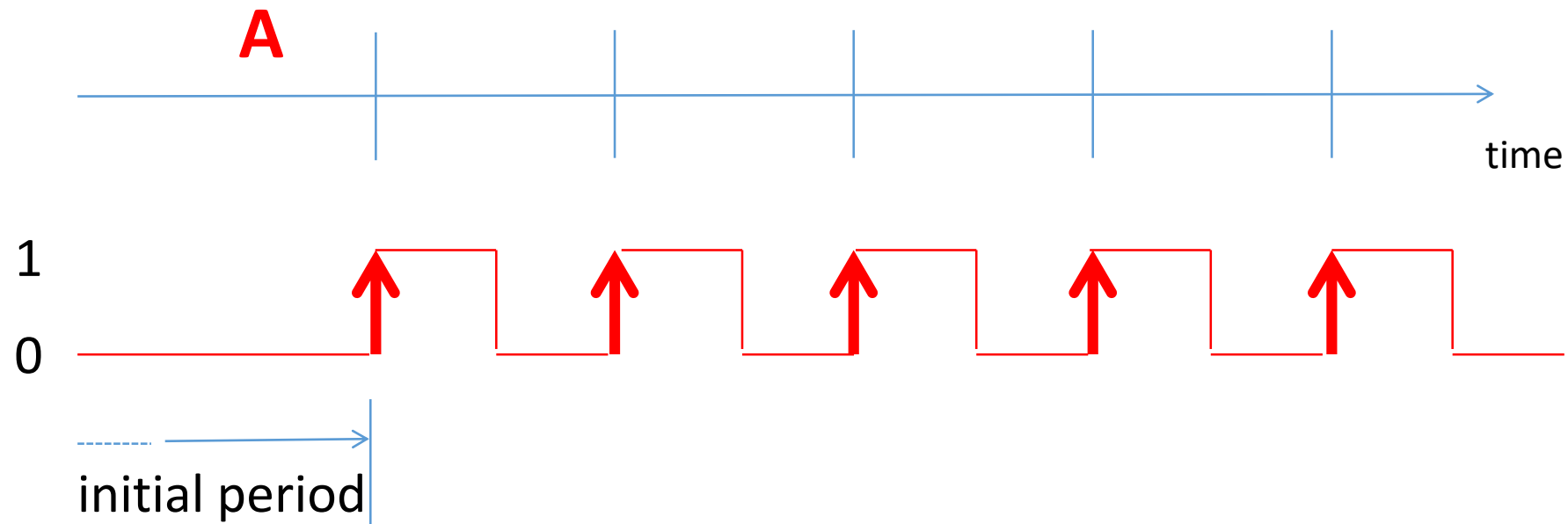

Initially, i.e. shortly after switching on the FSM and **before the first rising edge of clock**, there is the initial period. In this period, the FSM is in the “**initial state**”.


State diagram:

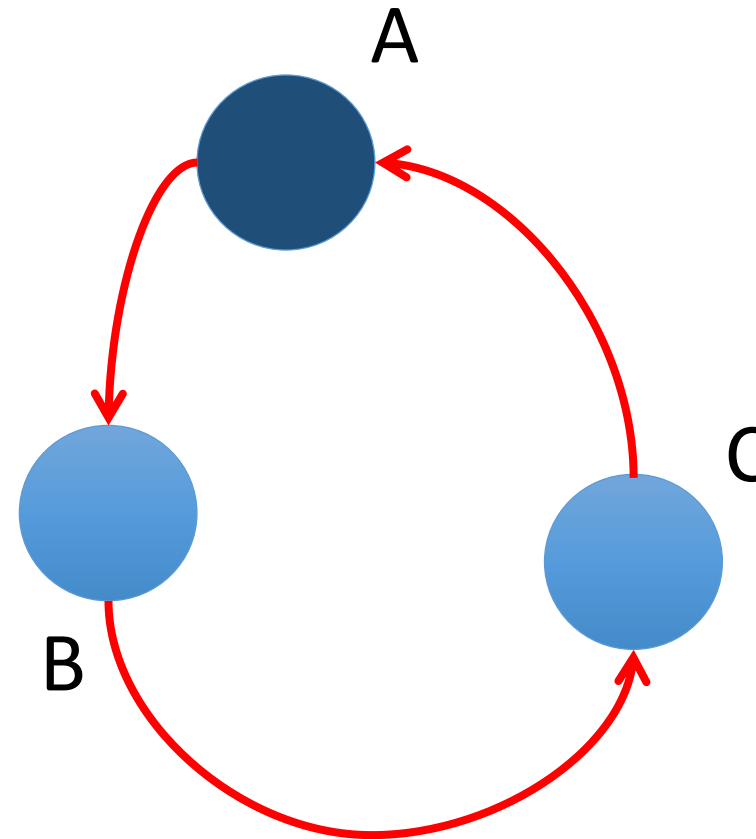


With arrows we
define the **sequence**
of states.

The sequence of states can also be defined in a **state transition table**.

present state	next state
A	B
B	C
C	A

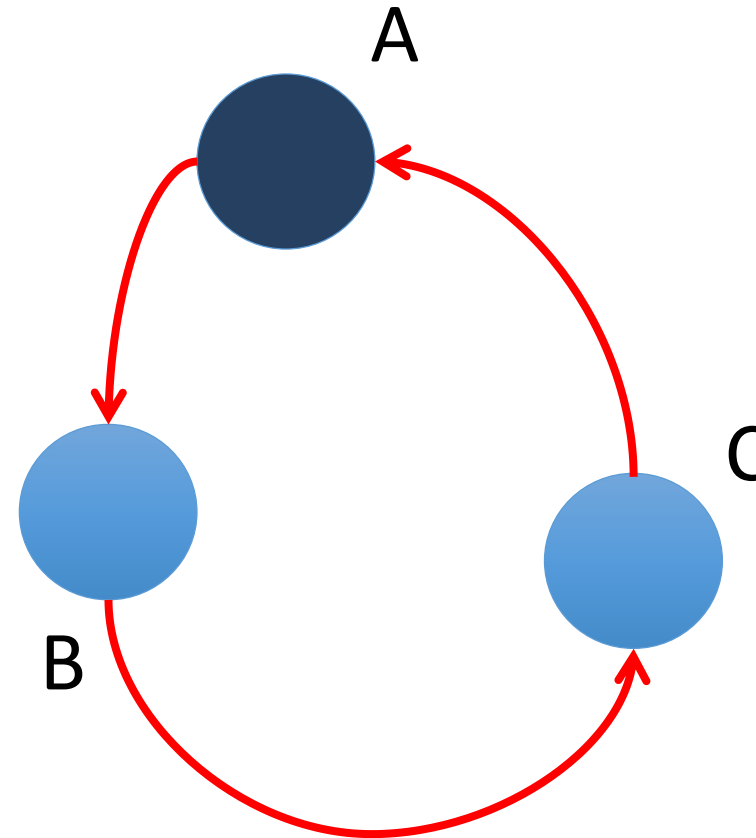

Timing diagram

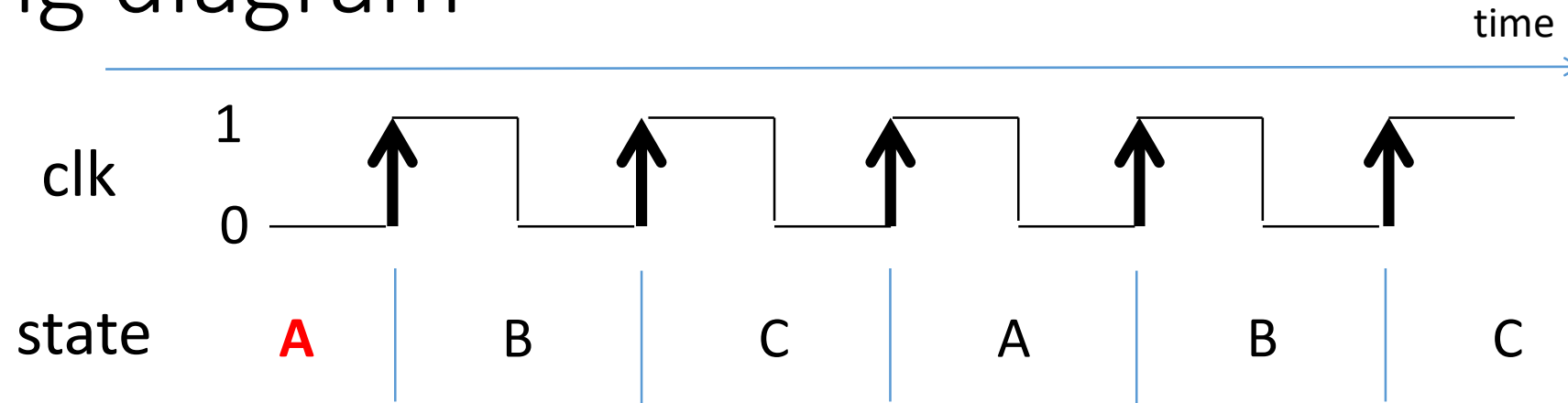


Initially, the FSM is in the **initial state A**.


With every **positive clock edge**, the next state becomes the current state.

An FSM has **always** a next state.

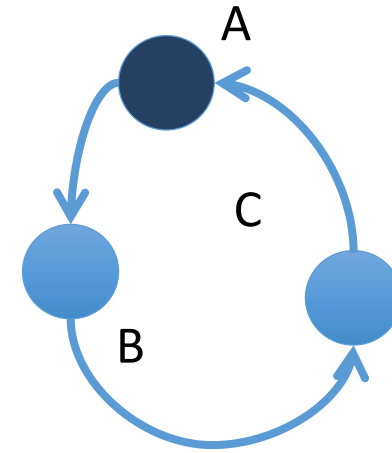In order to technically realize
("implement") a state diagram,
we start by giving
each state
a **unique number**.




Popular state-encoding schemes

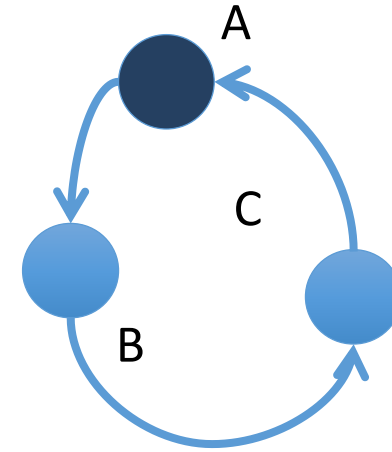


- **Binary encoding**
 - needs minimum amount of flip-flops.
- **One-hot encoding**
 - Tends to have a simpler next-state logic.

Binary encoding

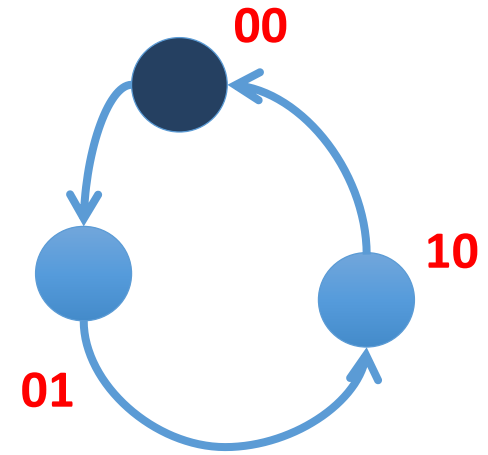

state	number
A	00
B	01
C	10

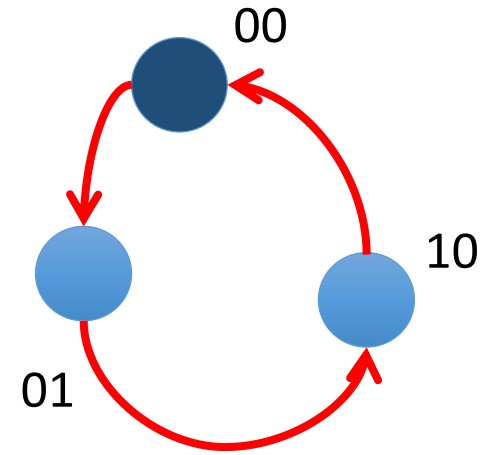


Binary encoding:

The state transition table has also only binary numbers.


present state	next state
00	01
01	10
10	00

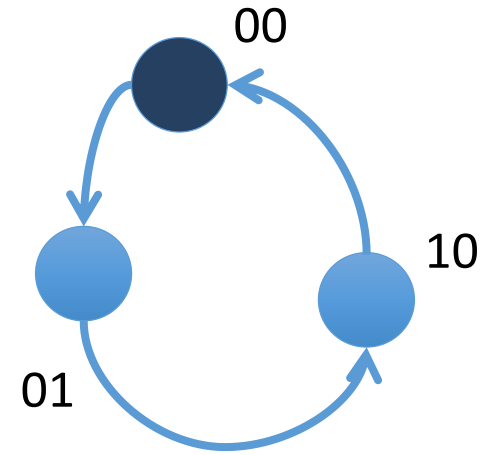We also enter the unused combination “11”.
 This state does not exist.
 “x” stands for “Don’t care”.




present state	next state
00	01
01	10
10	00
11	xx

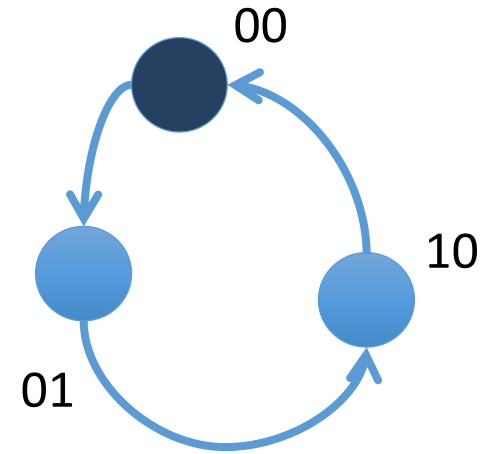We define names for the two state bits, e.g. $s1$, $s0$.




present		next	
$s1$	$s0$	$s1$	$s0$
0	0	0	1
0	1	1	0
1	0	0	0
1	1	x	x

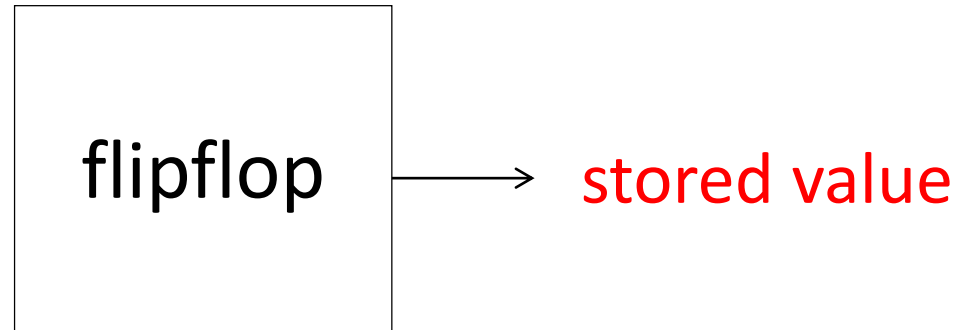Each state bit is **stored** in a **flipflop**




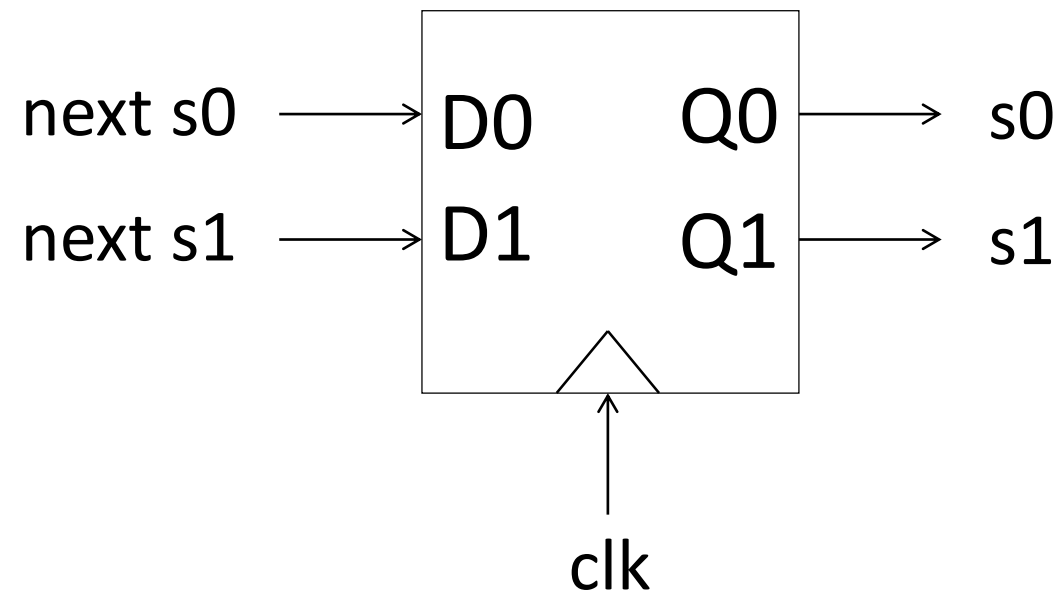In our example, we need 2 flip-flops for storing the state bits.




Flipflops which can store several bits are also called “**registers**”.

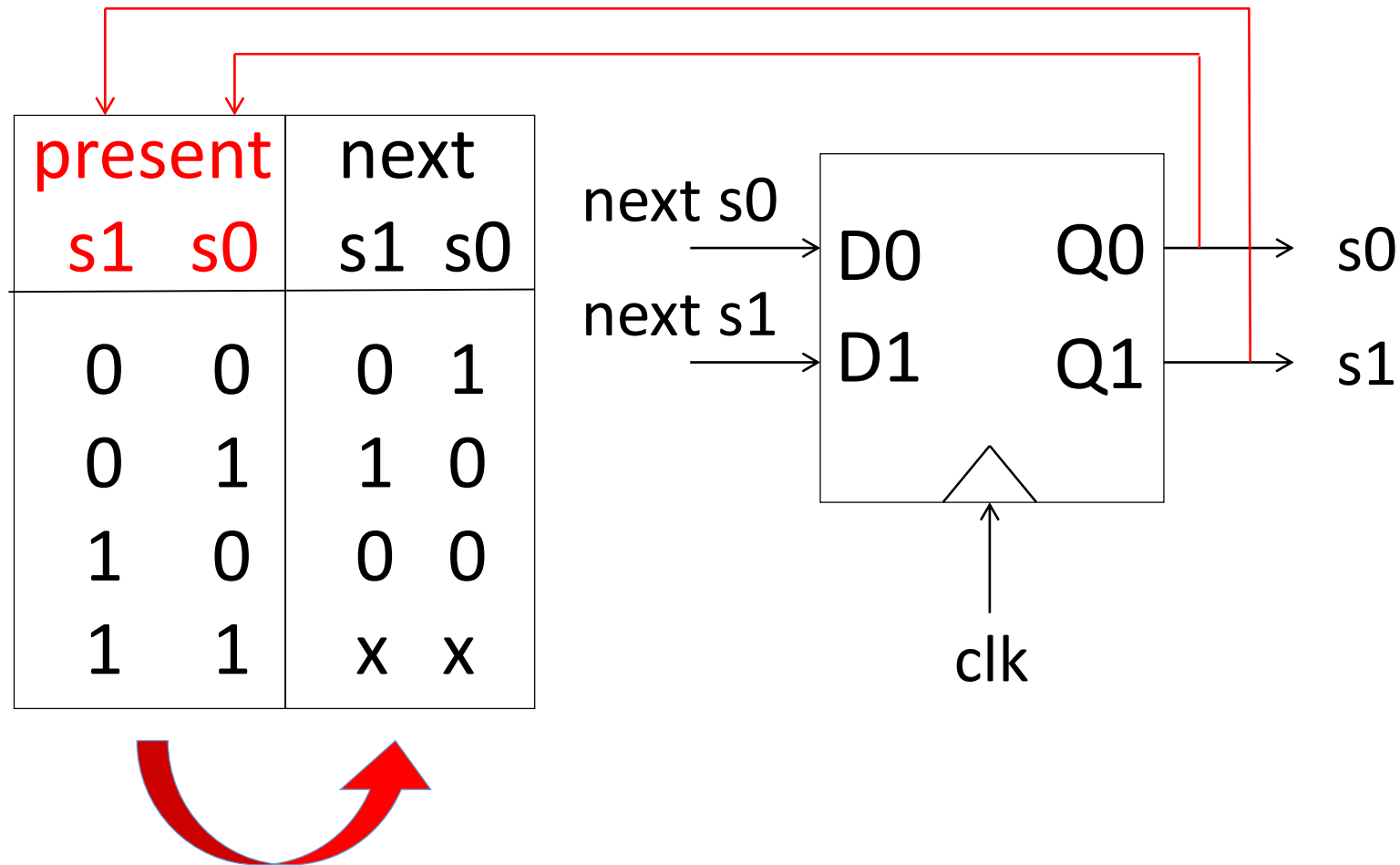
We use the state transition table as a “lookup table” ...




...and thus find out the **next state**

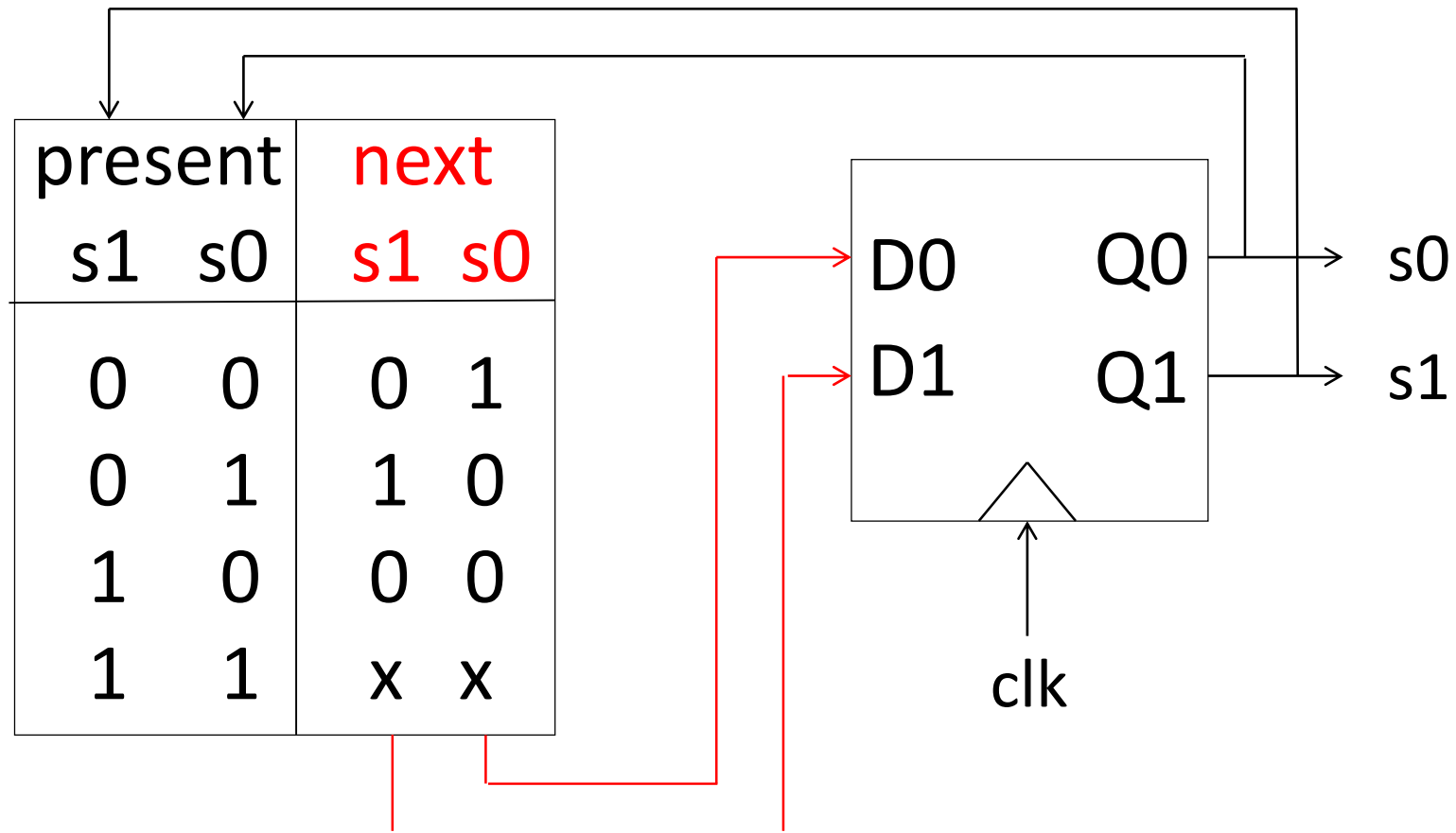

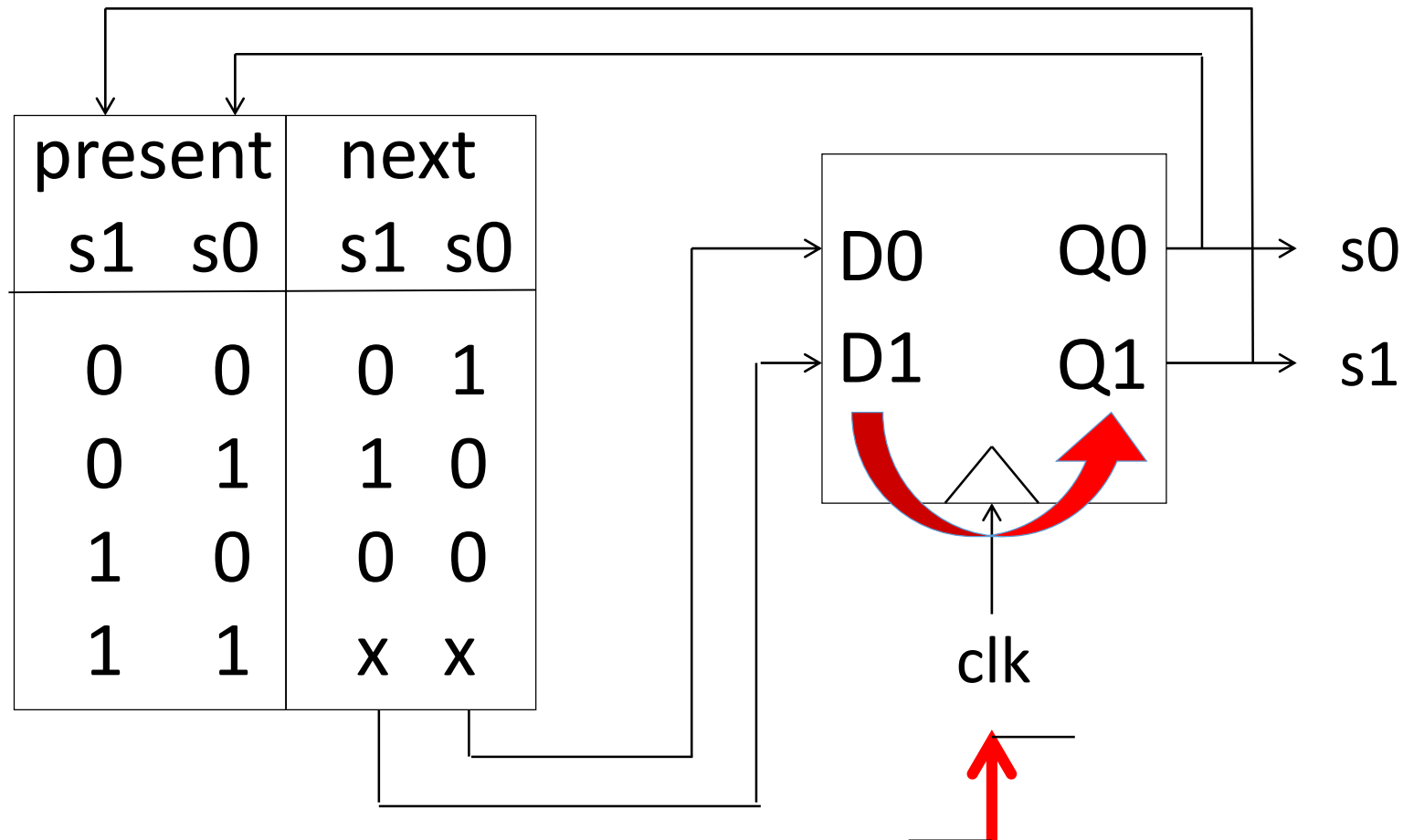At each positive edge of clk, the next state gets stored as the current state.




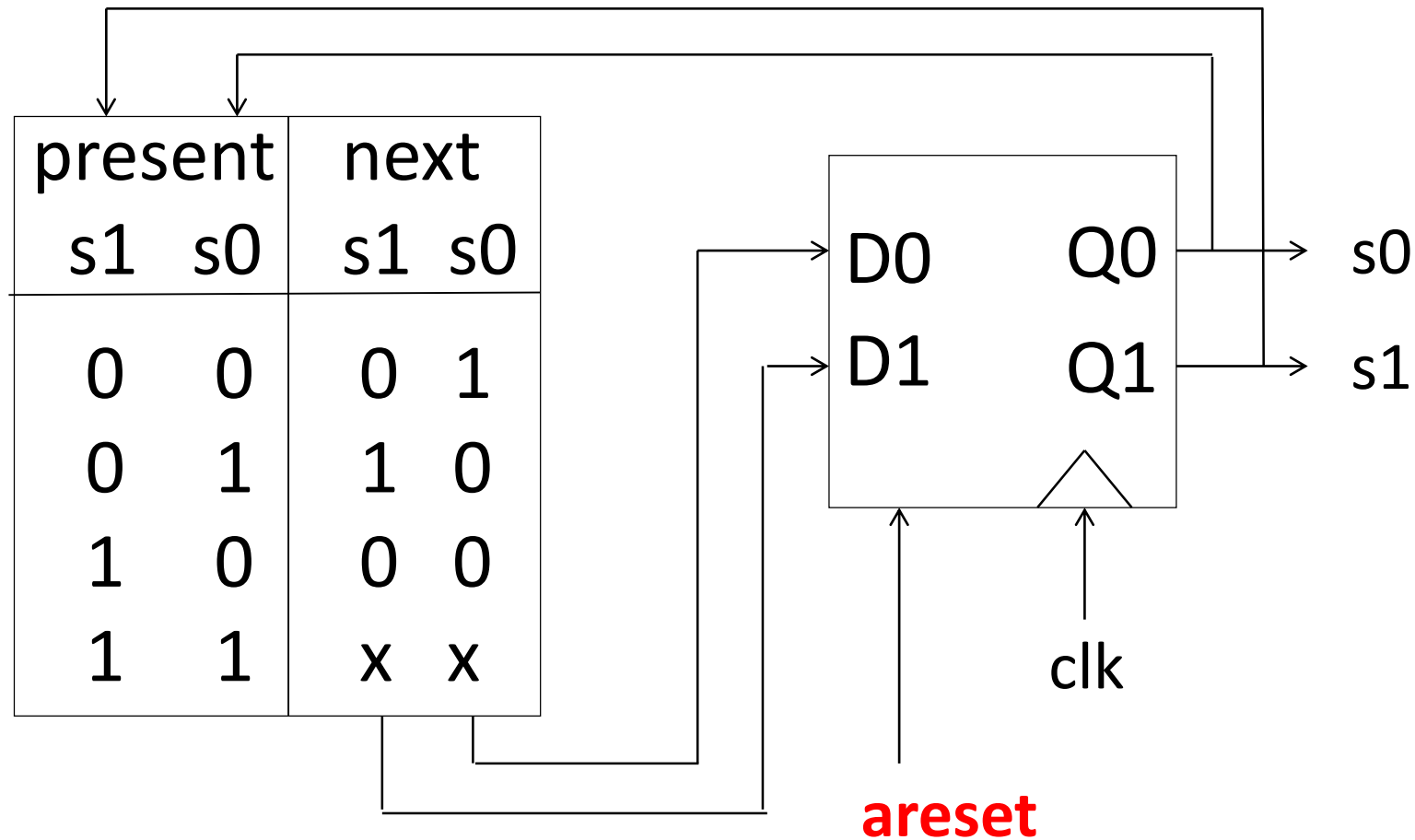In order to get the initial state “00”, we use flipflops with an “**asynchronous reset input**”. Shortly after switching on the circuit, we apply “**areset**”.



The state transition function in this example can be derived from the truth table:
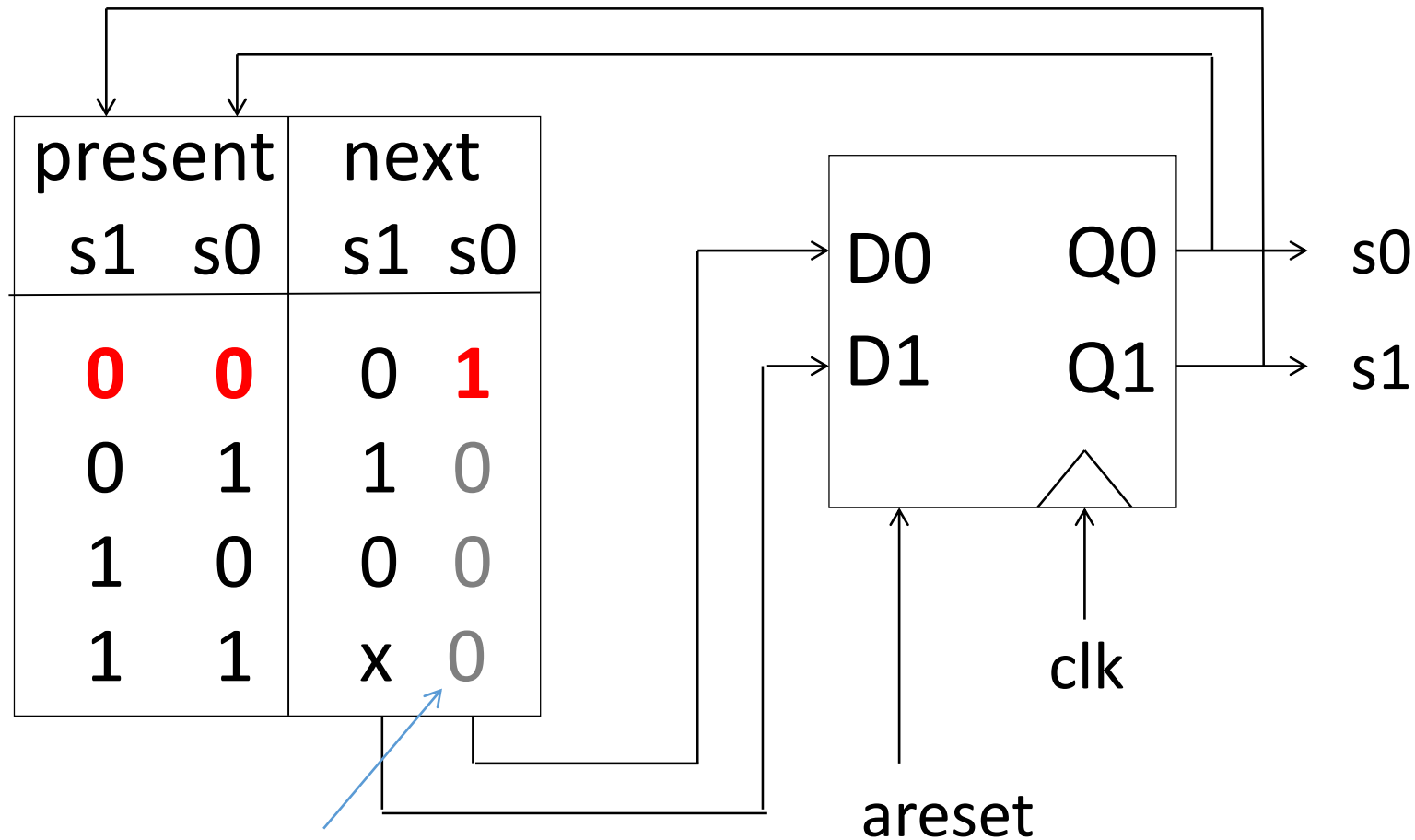
$$\text{next } s0 = (\sim s1) \& (\sim s0)$$




We set the don't care to 0.

The state transition function:


$$\text{next } s0 = (\sim s1) \& (\sim s0)$$

$$\text{next } s1 = (\sim s1) \& s0$$

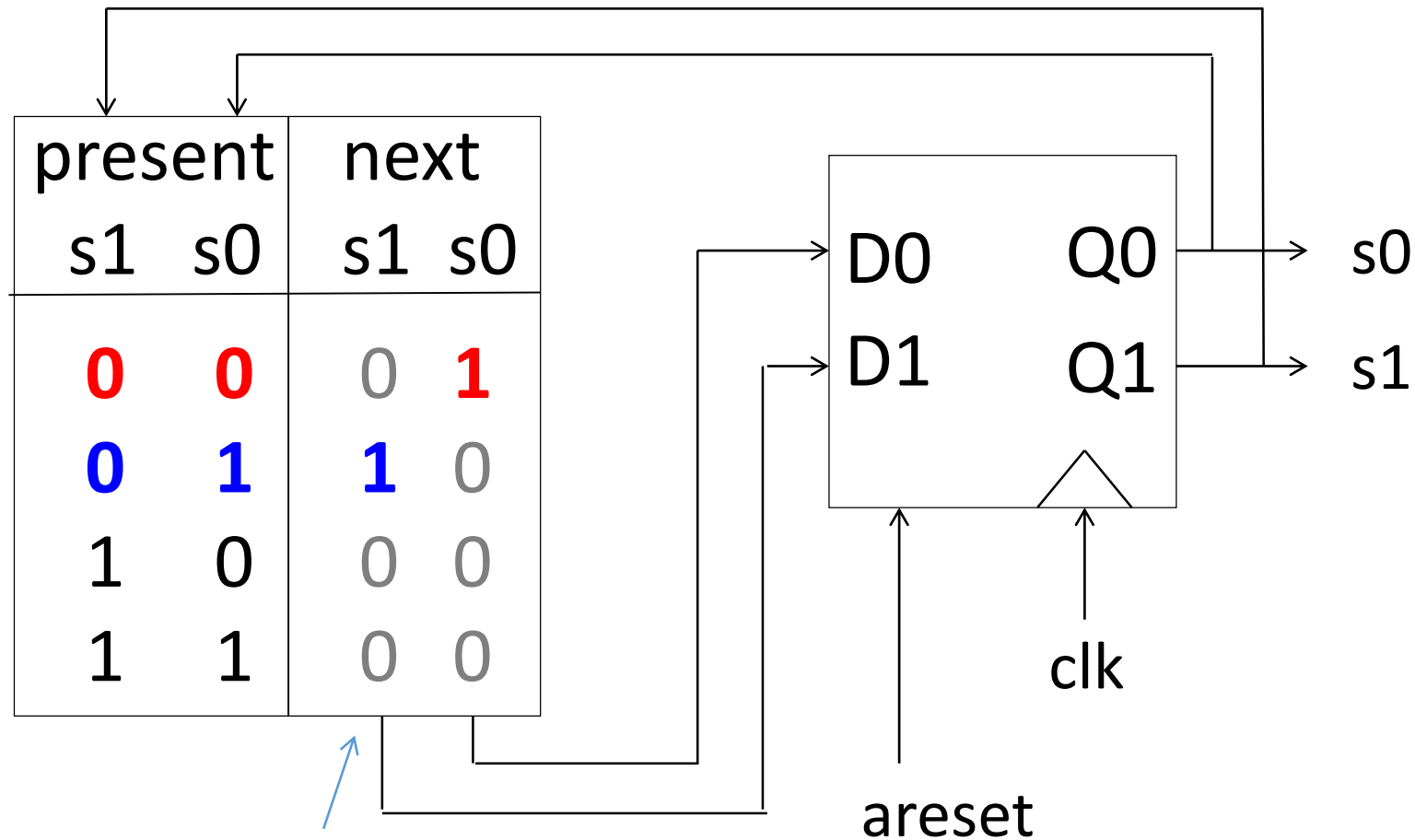

We set this don't care value also to 0.

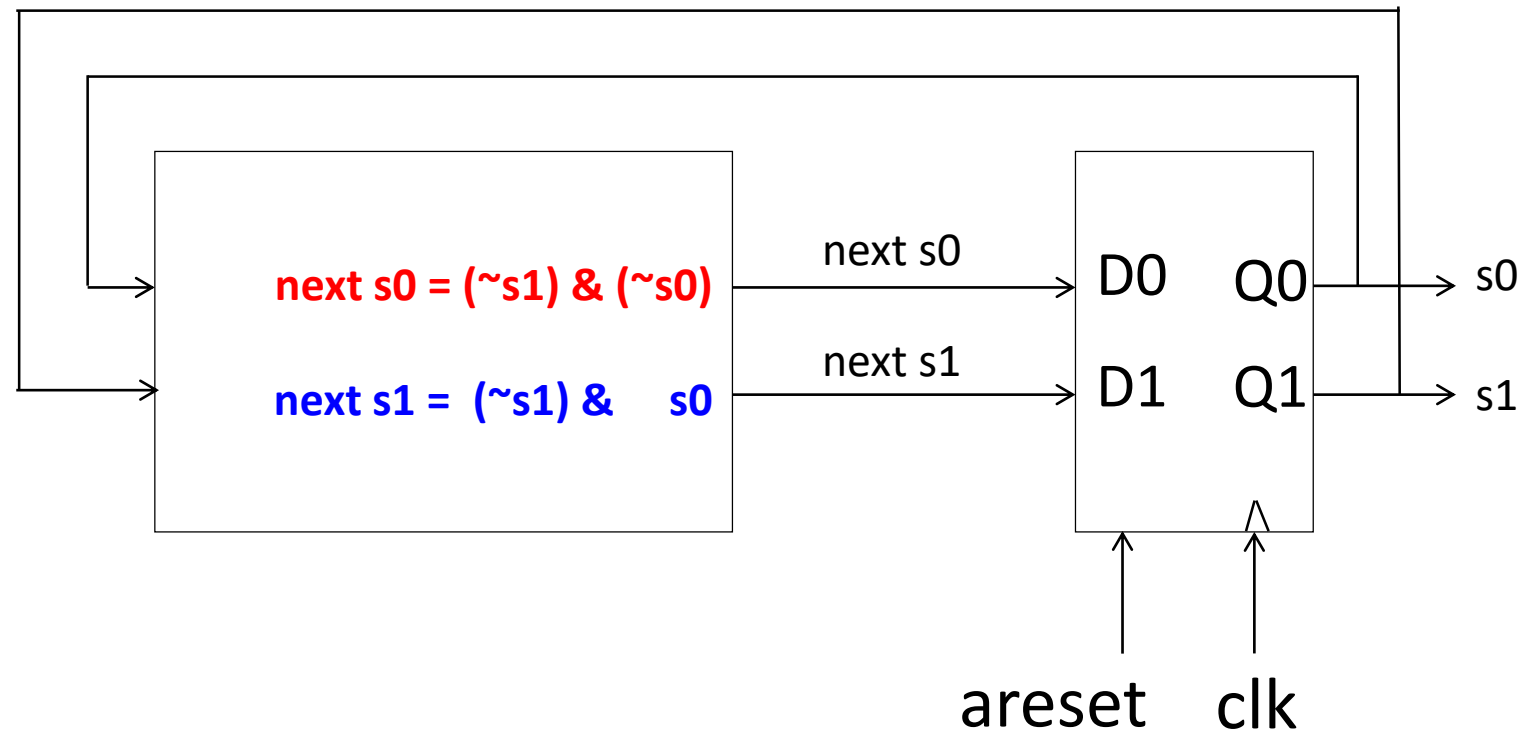Structural diagram of the FSM:
State-transition function,
storage elements, and feedback of state.



Essence so far


State diagram:

“next state” is a function of (present) “state”

State transitions:

the “next state” becomes (the present) “state”
on the rising edge of the clock

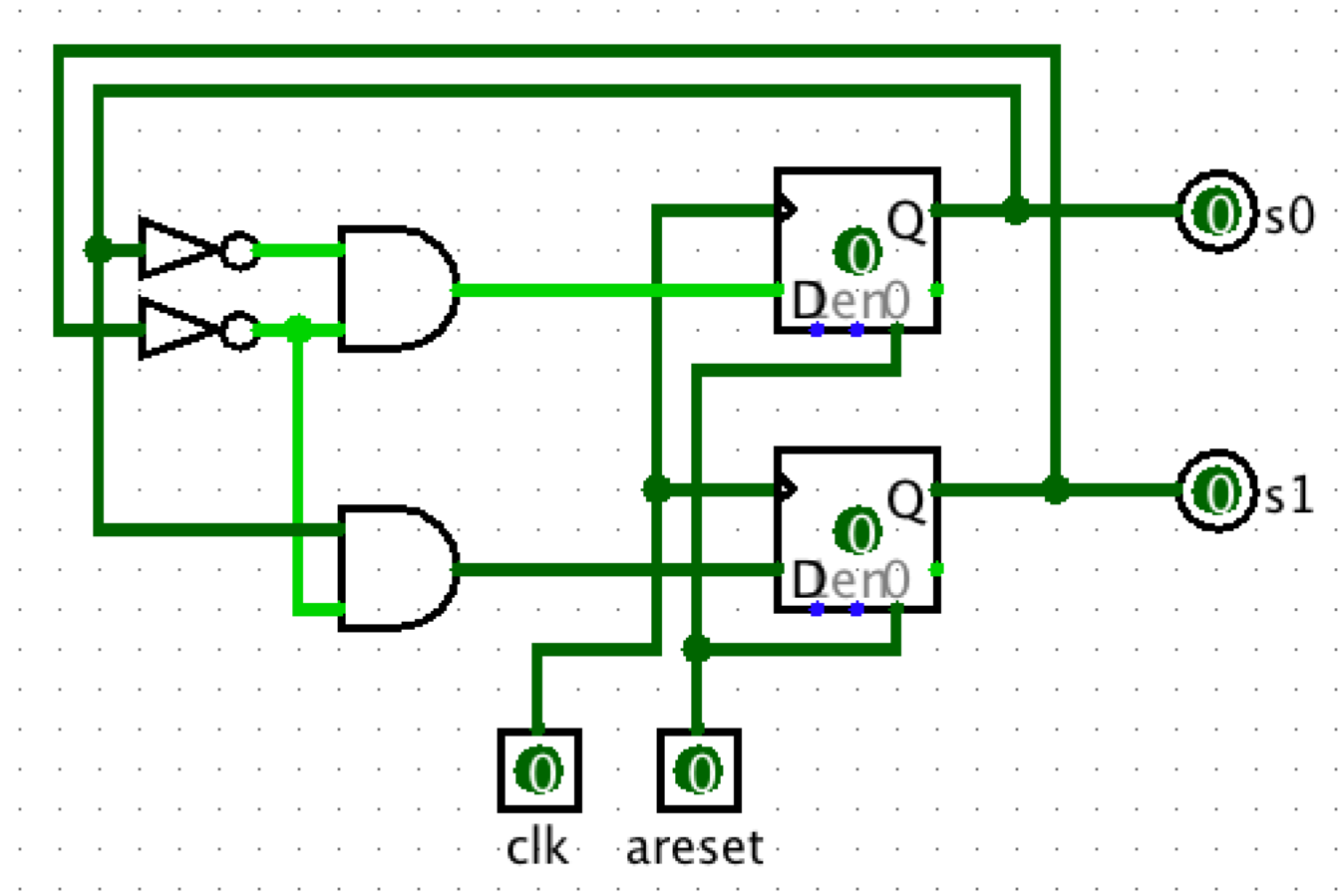The FSM modeled and simulated with Digital



For an example of this FSM see


fsm_moore_no_input

Inputs

FSMs can also have **inputs** influencing the transition to the next state

next state = $f(\text{state}, \text{input})$

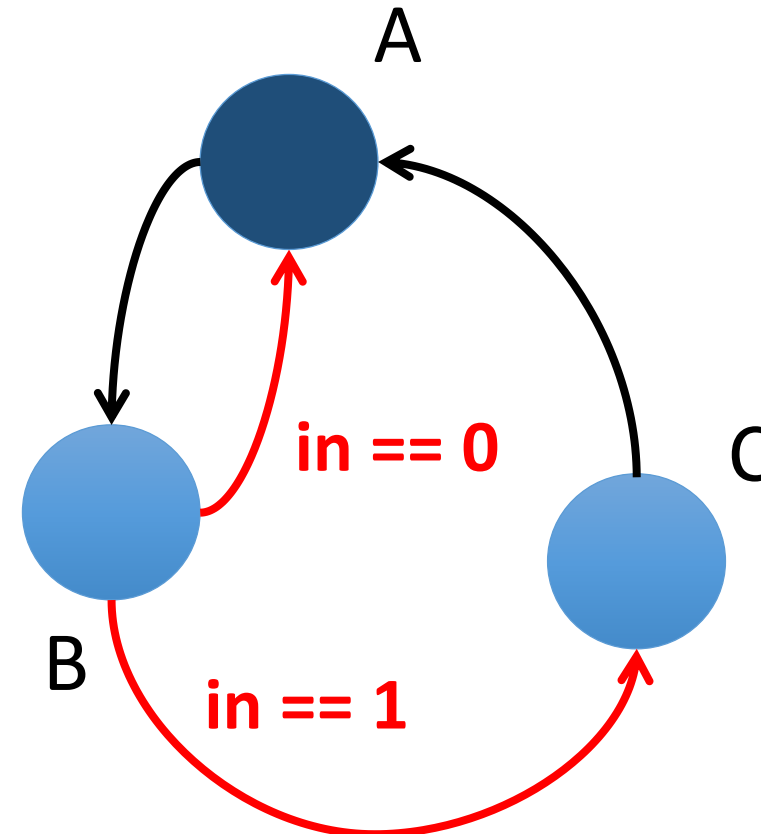In this example we see that the one-bit input "in" influences the choice of the state after B.




FSMs can also have **inputs** influencing the transition to the next state

$$\text{next state} = f(\text{state}, \text{input})$$


In this example we see that the one-bit input “**in**” influences the choice of the state after B.

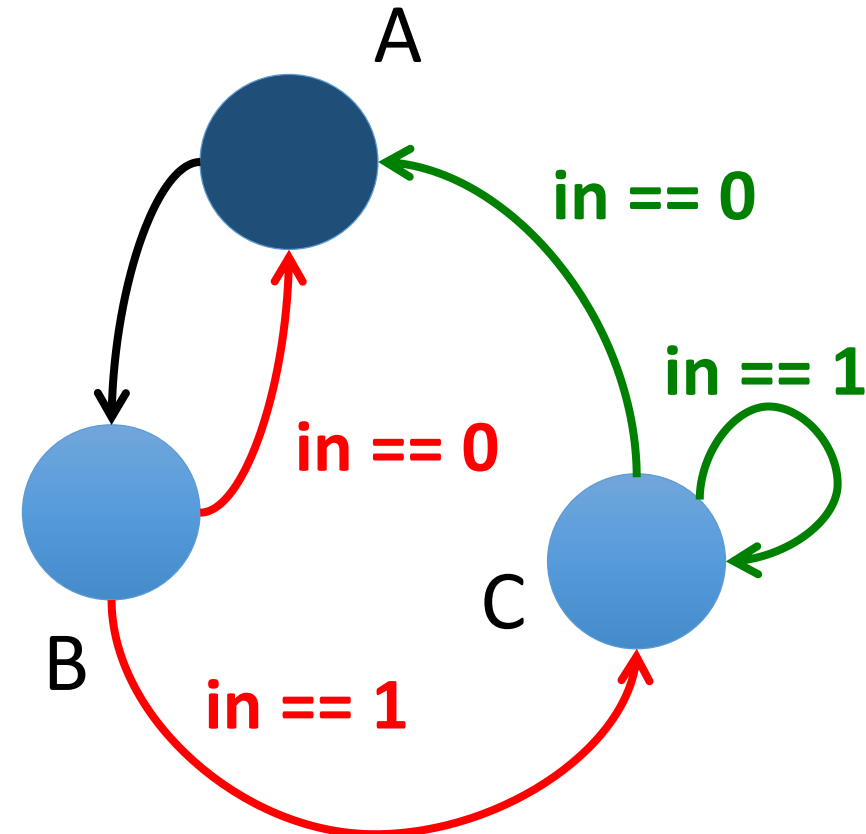The following state can also be the same as the current state.




The state transition table

present state	in	next state
A	0	B
A	1	B
B	0	A
B	1	C
C	0	A
C	1	C

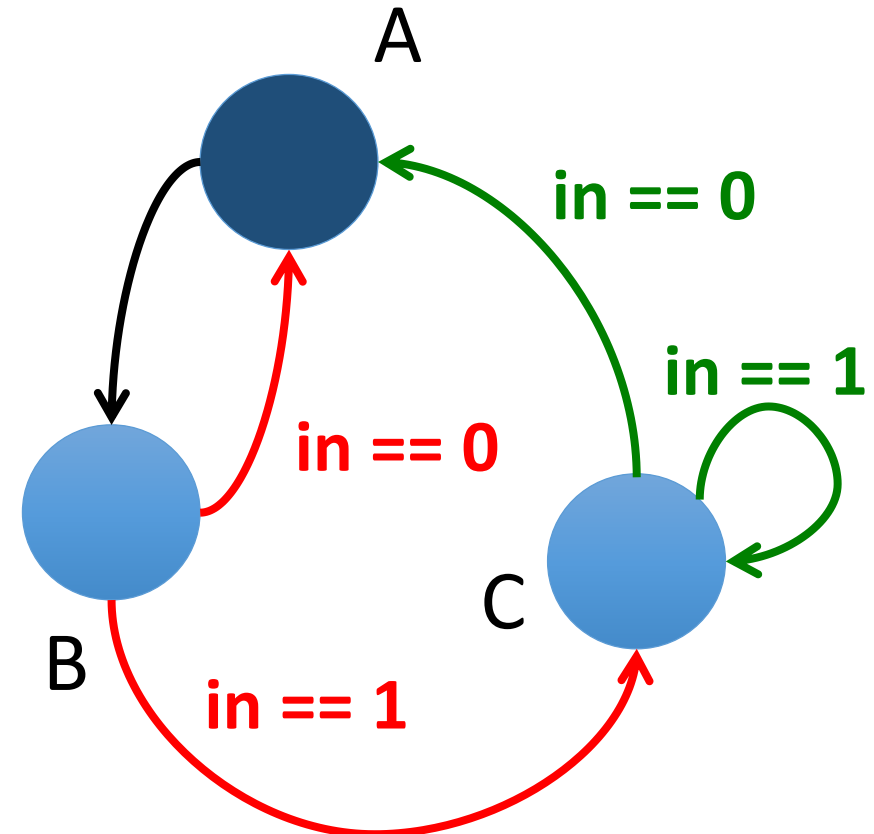


Timing diagram. Example 1

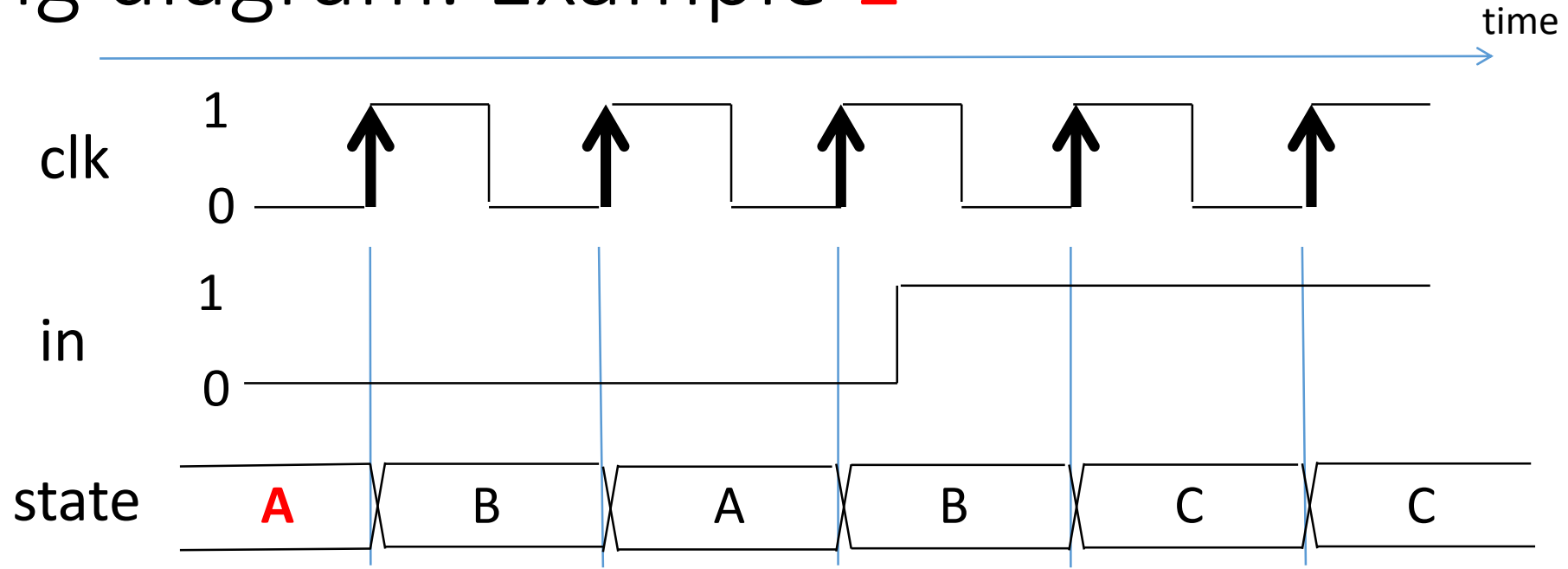


For a timing diagram, we need to choose values for the input signal “in”. Only after some choice for “in” we can derive the sequence of states from the state diagram.

Timing diagram. Example 2

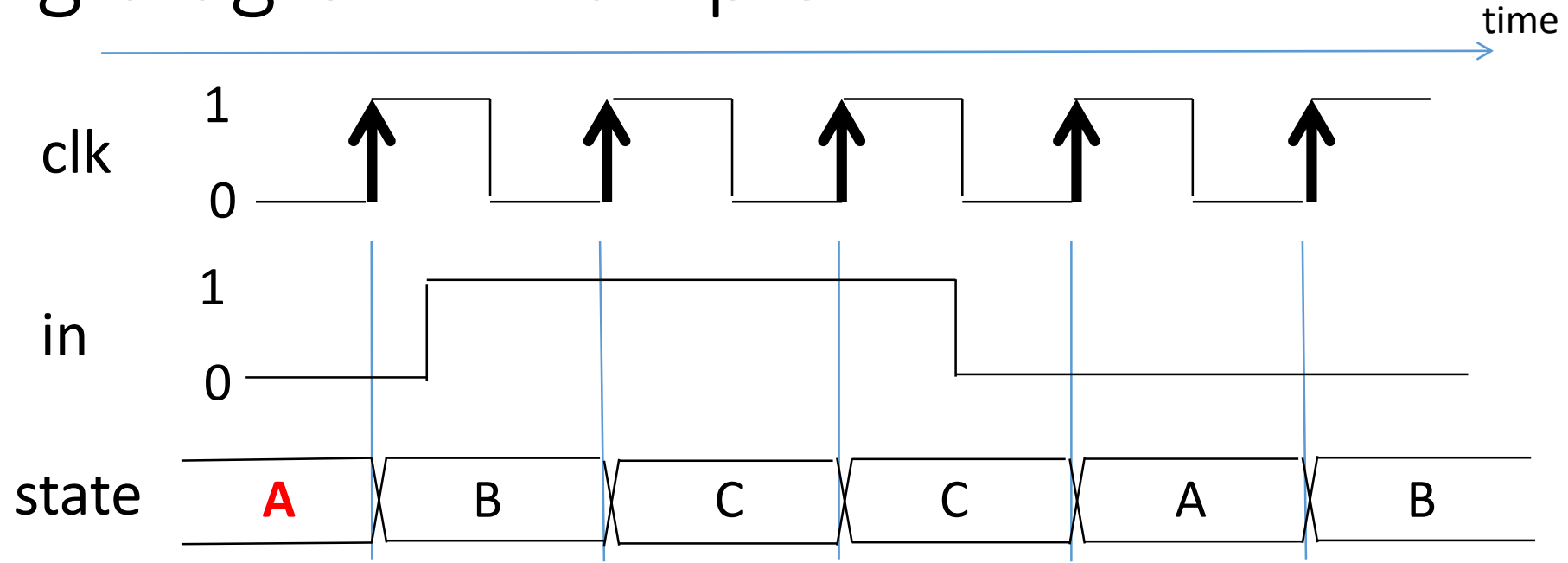

For a timing diagram, we need to choose values for the input signal “in”. Only after some choice for “in” we can derive the sequence of states from the state diagram.


Timing diagram. Example 3

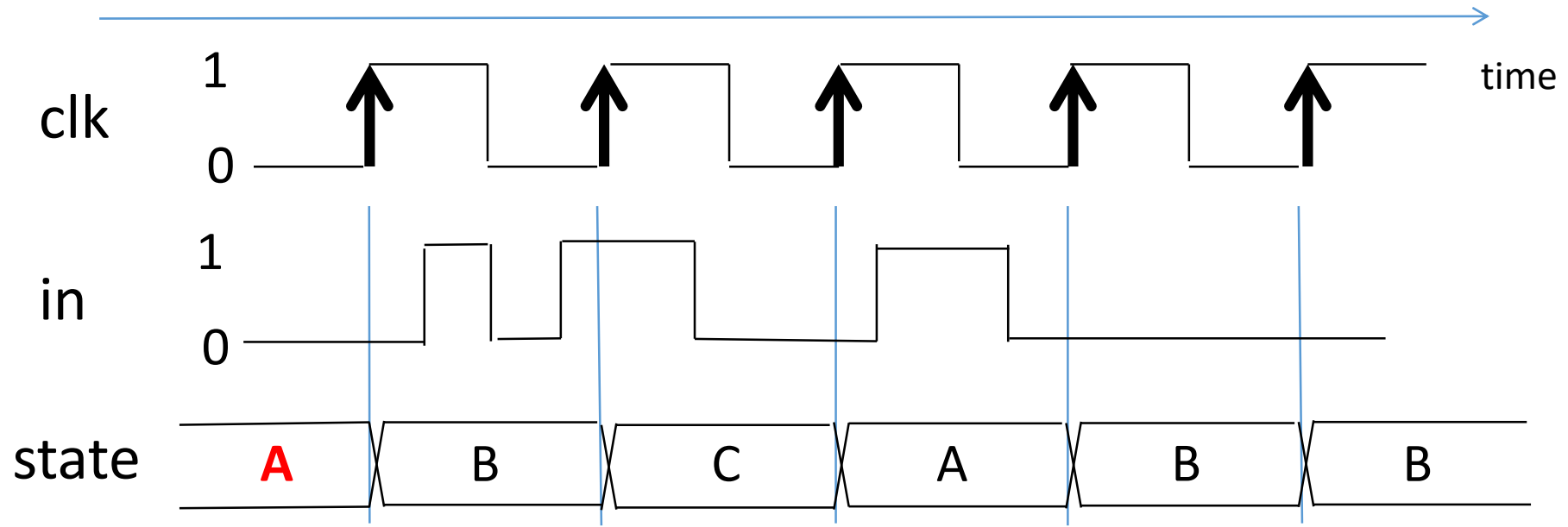

For a timing diagram, we need to choose values for the input signal “in”. Only after some choice for “in” we can derive the sequence of states from the state diagram.


Binary state encoding: Instead of symbolic state names we use numbers

present state		in	next state	
0	0	0	0	1
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0

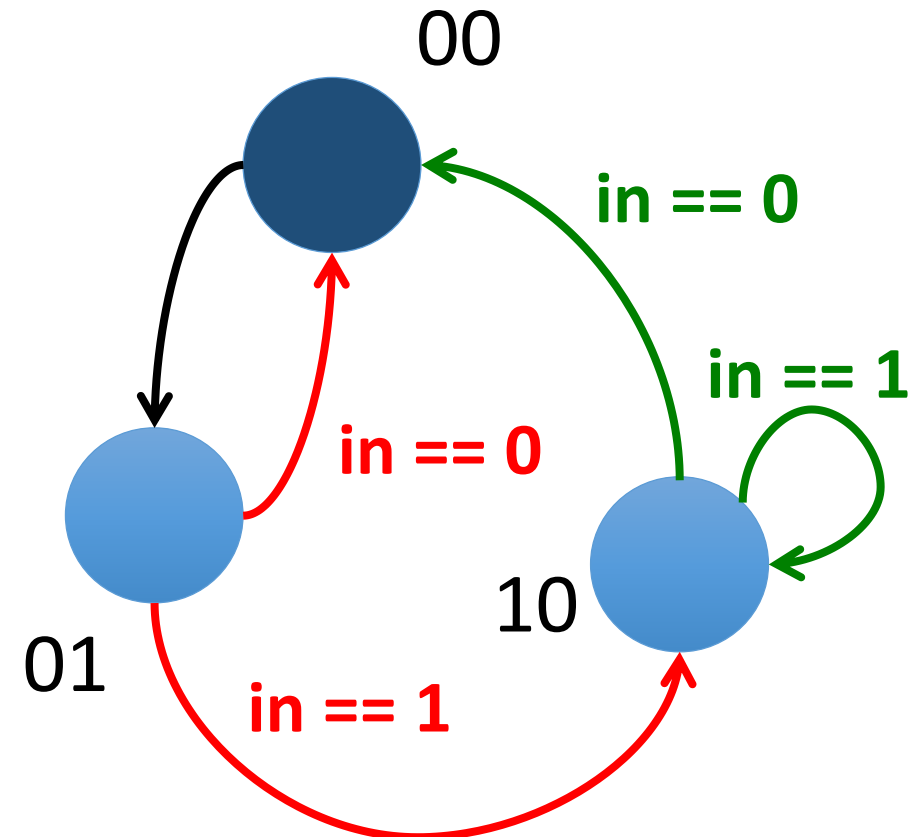

“11” does not exist: We use “Don’t Care” as the following state


present state		in	next state	
0	0	0	0	1
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	x	x
1	1	1	x	x

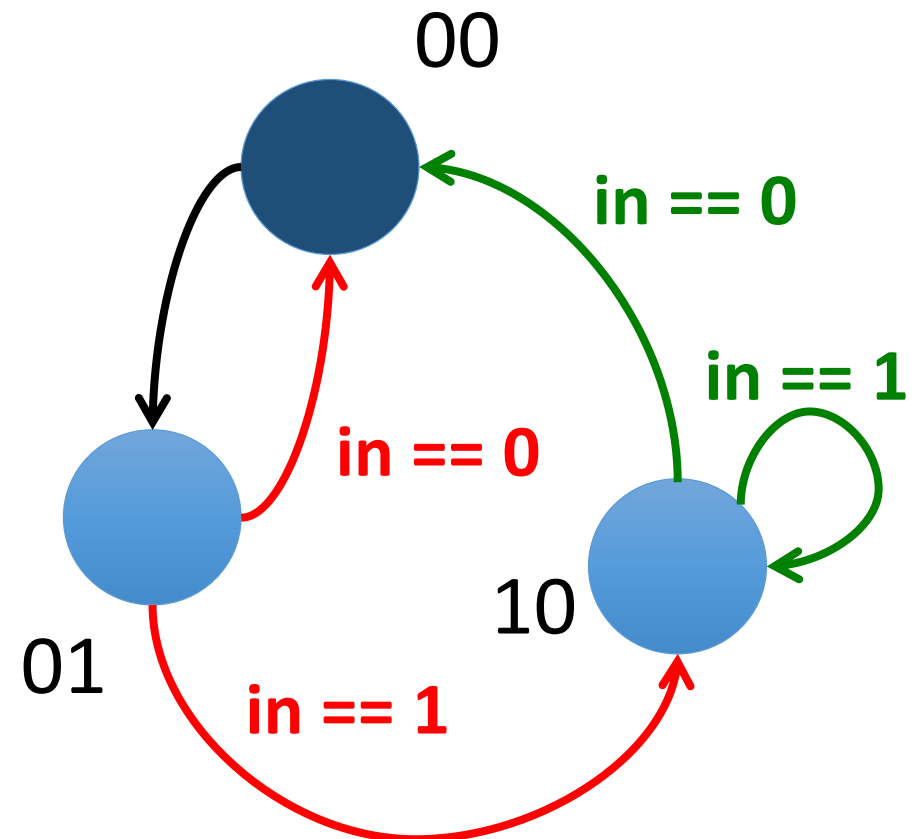

I have ordered the lines in the state transition table from 0 to 7. This makes it easier to “read” the table.


	present state		in	next state	
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	0
5	1	0	1	1	0
6	1	1	0	x	x
7	1	1	1	x	x

↑

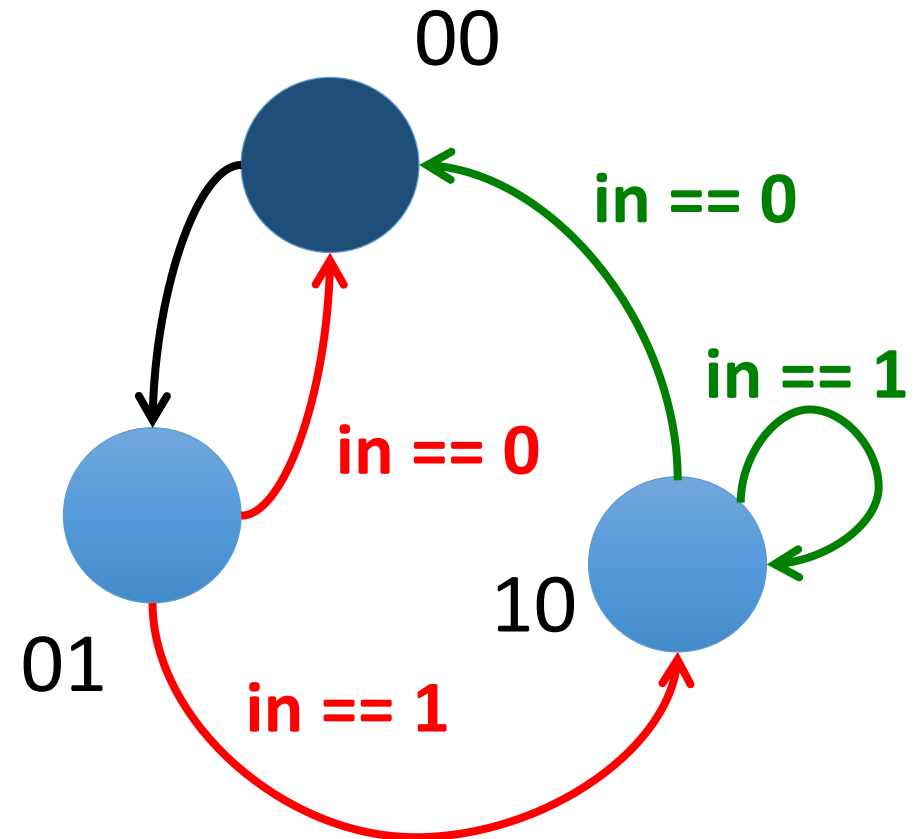


We call the state bits “s1” and “s0”

	present		in	next	
	s1	s0		s1	s0
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	0
5	1	0	1	1	0
6	1	1	0	x	x
7	1	1	1	x	x

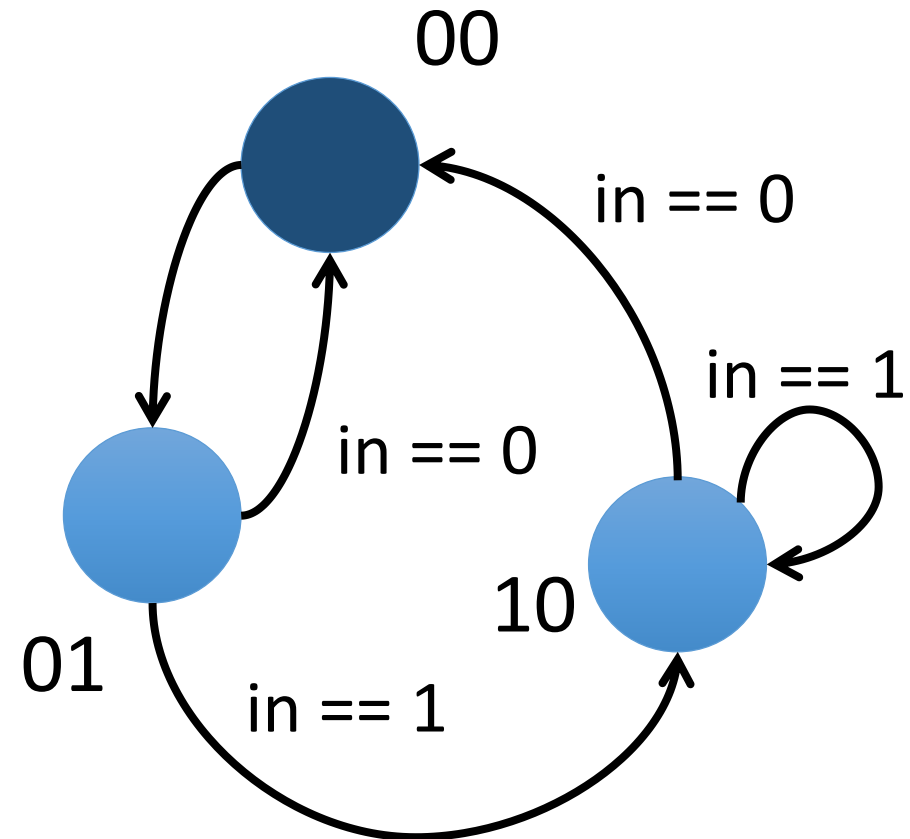


$$\text{next } s0 = \begin{aligned} & ((\sim s1) \& (\sim s0) \& (\sim in)) \\ & | ((\sim s1) \& (\sim s0) \& in) \end{aligned}$$

	present		in	next	
	s1	s0		s1	s0
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	0
5	1	0	1	1	0
6	1	1	0	x	0
7	1	1	1	x	0

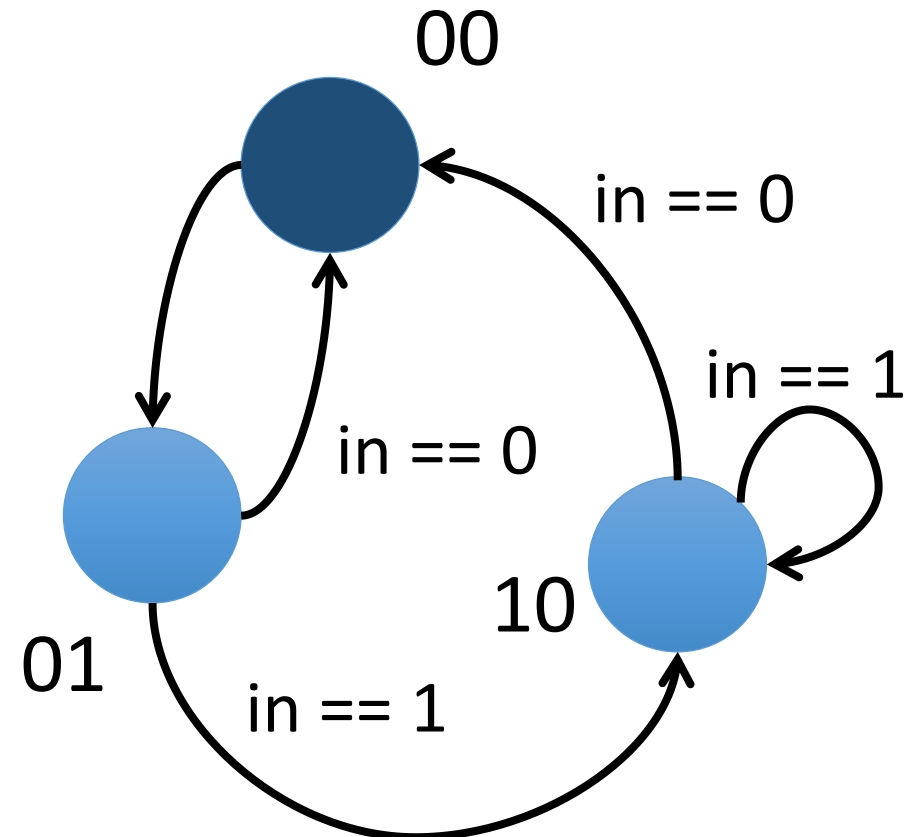


$$\text{next } s1 = ((\sim s1) \& s0 \& \text{in}) \mid (s1 \& (\sim s0) \& \text{in})$$


	present		in	next	
	s1	s0		s1	s0
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	0
5	1	0	1	1	0
6	1	1	0	0	0
7	1	1	1	0	0

 

Structural diagram of the FSM

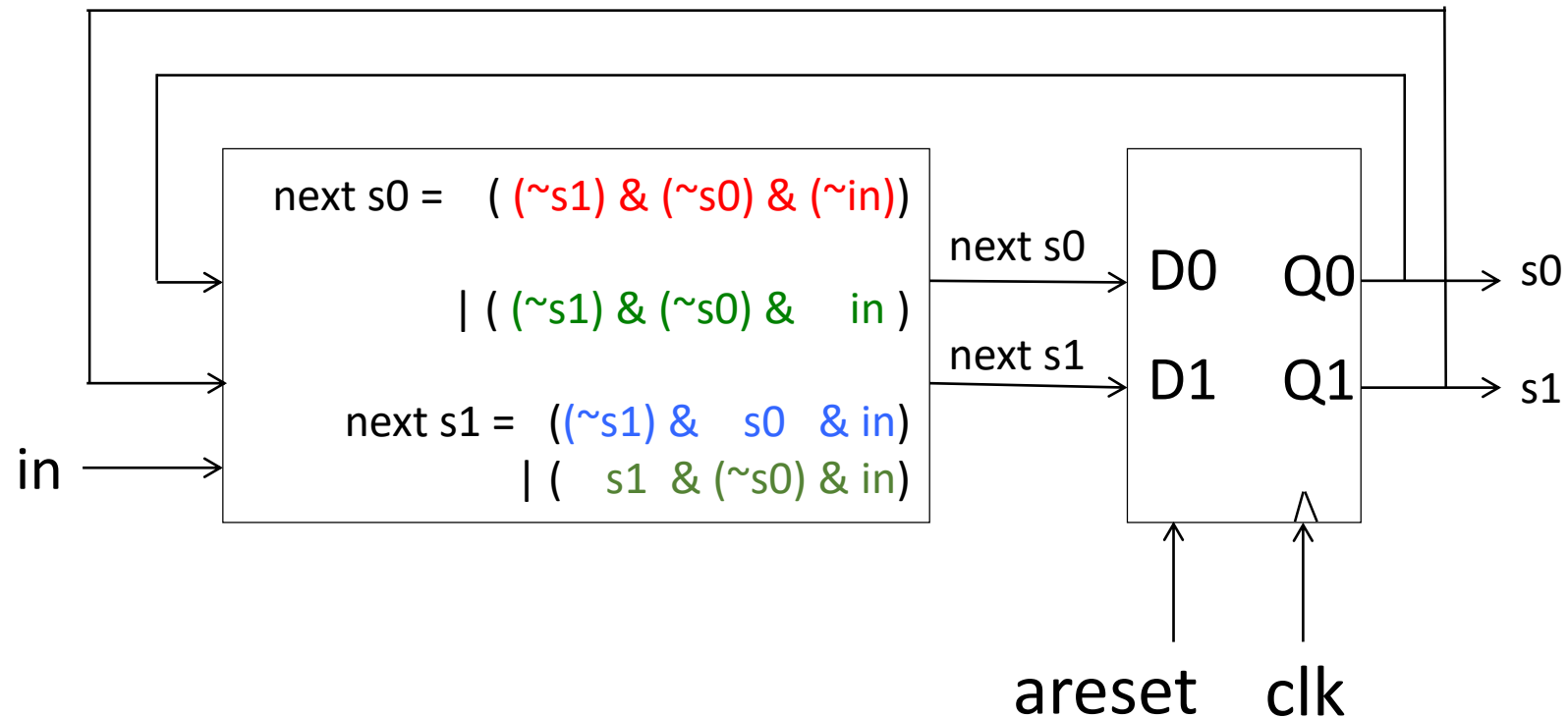

Implementation with Digital

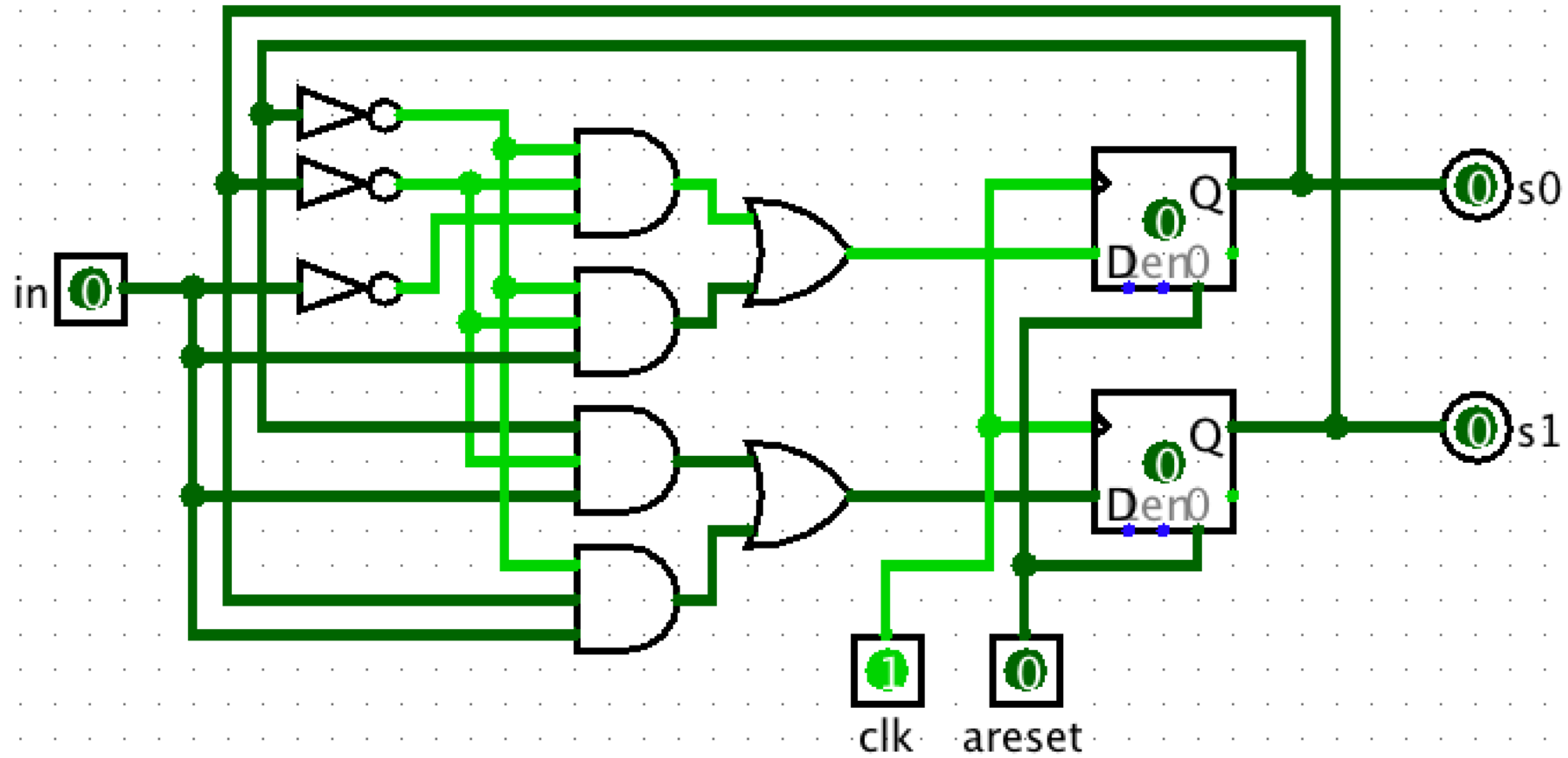

For an example of this FSM see

fsm_moore_no_output_function


Outputs

FSMs typically also have **outputs**

In this example we see that the outputs are a function of the state. We write the output values into the circles.

We call such machines also **“Moore machines”**:

output = f(state)

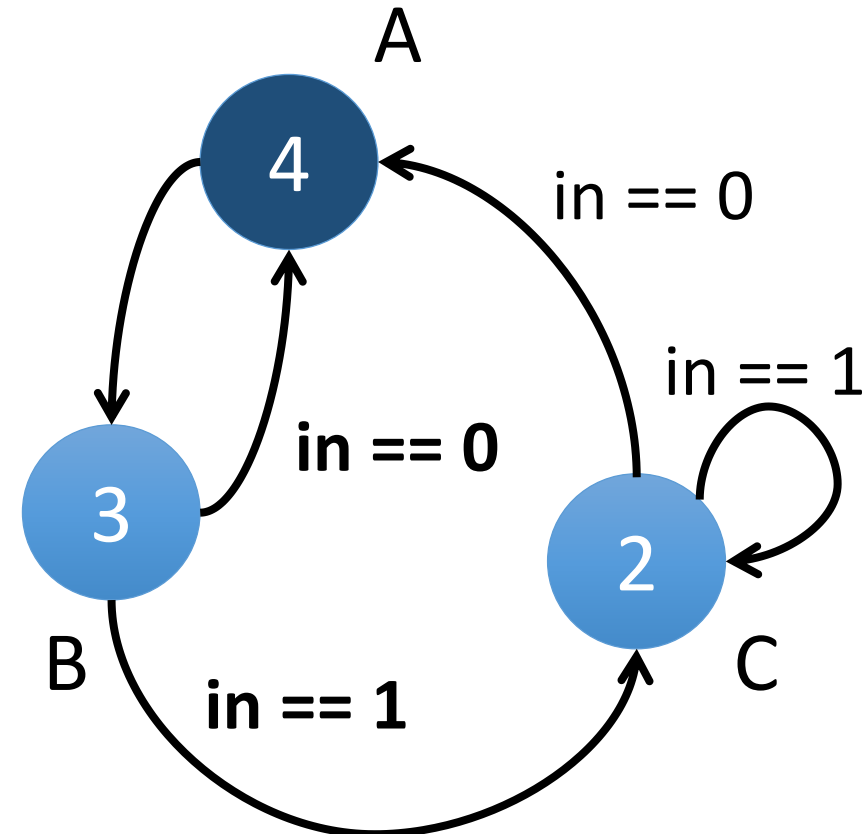


We define the outputs with the “output function”


Moore machines:

output = f(state)

state	output
A	4
B	3
C	2

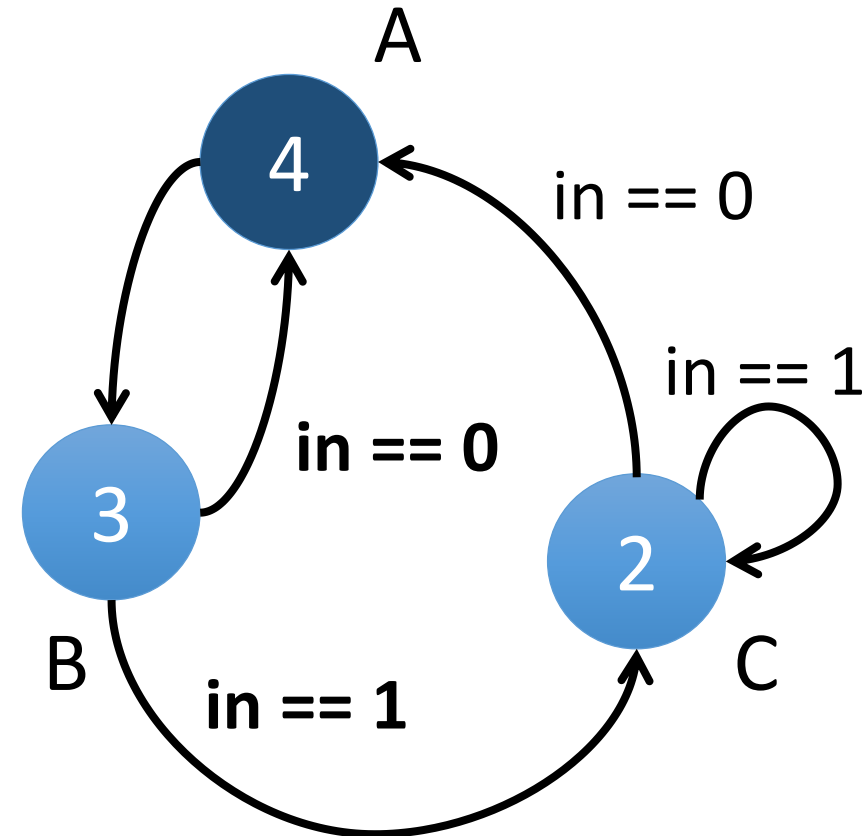

Timing diagram. Example 3

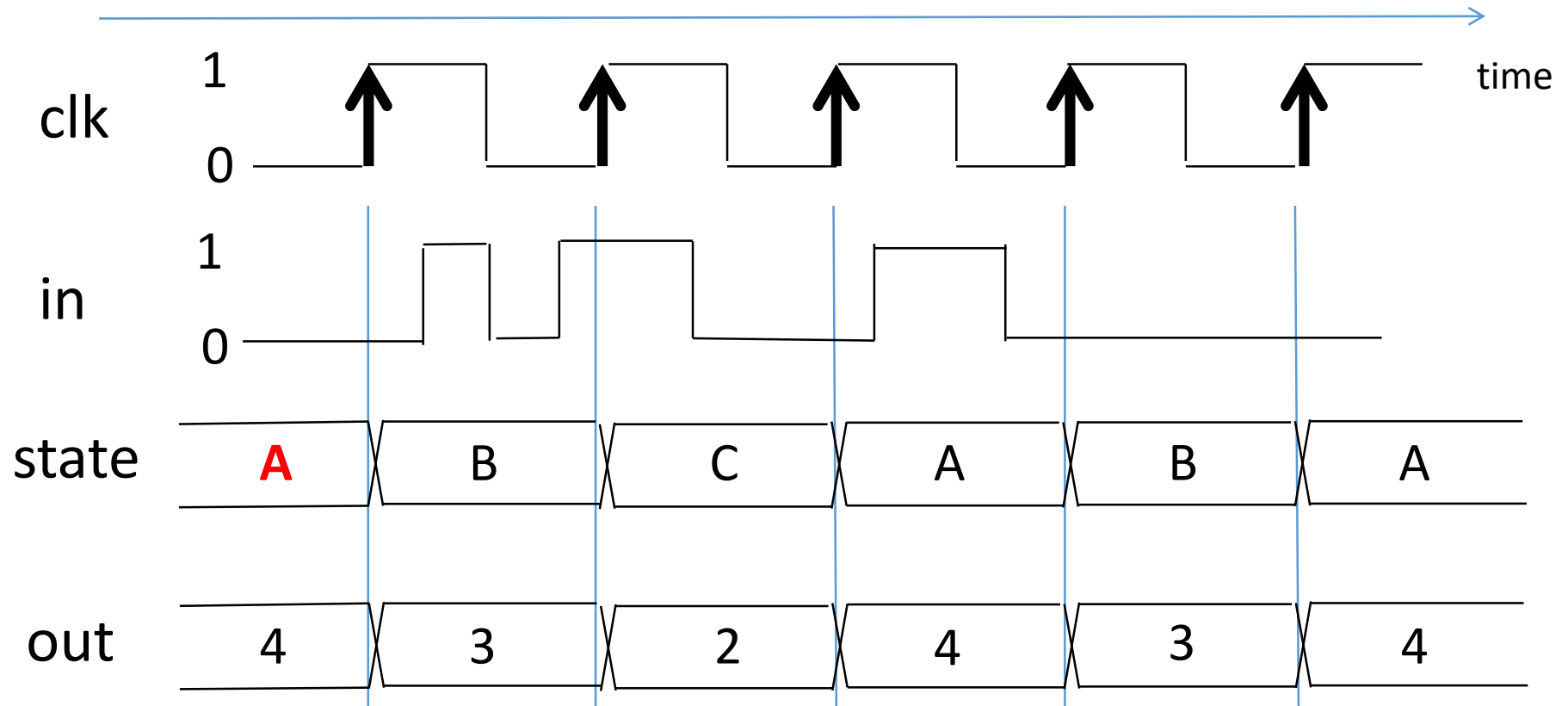


For a timing diagram, we need to choose values for the input signal “in”. Only after some choice for “in” we can derive the sequence of states from the state diagram.

We define the outputs with binary values

Moore machines:

output = f(state)

state	output
A	100 (=4)
B	011 (=3)
C	010 (=2)

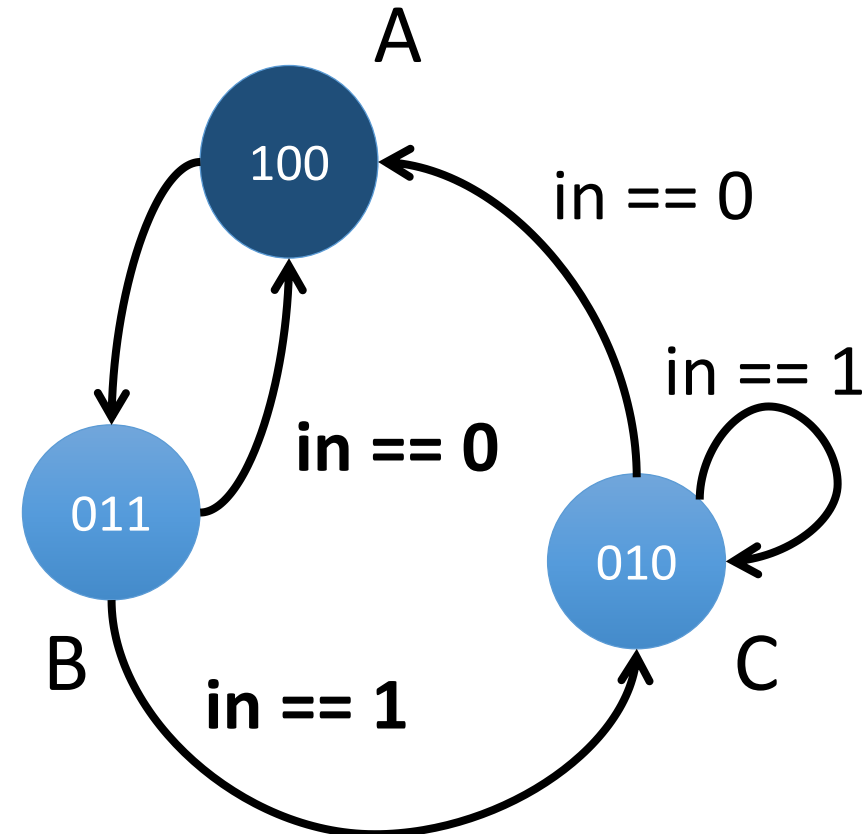


We define the outputs with binary values

Moore machines:

output = f(state)


state	o2	o1	o0
A	1	0	0
B	0	1	1
C	0	1	0

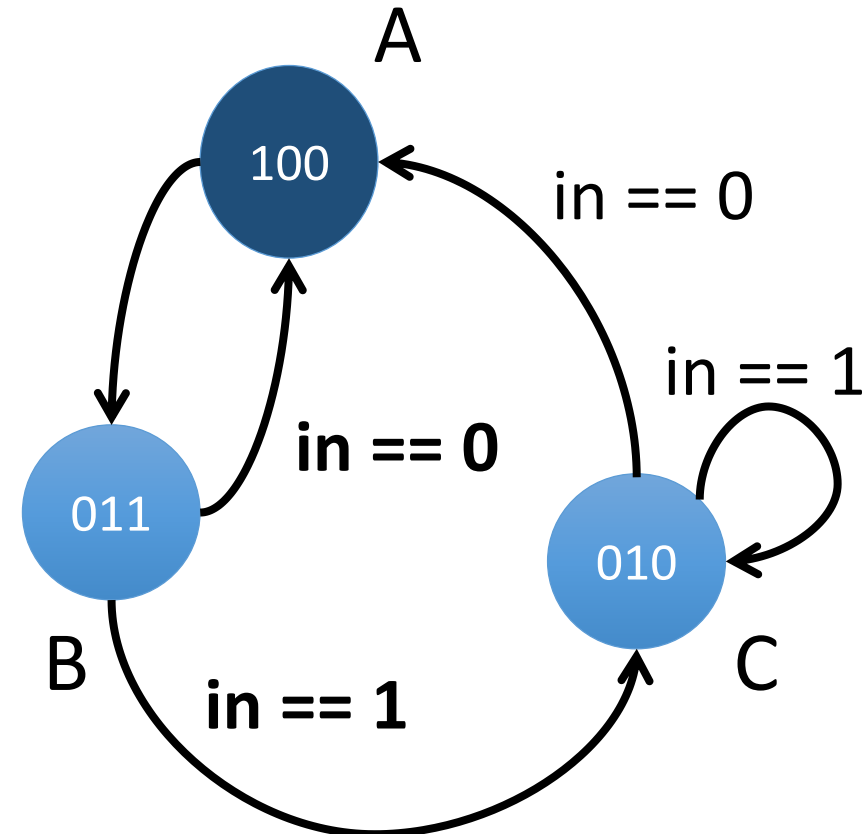

For an example of this FSM see
fsm_moore_with_output_function

Binary state encoding: We define the outputs with binary values


state	o2	o1	o0
0 0	1	0	0
0 1	0	1	1
1 0	0	1	0

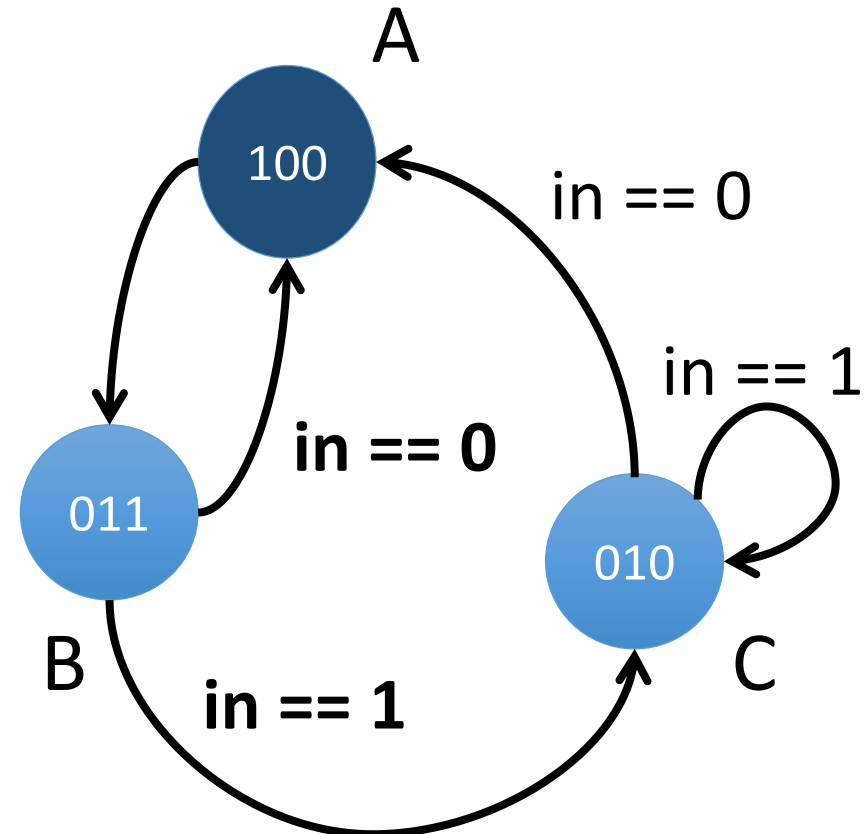

We define the outputs with binary values

$$o2 = \sim s1 \ \& \ \sim s0$$

s1	s0	o2	o1	o0
0	0	1	0	0
0	1	0	1	1
1	0	0	1	0

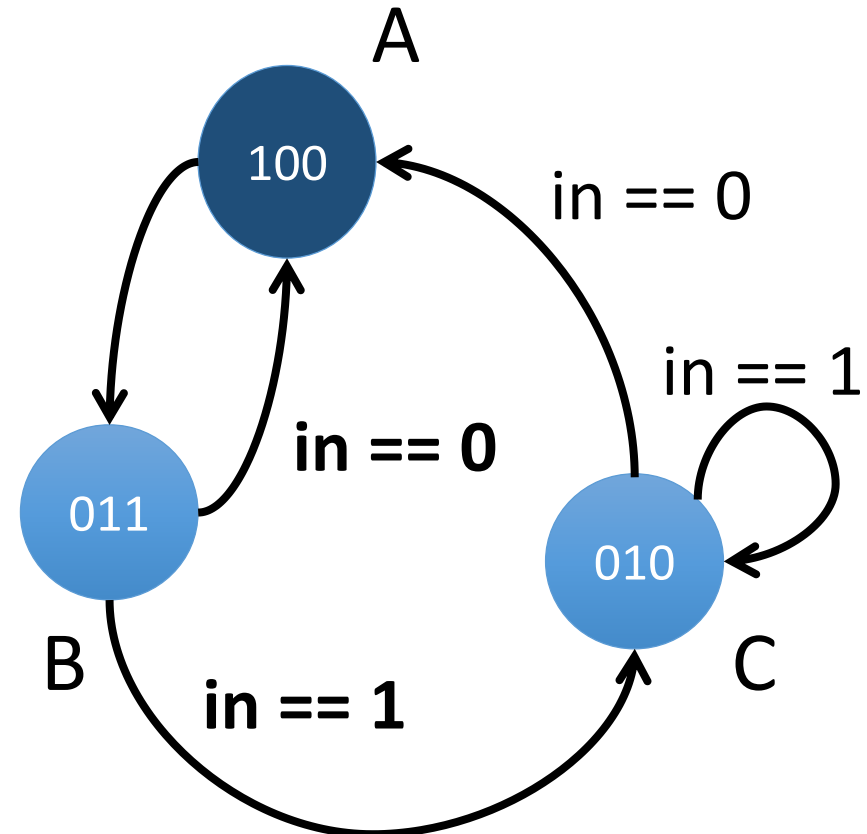


We define the outputs with binary values

$$o2 = \sim s1 \ \& \ \sim s0$$

$$o1 = (\sim s1 \ \& \ s0) \ | \ (s1 \ \& \ \sim s0)$$

s1	s0	o2	o1	o0
0	0	1	0	0
0	1	0	1	1
1	0	0	1	0

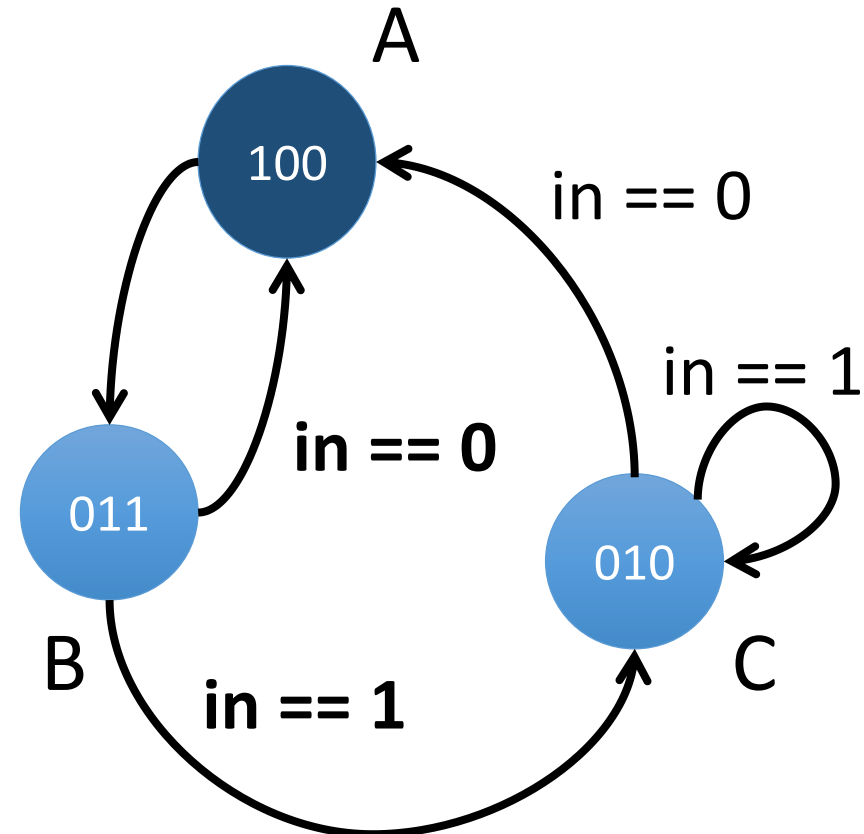


We define the outputs with binary values

$$o2 = \sim s1 \ \& \ \sim s0$$


$$o1 = (\sim s1 \ \& \ s0) \ | \ (s1 \ \& \ \sim s0)$$

$$o0 = \sim s1 \ \& \ s0$$


s1	s0	o2	o1	o0
0	0	1	0	0
0	1	0	1	1
1	0	0	1	0

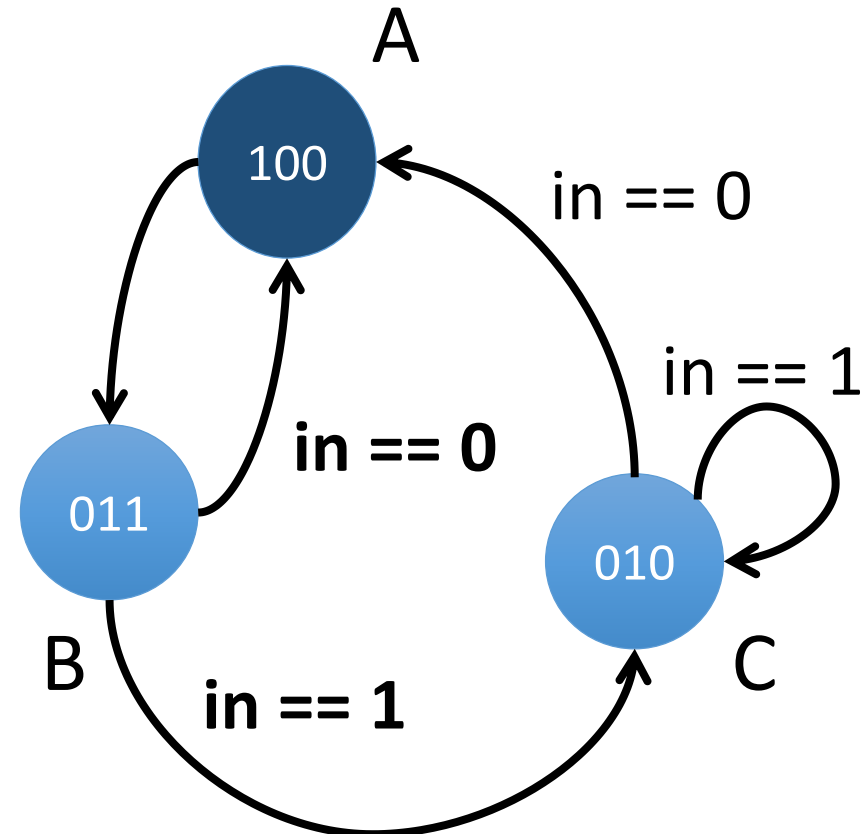

Structural diagram of the FSM

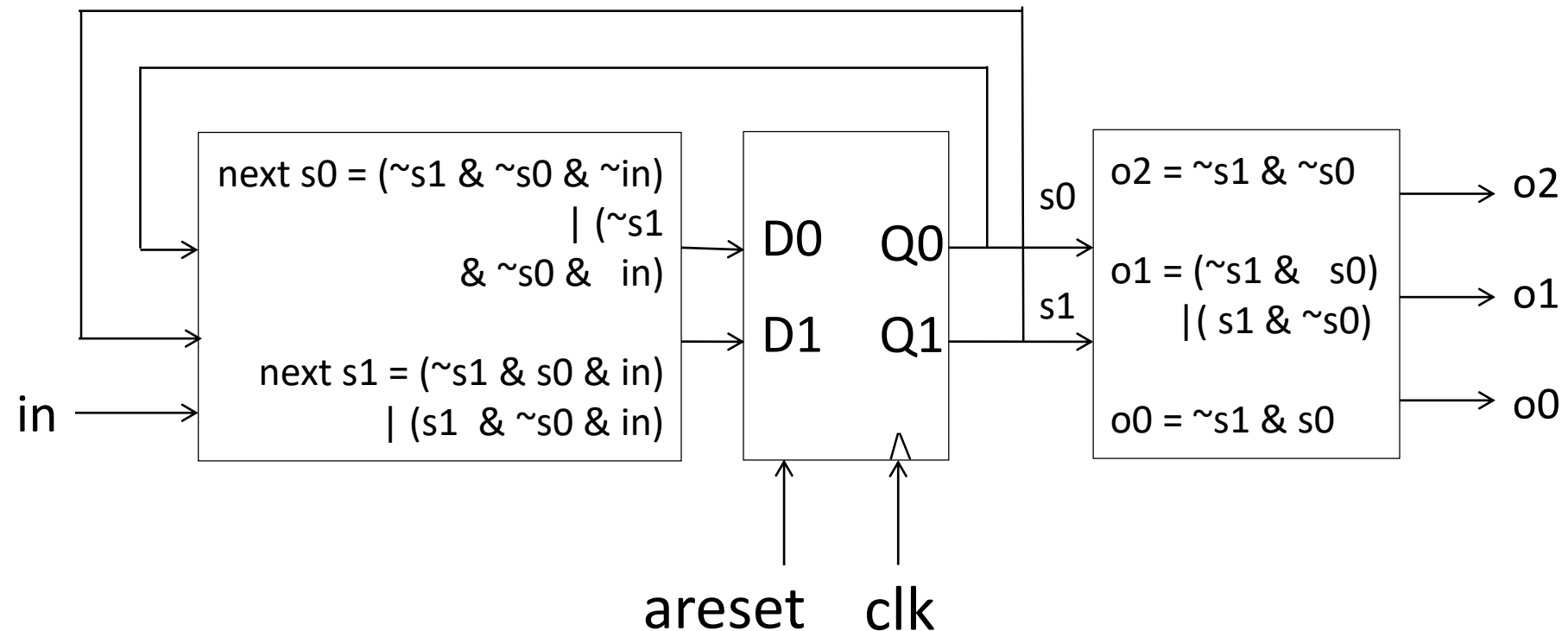


Implementation with Digital

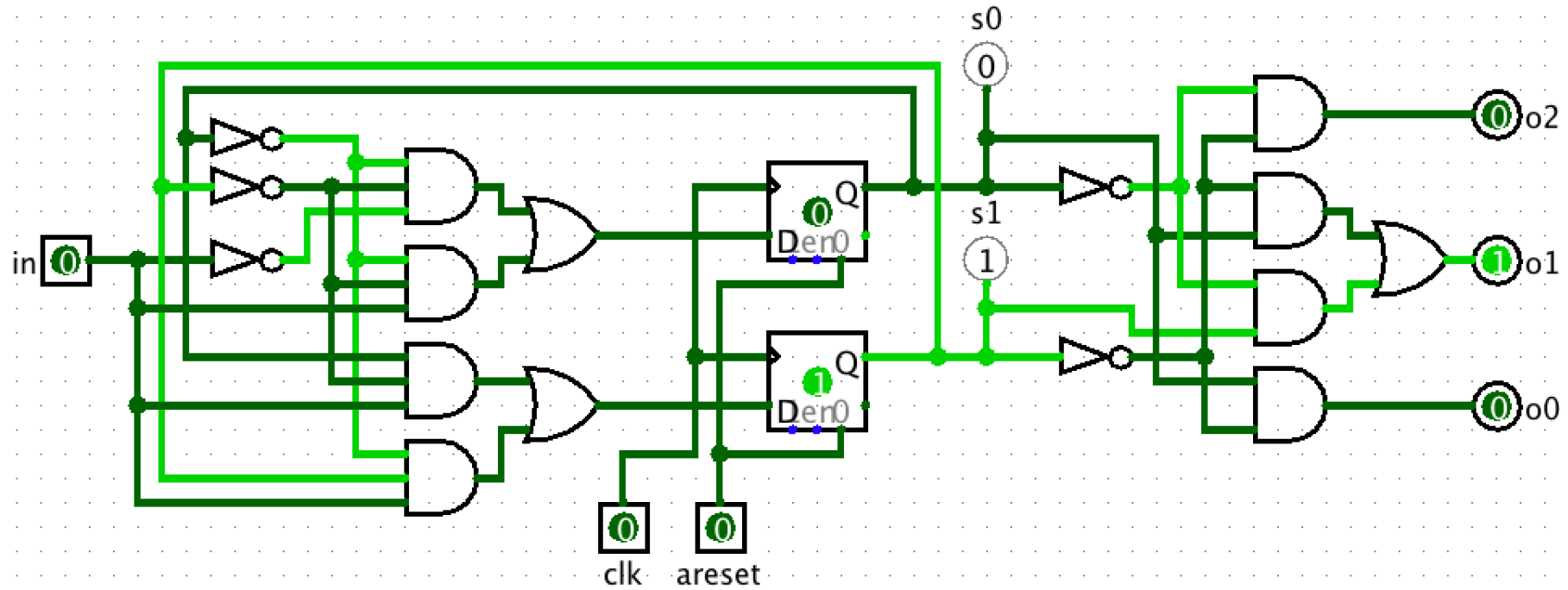


Essence of Moore Machines

the state is
stored
in a register

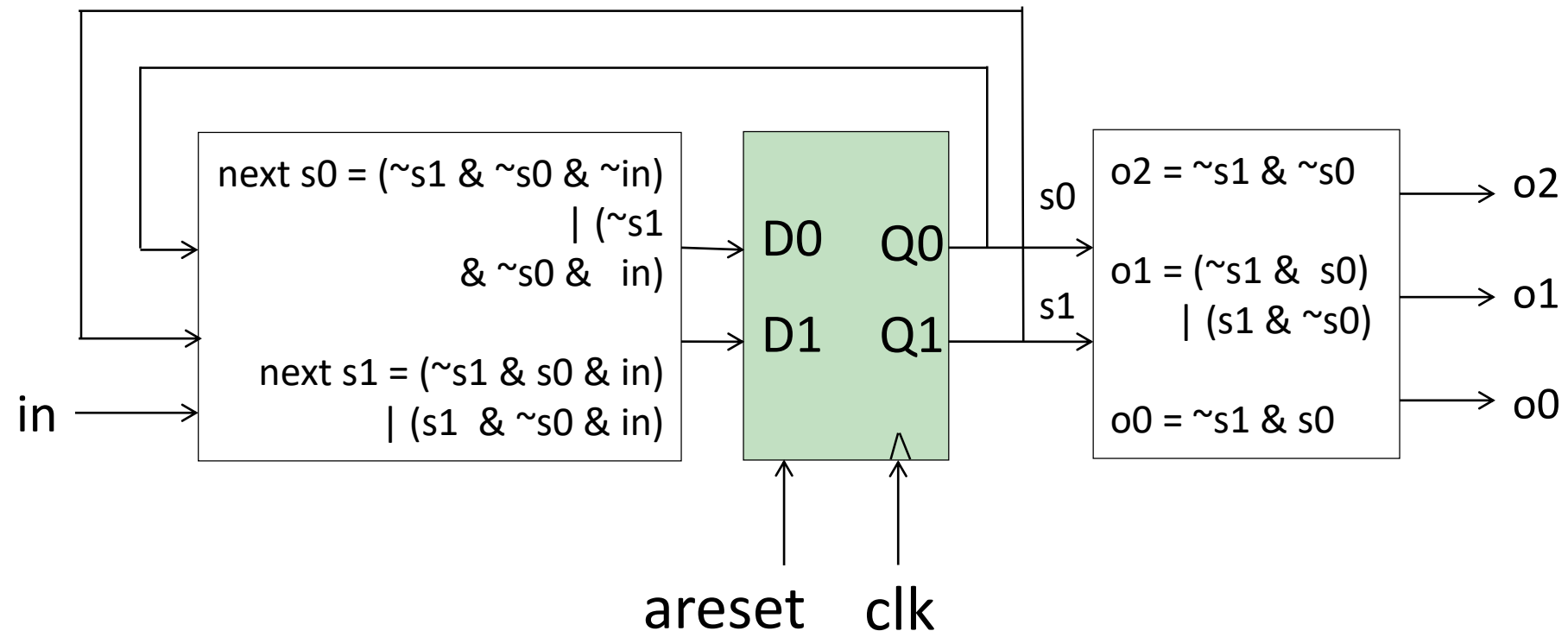

Essence of Moore Machines


**the state is
stored
in a register**

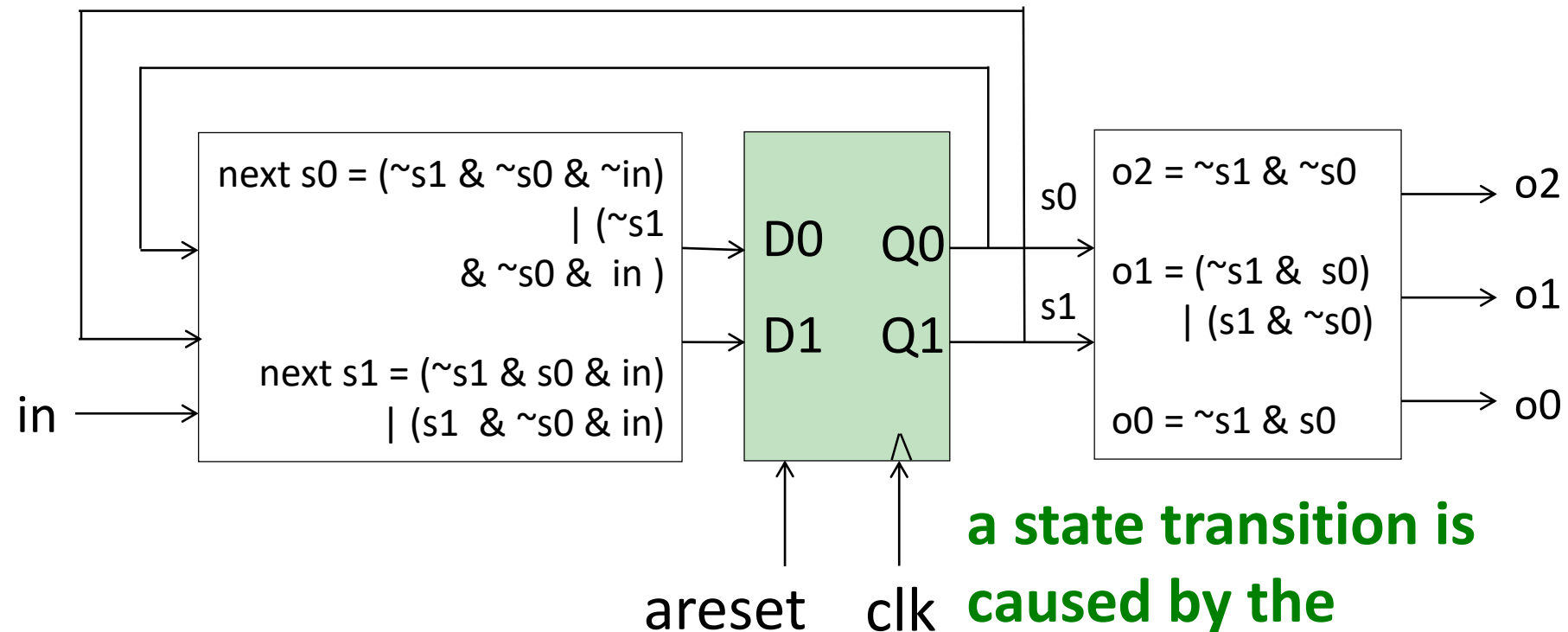

**a state transition is
caused by the
clock signal.**

Essence of Moore Machines

**the state is
stored
in a register**

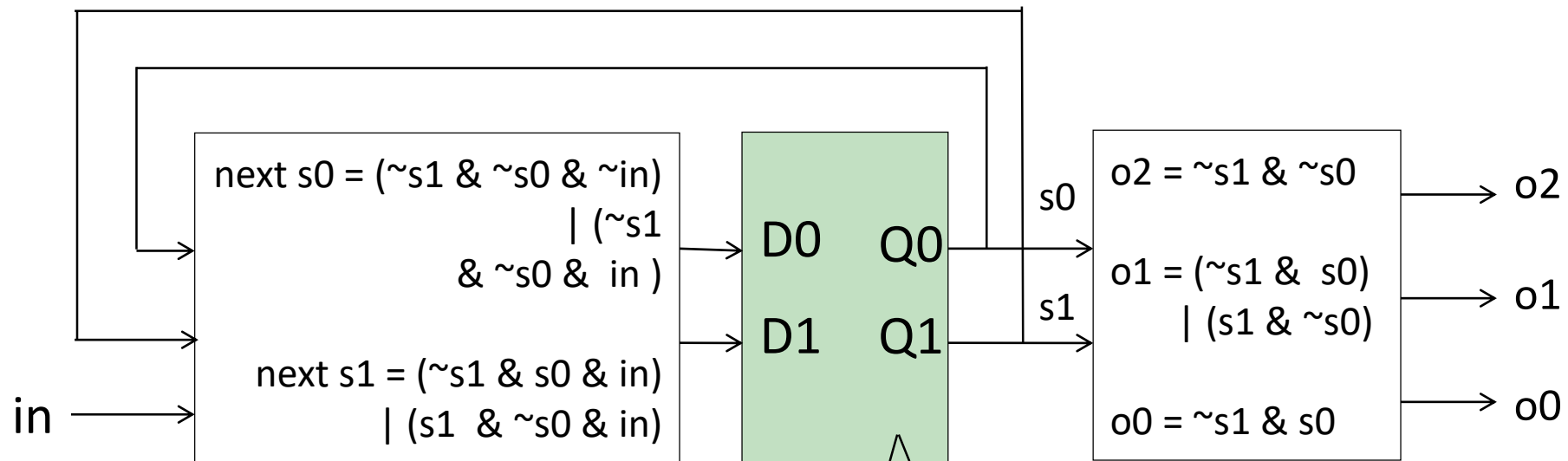

**With “areset” we can
initialize the ASM
 (“initial state”).**


areset

clk

**a state transition is
caused by the
clock signal.**

Essence of Moore Machines

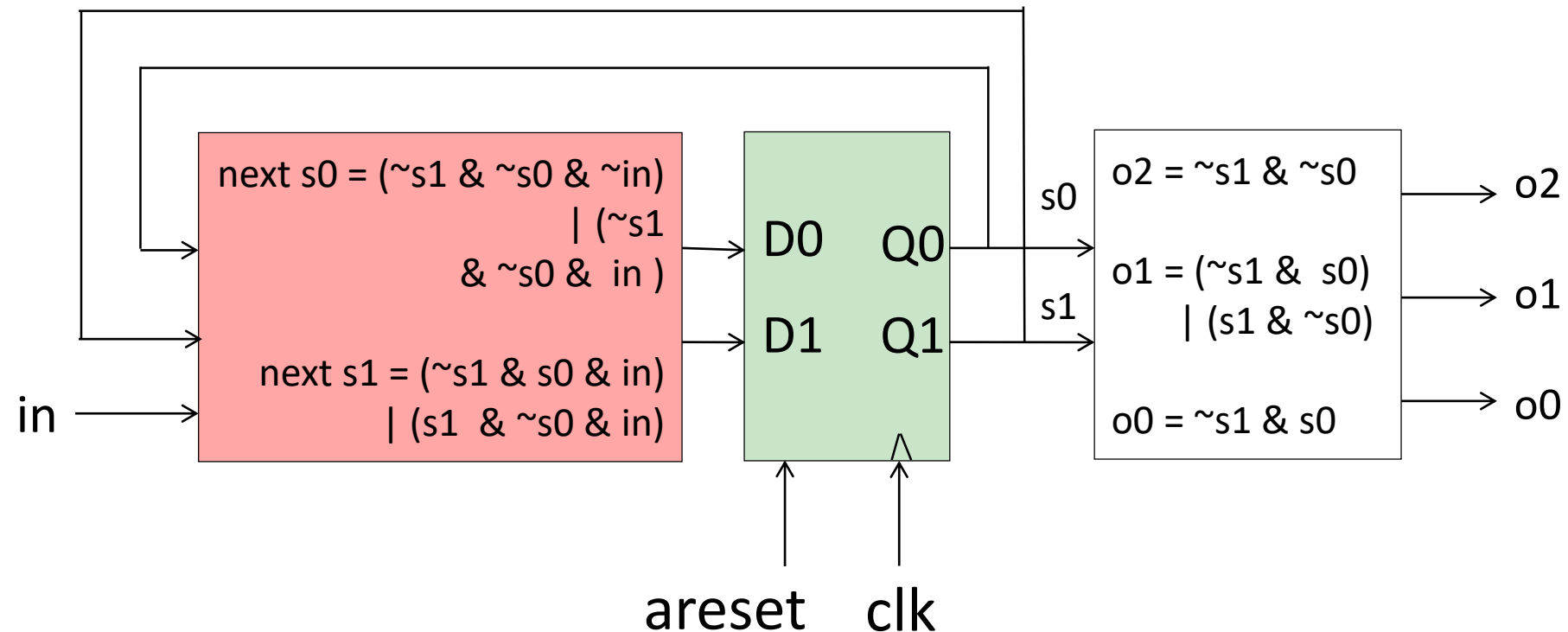
**With the next-state function f
we compute the next state:
next state = $f(\text{state}, \text{input})$**




Essence of Moore Machines

With the output function we compute the output values:

output = g(state)

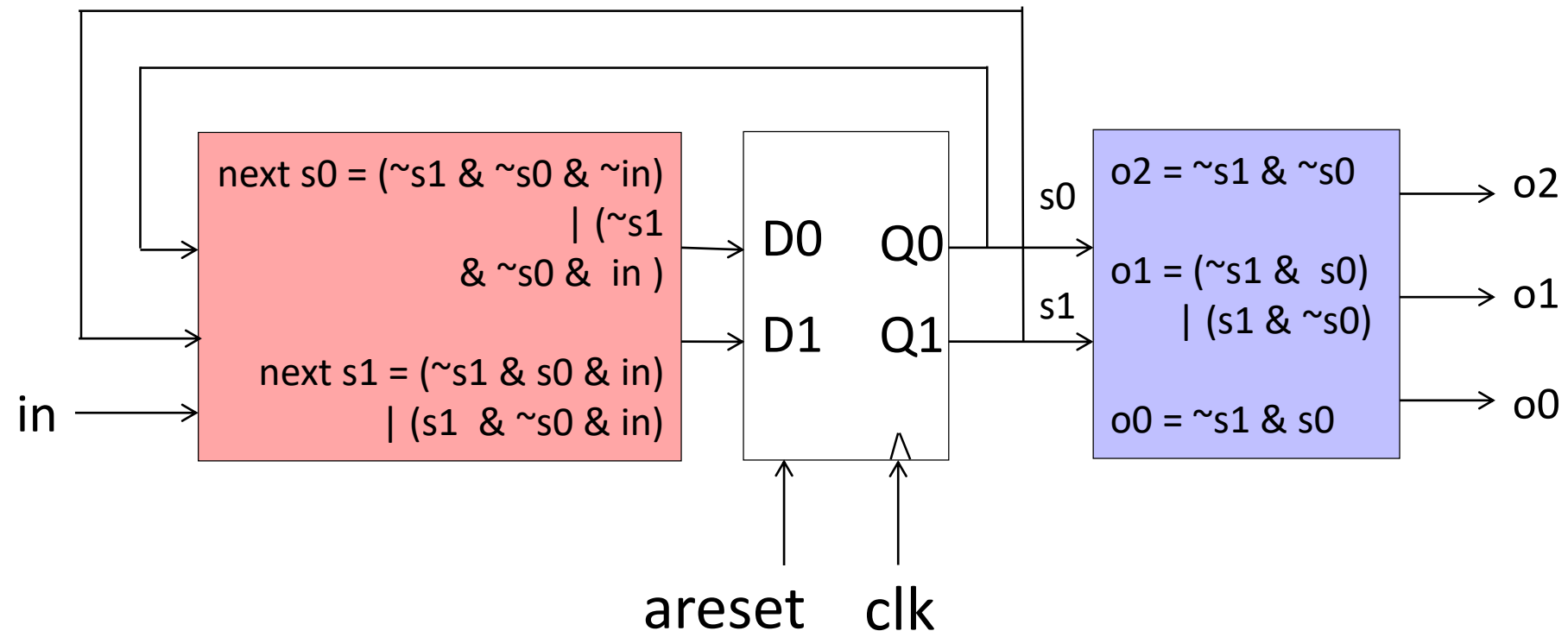


Essence of Moore Machines

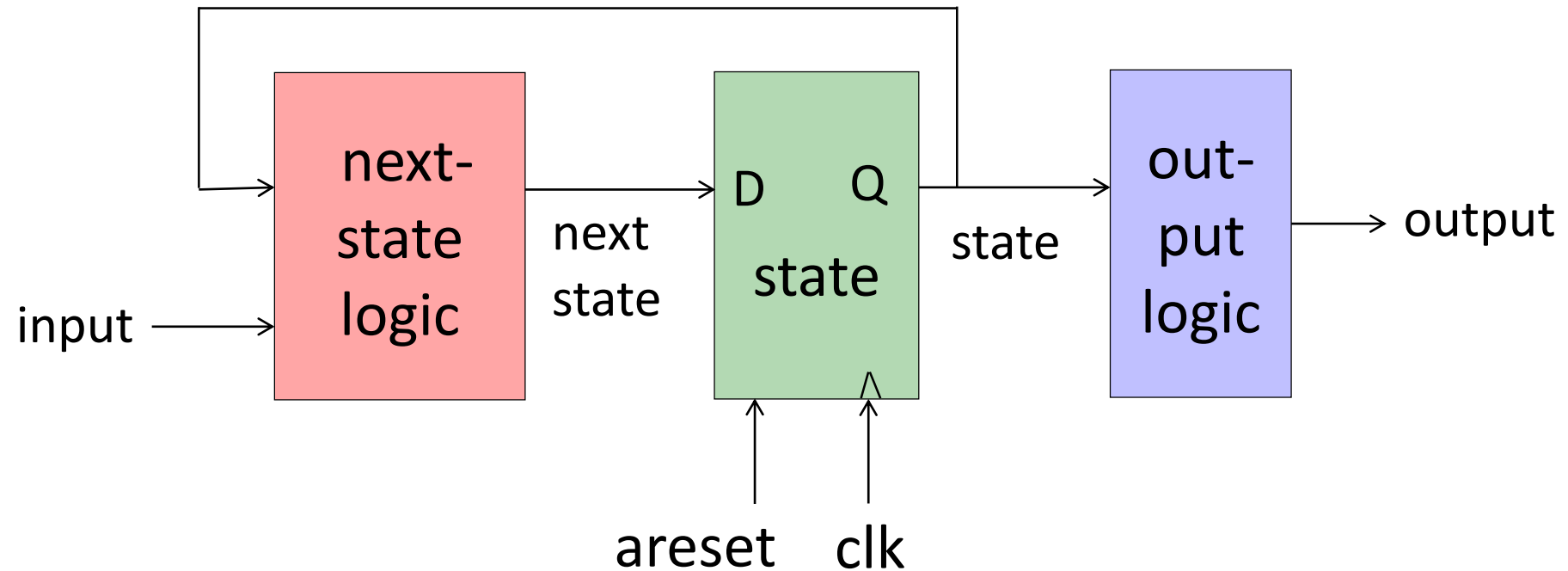

There exist 2 types of machines:
check out the
LITTLE but IMPORTANT difference


- **Moore Machines**
 - next state = function of present state and input
 - output = function of present state
- **Mealy Machines**
 - next state = function of present state and input
 - output = function of present state **and input**

Essence of **Moore** Machines

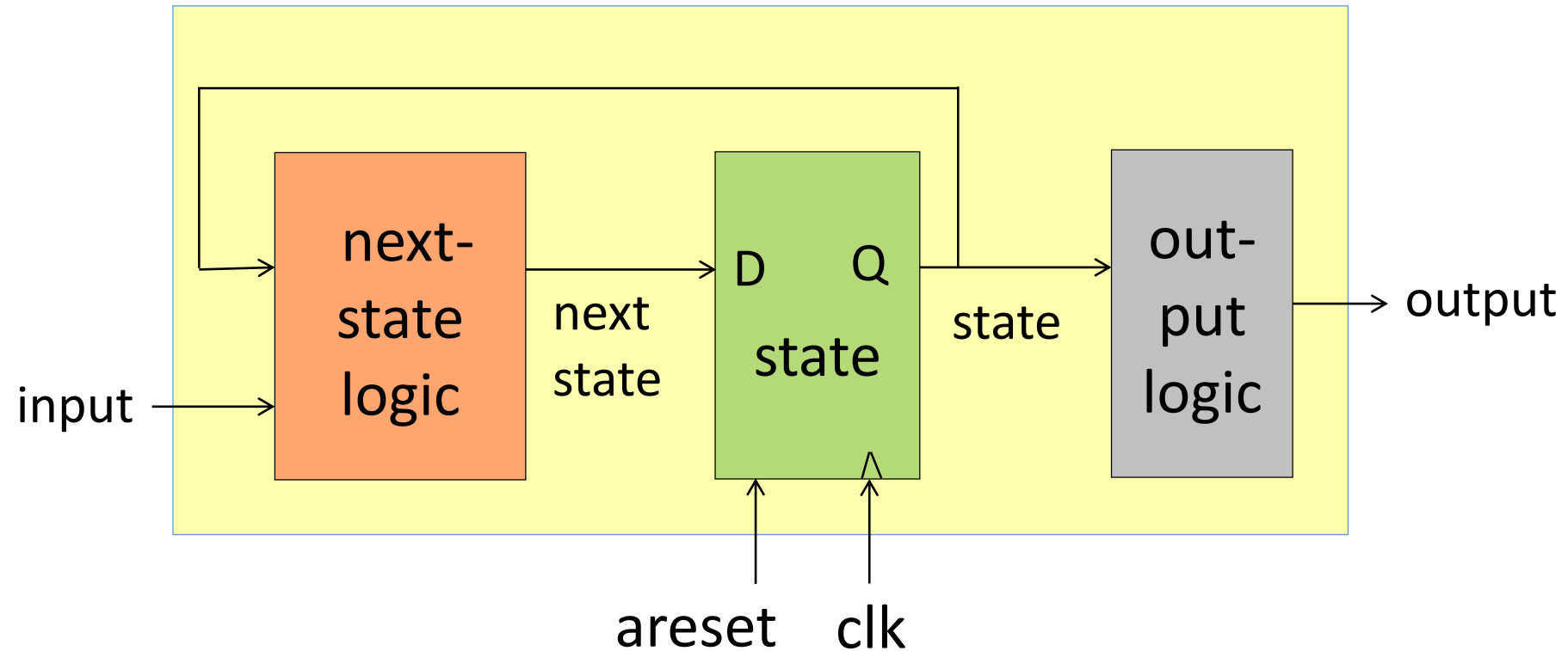


Essence of **Mealy** Machines
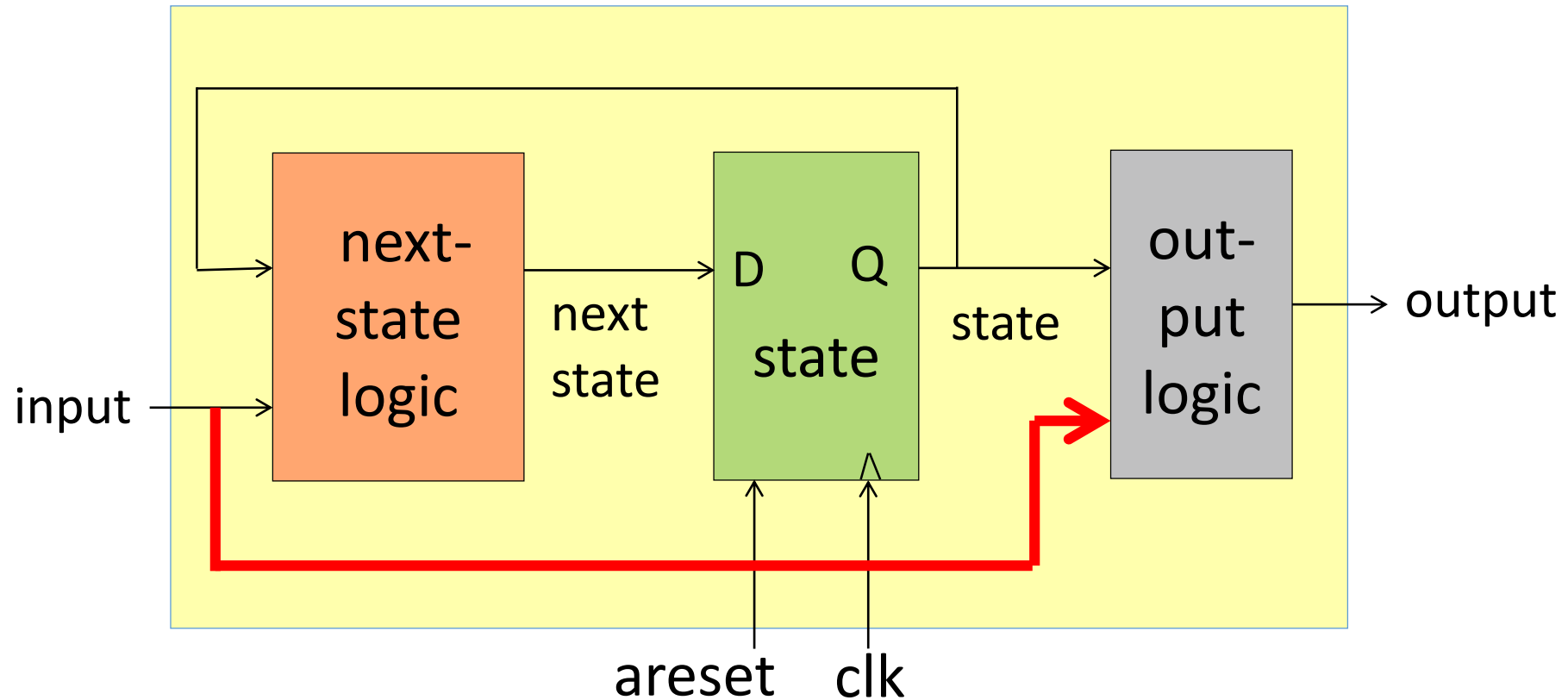
$$\text{output} = g(\text{state}, \text{input})$$




An example for a Mealy Machine

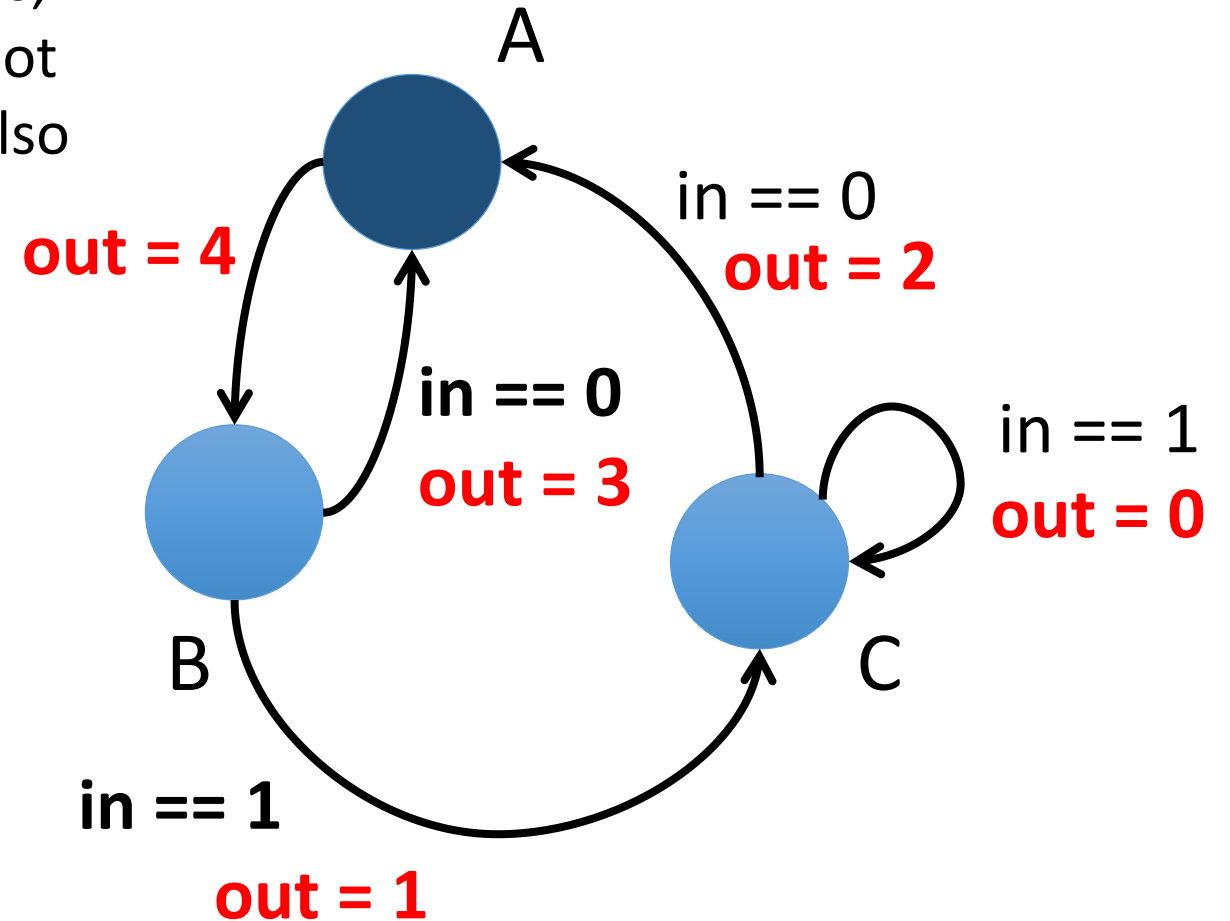We write the **output values** next to the transition arrows, since the output depends not only on the state, but can also depend on the input.



The state transitions are the same as in the previous example with the Moore Machine

present state	in	next state
A	0	B
A	1	B
B	0	A
B	1	C
C	0	A
C	1	C

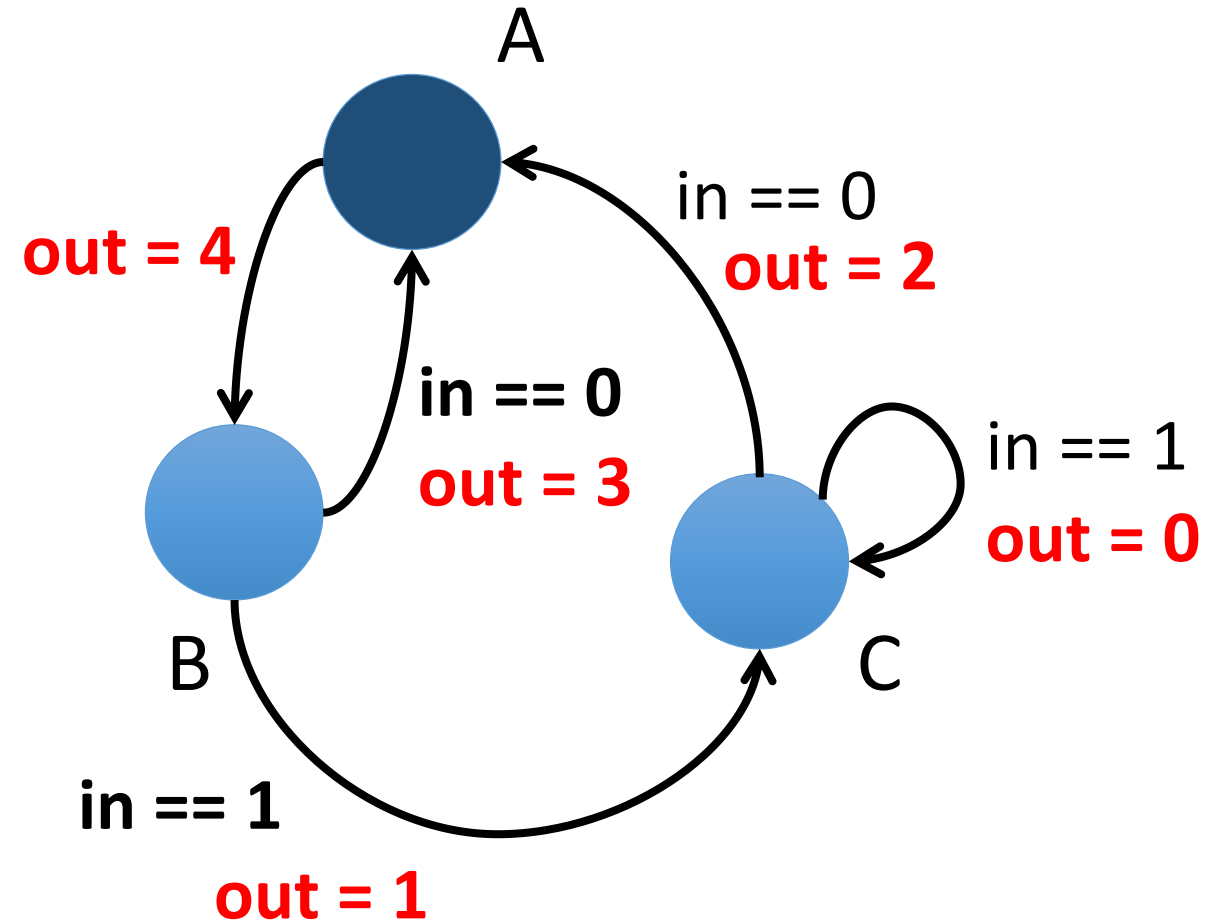


The output function


The output function can be derived from the state diagram.

output = g(state, input)

state	in	output
A	0	4
A	1	4
B	0	3
B	1	1
C	0	2
C	1	0

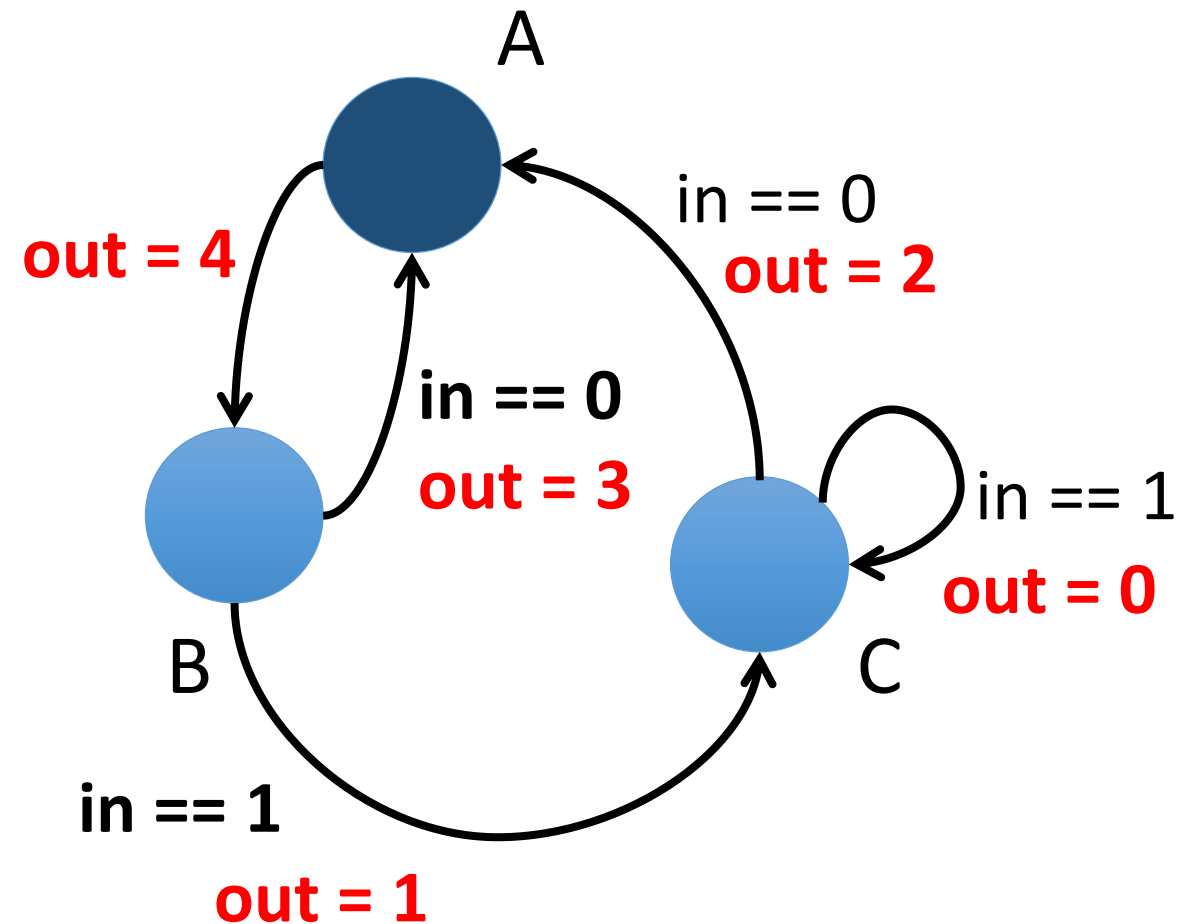

Timing diagram

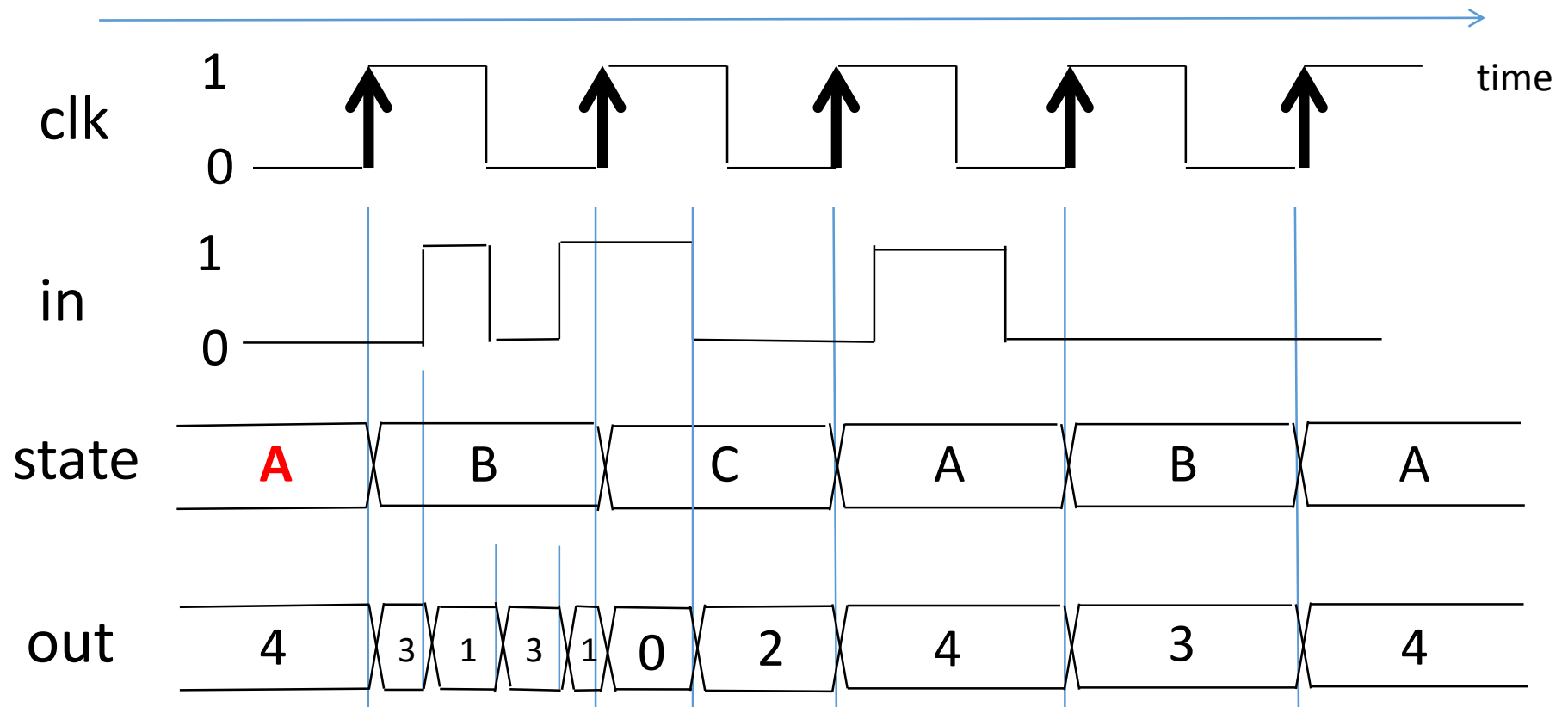


For a timing diagram, we need to choose values for the input signal “in”. Only after some choice for “in” we can derive the sequence of states from the state diagram. We see here also, how the value of “in” immediately influences the value of “out”.

Binary encoding: Re-writing the output table with binary values.

And completing the table with the unused bit combinations.

s1	s0	in	o2	o1	o0
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	x	x	x
1	1	1	x	x	x

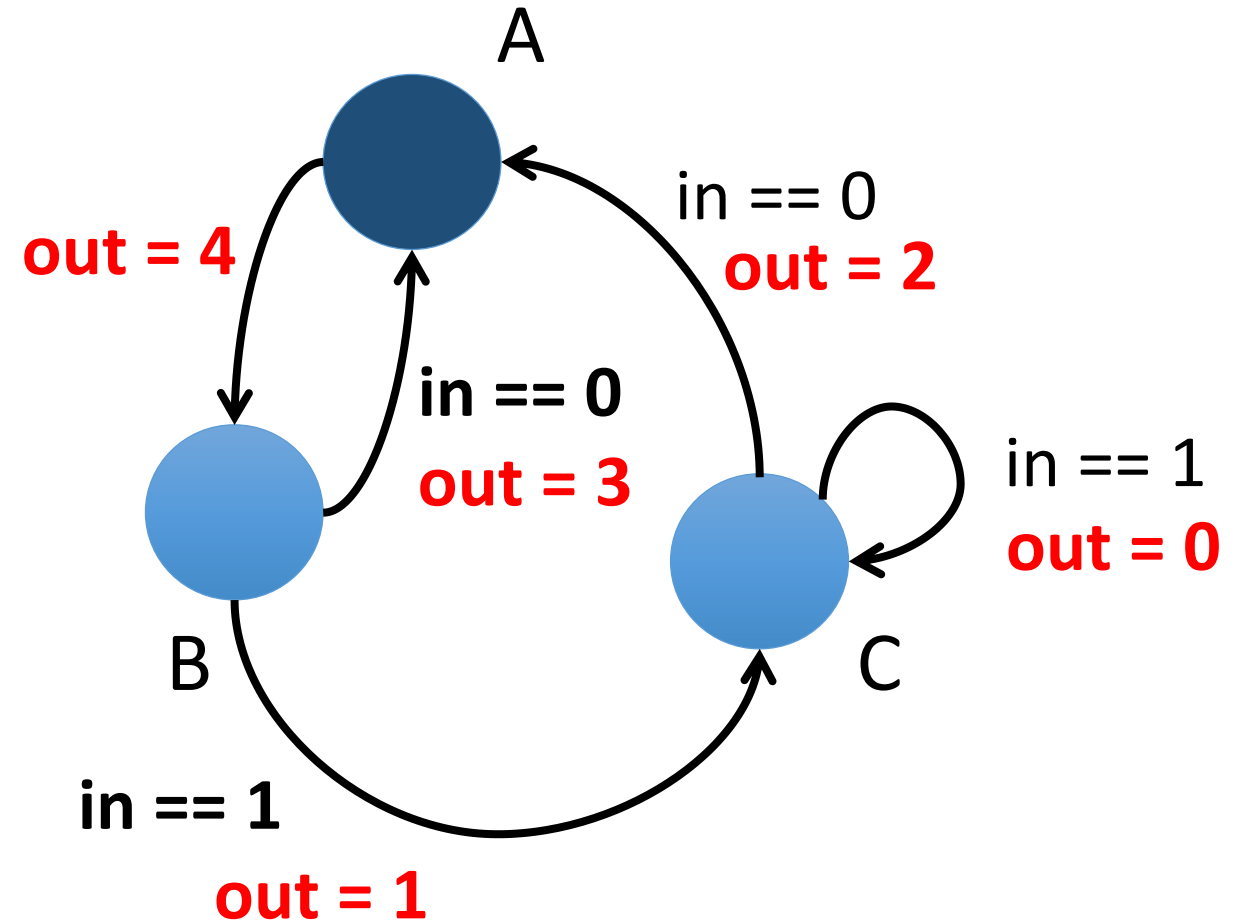

We can derive the logic functions for o2, o1, and o0

s1	s0	in	o2	o1	o0
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	x	x	x
1	1	1	x	x	x

$$o2 = \sim s1 \ \& \ \sim s0$$

We can derive the logic functions for o2, o1, and o0

s1	s0	in	o2	o1	o0
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	x	x	x
1	1	1	x	x	x

$$o2 = \sim s1 \ \& \ \sim s0$$

$$o1 = (\sim s1 \ \& \ s0 \ \& \ \sim in) \\ | (s1 \ \& \ \sim s0 \ \& \ \sim in)$$

We can derive the logic functions for o2, o1, and o0


s1	s0	in	o2	o1	o0
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	x	x	x
1	1	1	x	x	x

$$o2 = \sim s1 \ \& \ \sim s0$$


$$o1 = (\sim s1 \ \& \ s0 \ \& \ \sim in) \\ \vee (s1 \ \& \ \sim s0 \ \& \ \sim in)$$

$$o0 = \sim s1 \ \& \ s0$$

The result

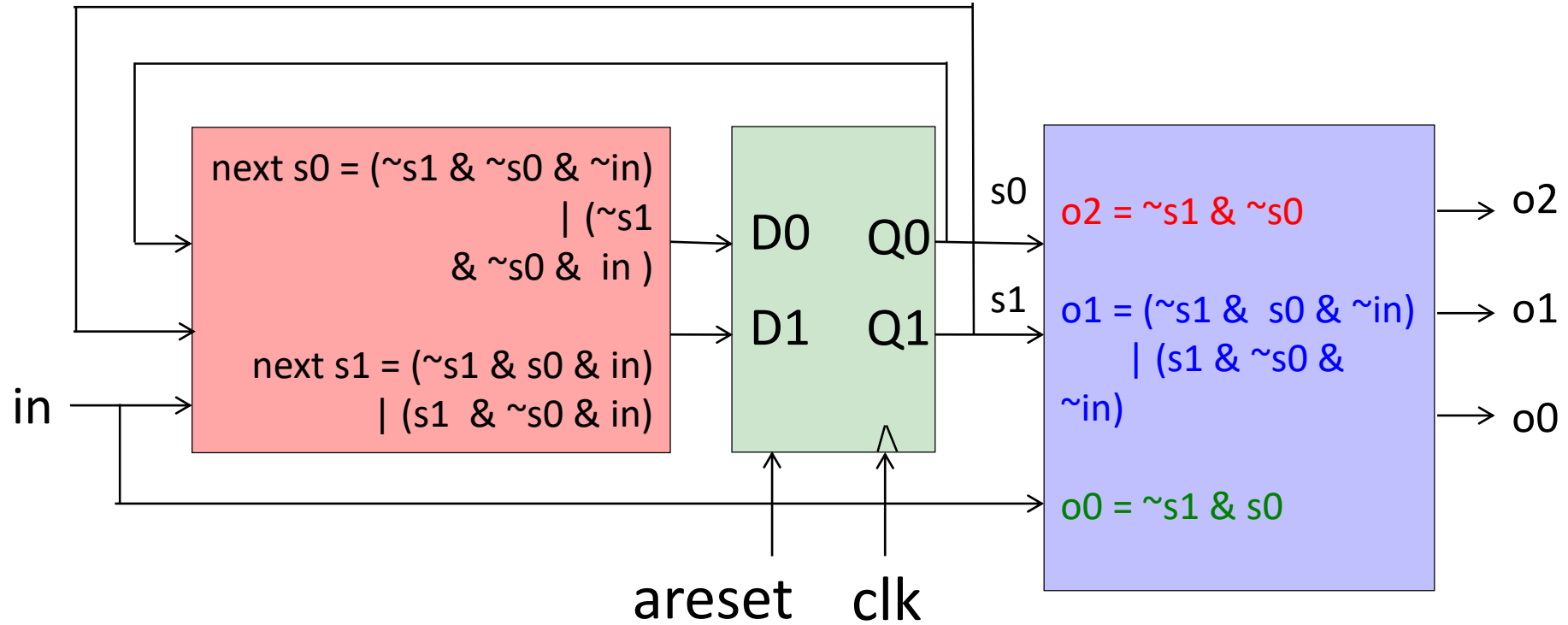

Modeling with Digital

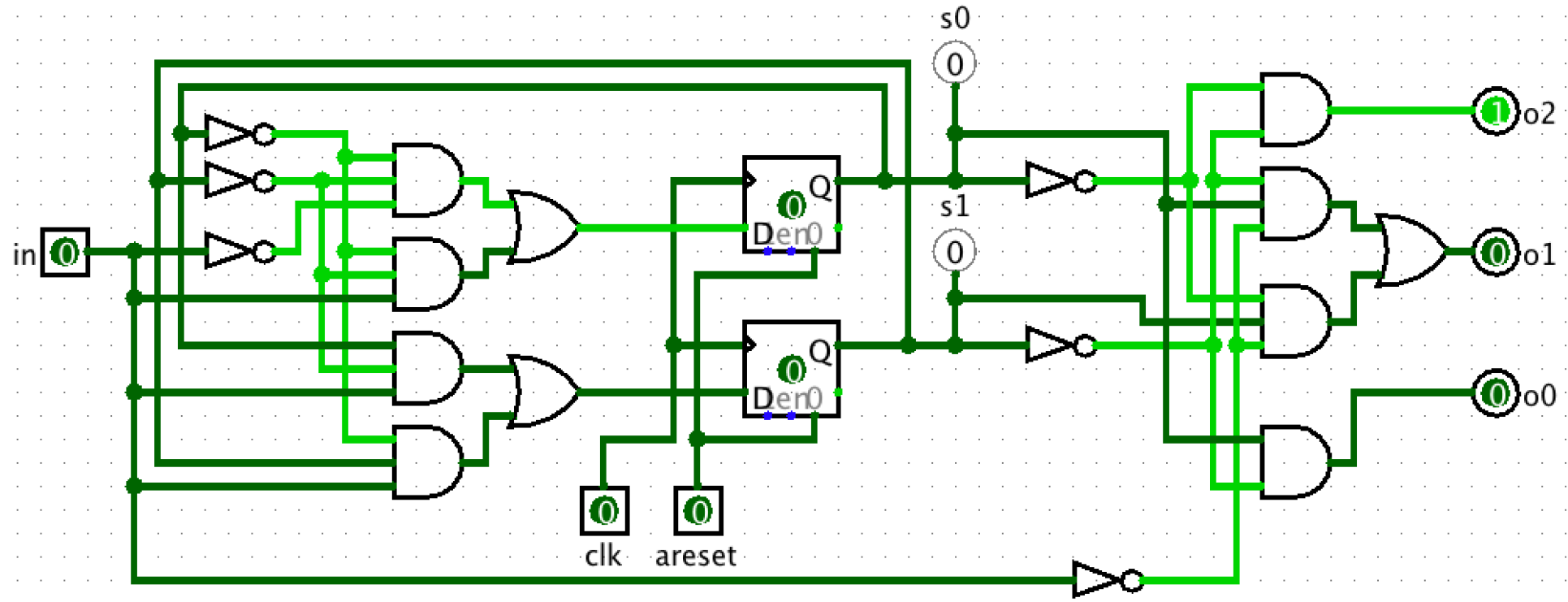


For a SystemVerilog example of this FSM see

con03_mealy_fsm


We can combine machines

- Combining Moore Machines causes no problem. We get another Moore Machine.
- Combining a Moore Machine with a Mealy Machine causes also no problem. We get a Moore Machine or a Mealy Machine.
- Combining two Mealy Machines can cause troubles: **One needs to avoid combinational loops!**

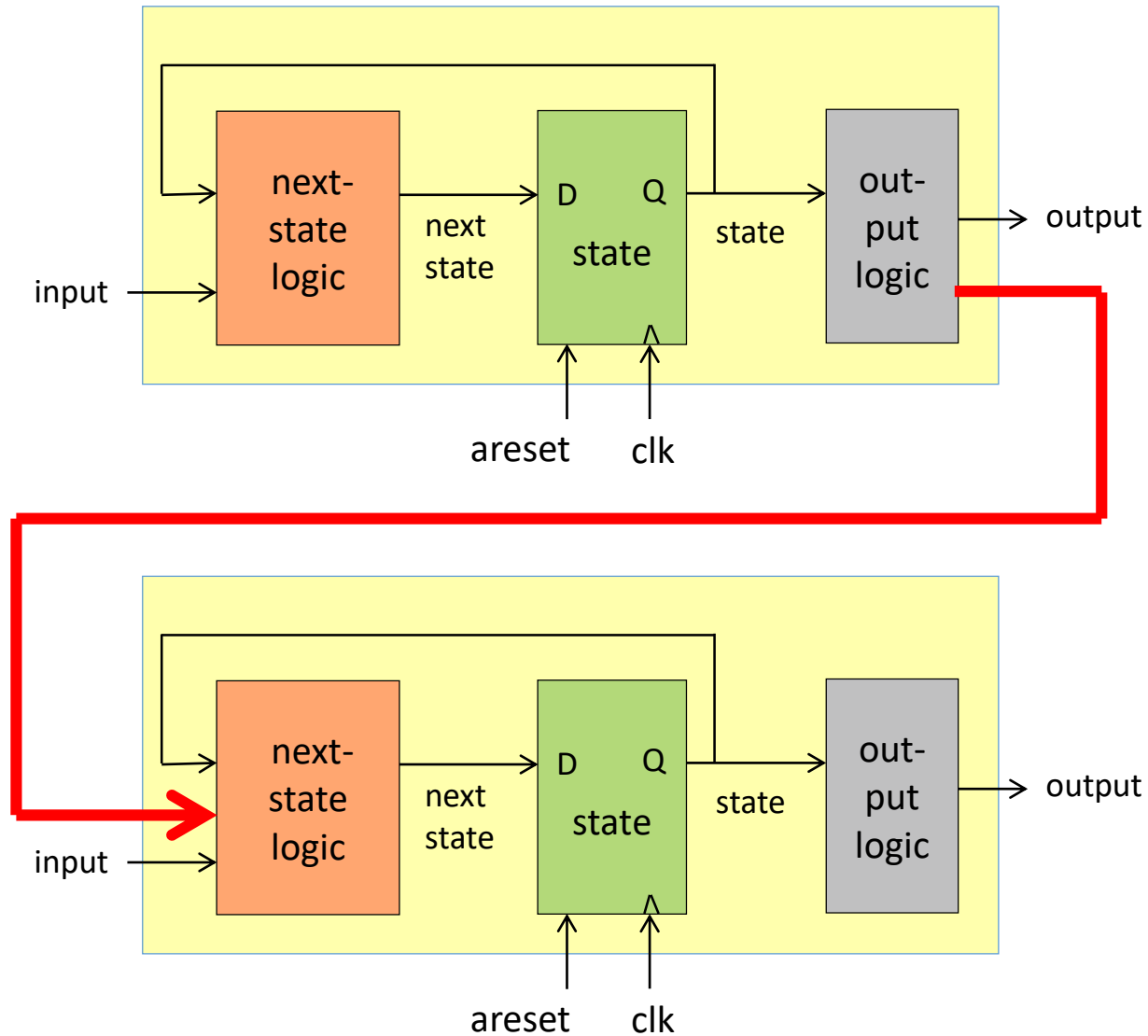
The combination of two Moore Machines creates again a (more complex) Moore Machine



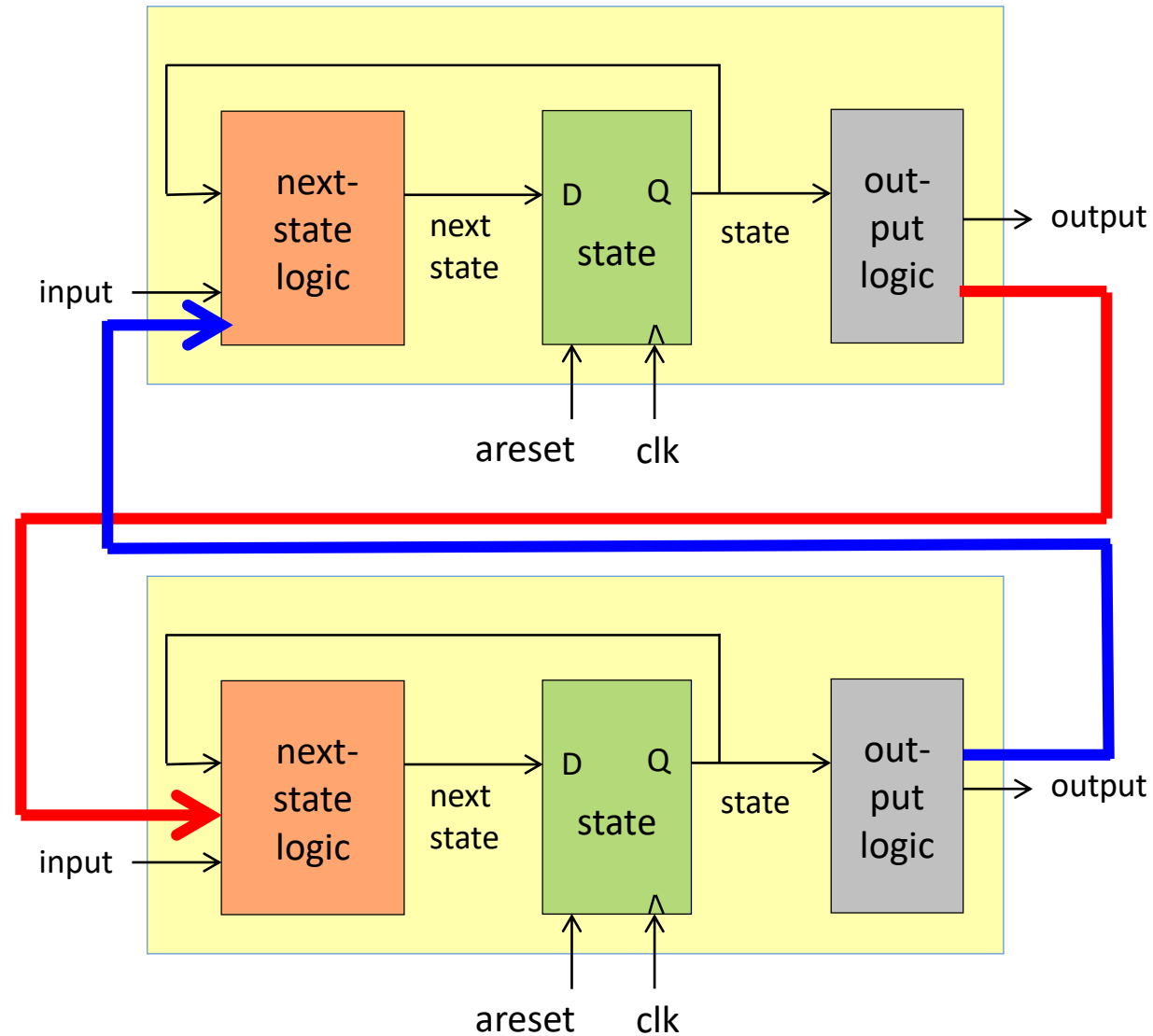
We can even connect More Machines in a loop-like fashion



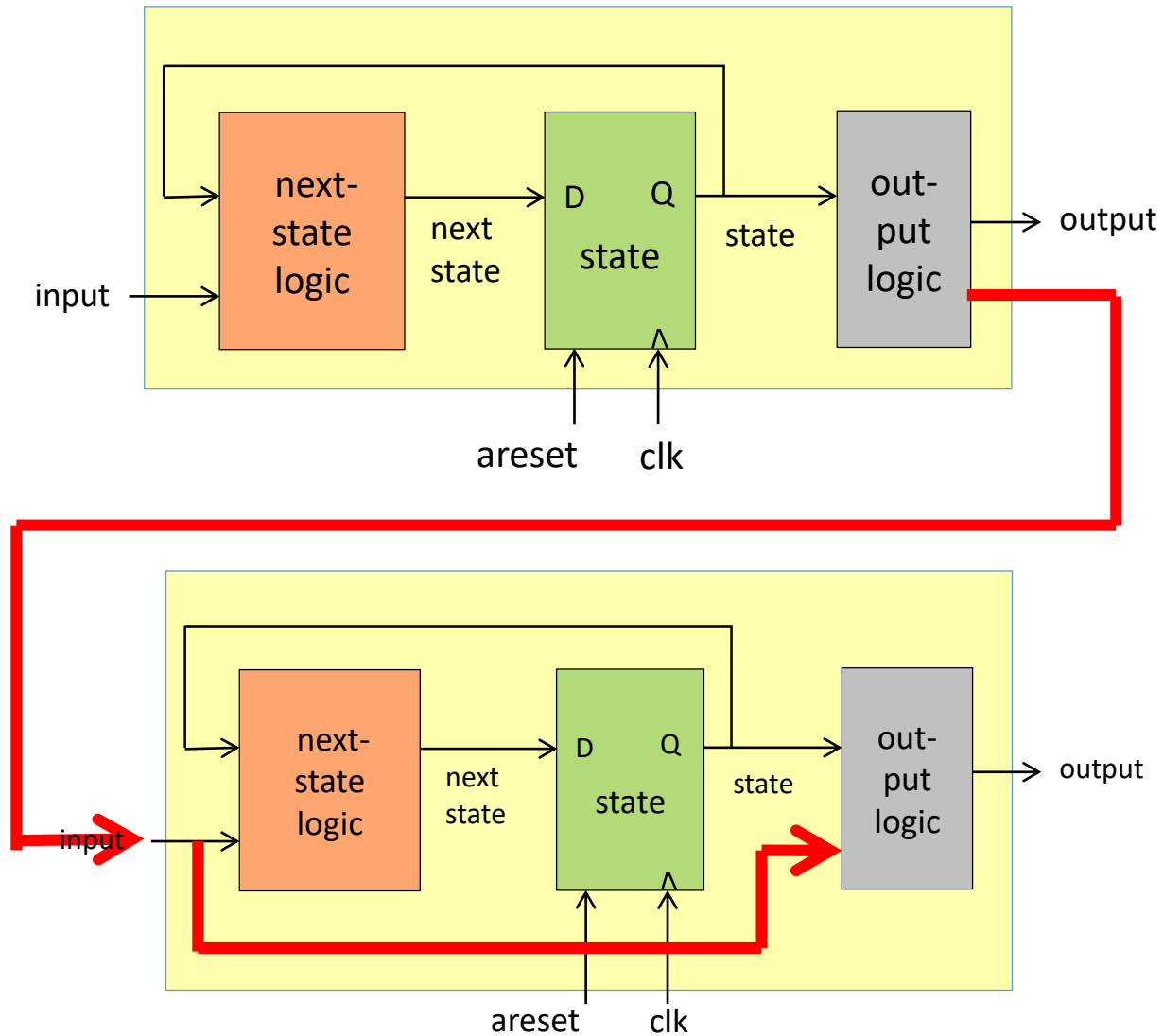
The combination of a Moore Machine with a Mealy Machine creates a Moore Machine or a Mealy Machine



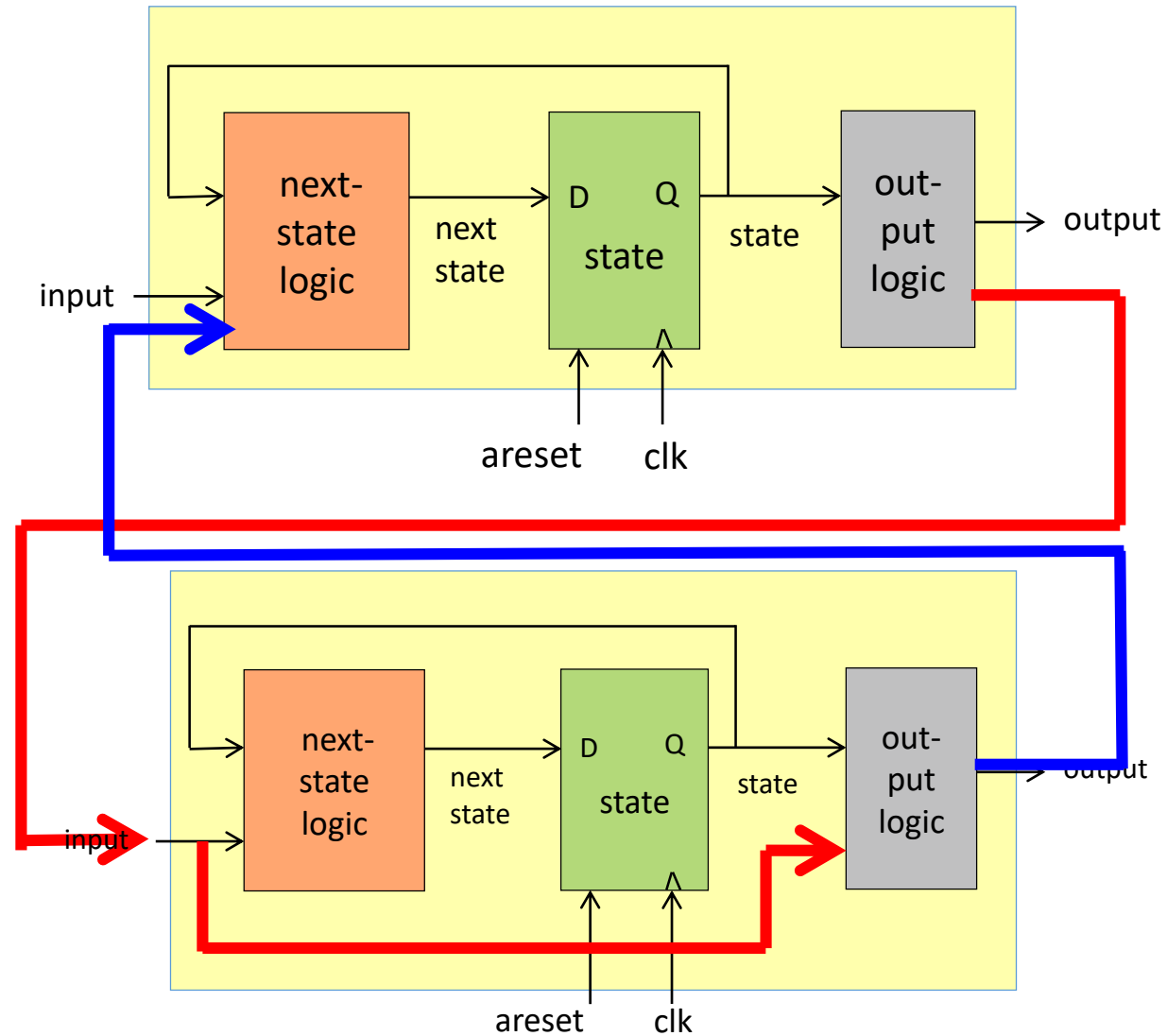
The combination of a Moore Machine with a Mealy Machine creates a Moore Machine or a Mealy Machine



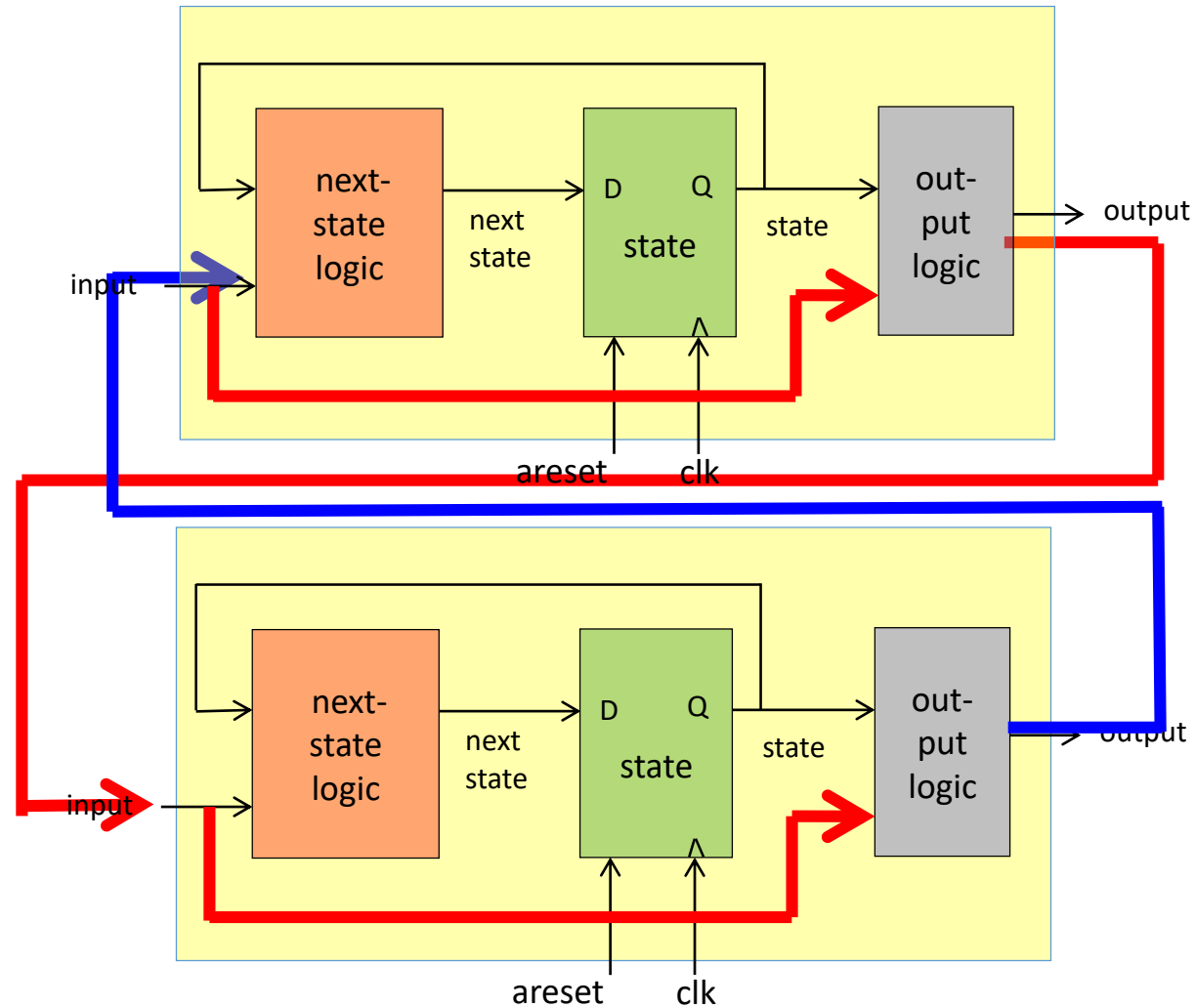The combination of **two Mealy Machines** is “dangerous”:
You need to avoid “combinational loops”



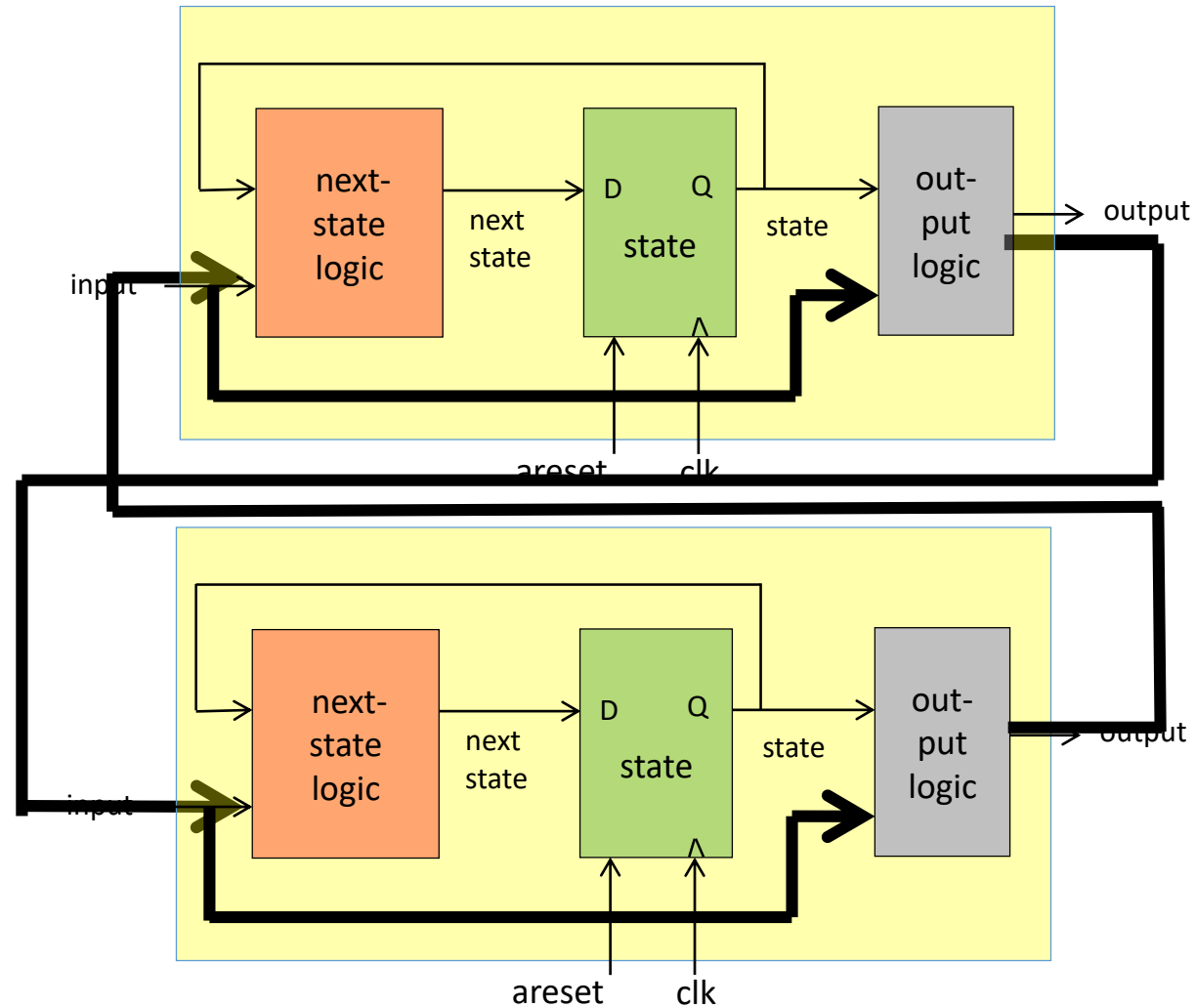The combination of two Mealy Machines is “dangerous”: You need to avoid “**combinational loops**”



Summary


- All digital logic can **in principle** be built with Moore Machines and Mealy Machines.
- You always start by defining the function with a state diagram.
- If you choose values for the input signal(s), then you can derive the timing diagram by using the state diagram.
- From a state diagram, you can always derive a circuit diagram.

Algorithmic State Machines




Algorithmic State Machines (ASMs)

- ASMs are a useful extension to finite state machines
- ASMs allow to specify a system consisting of a data path together with its control logic
- All FSM state diagrams have an equivalent ASM diagram


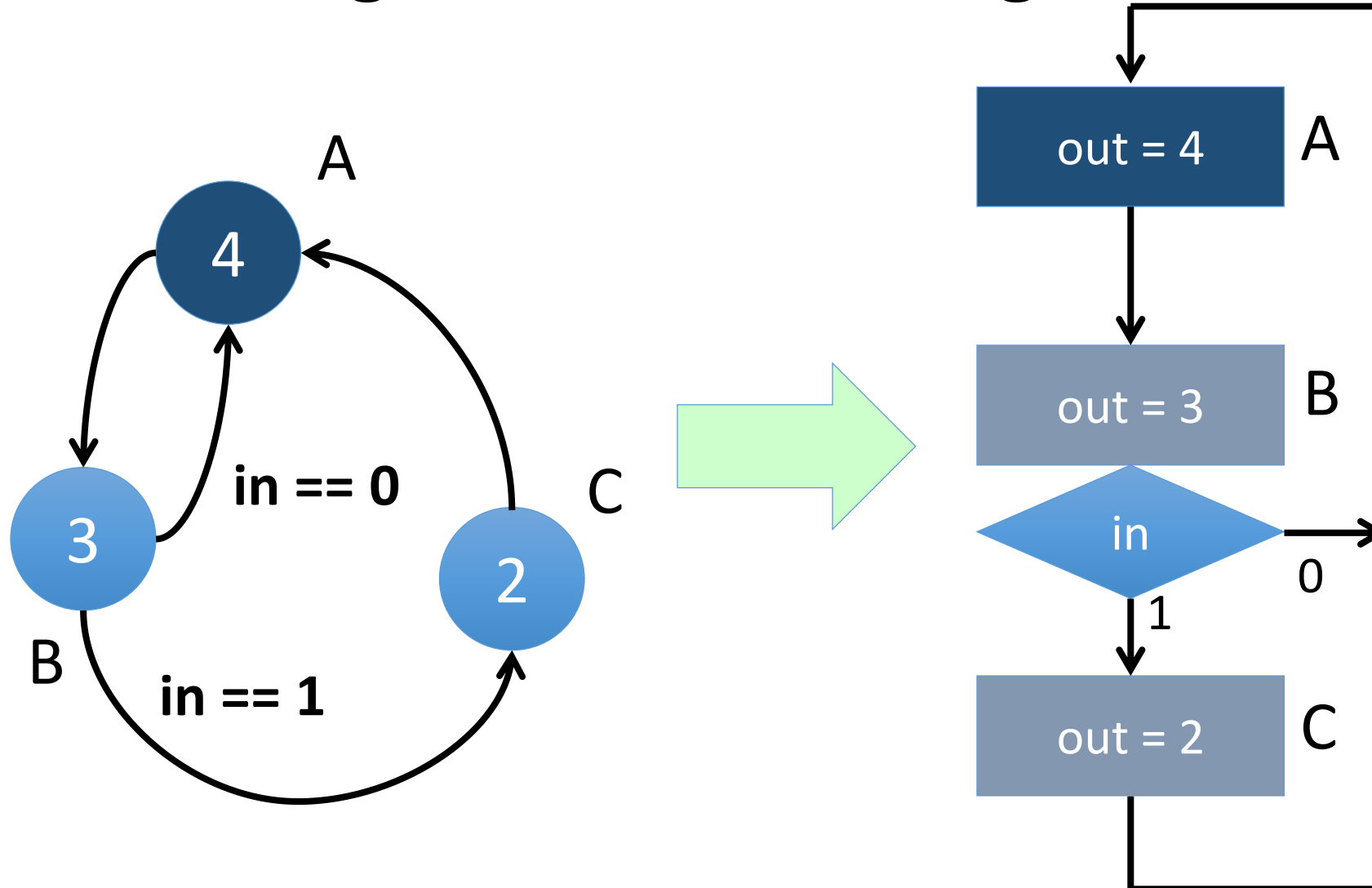
FSM state diagram \rightarrow ASM diagrams



Mealy Machines

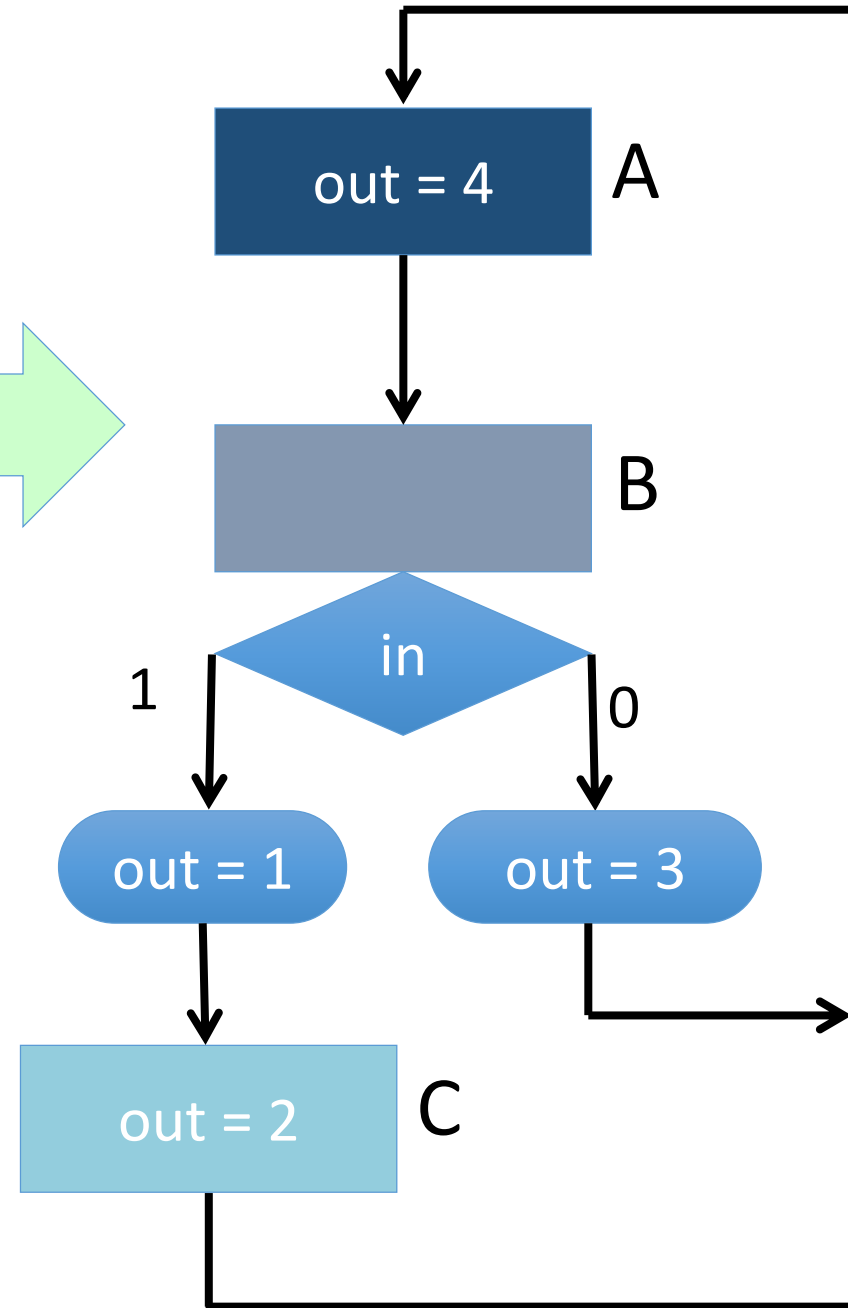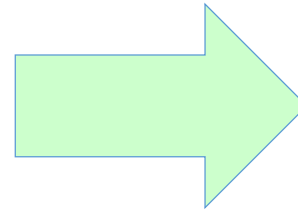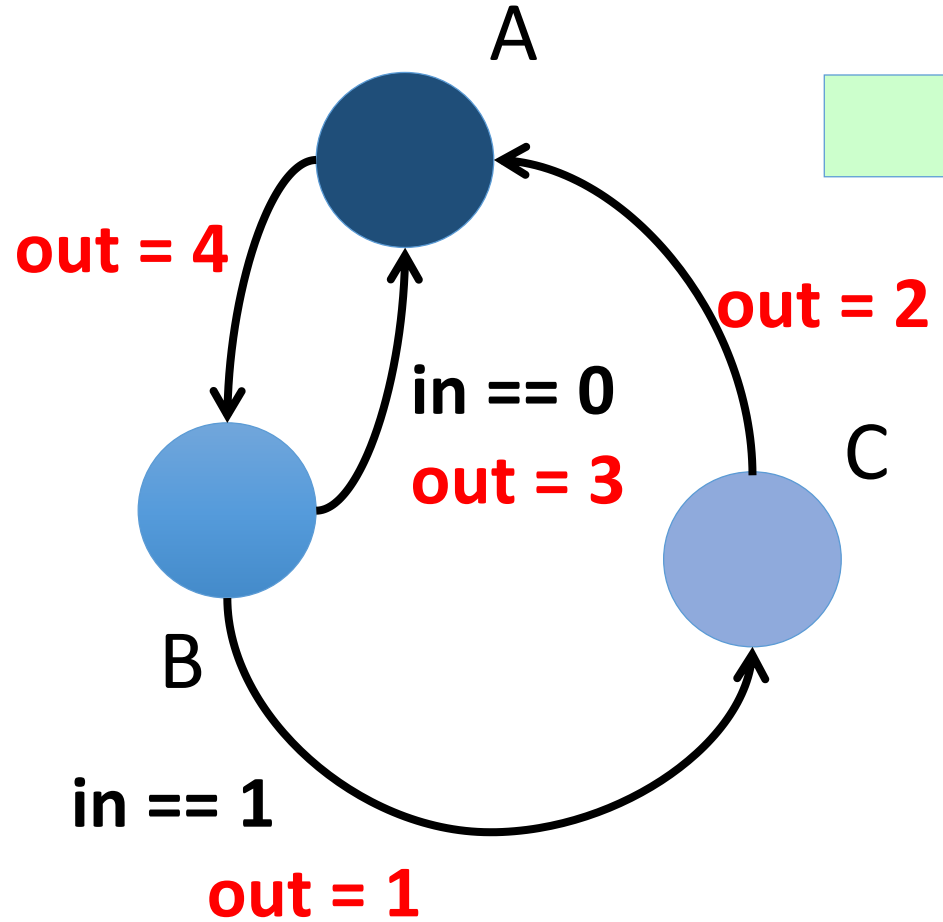


Mealy Machines

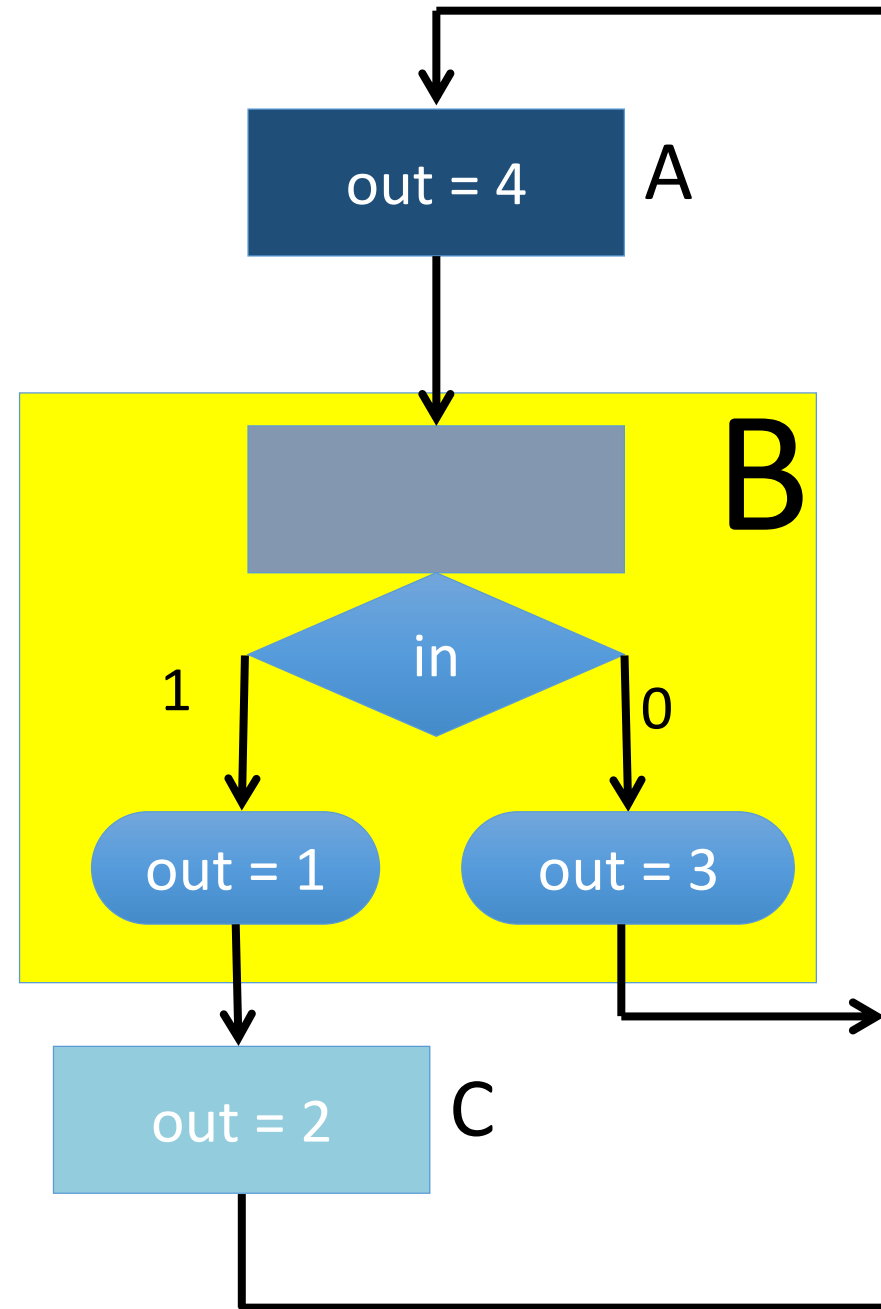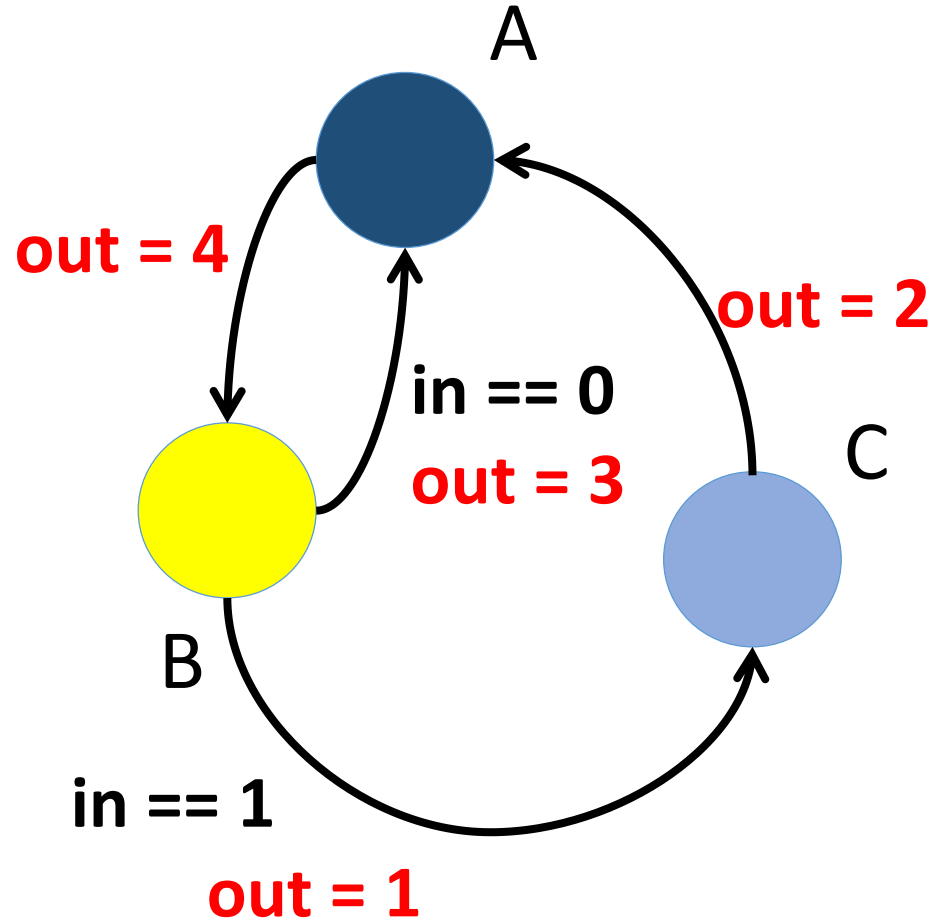


Register-Transfer Statements

- Register-transfer statements define the change of a value stored in a register.
- Values in registers can only change at the active (= rising) edge of clock.
- We denote “register-transfer statements” with a “left arrow” (“ \leftarrow ”)
- Example: “ $a \leftarrow x$ ” means that the value in the register “a” gets the value of “x” at the “next” active (= rising) edge of clock.
- We can specify register-transfer statement in an ASM diagram.

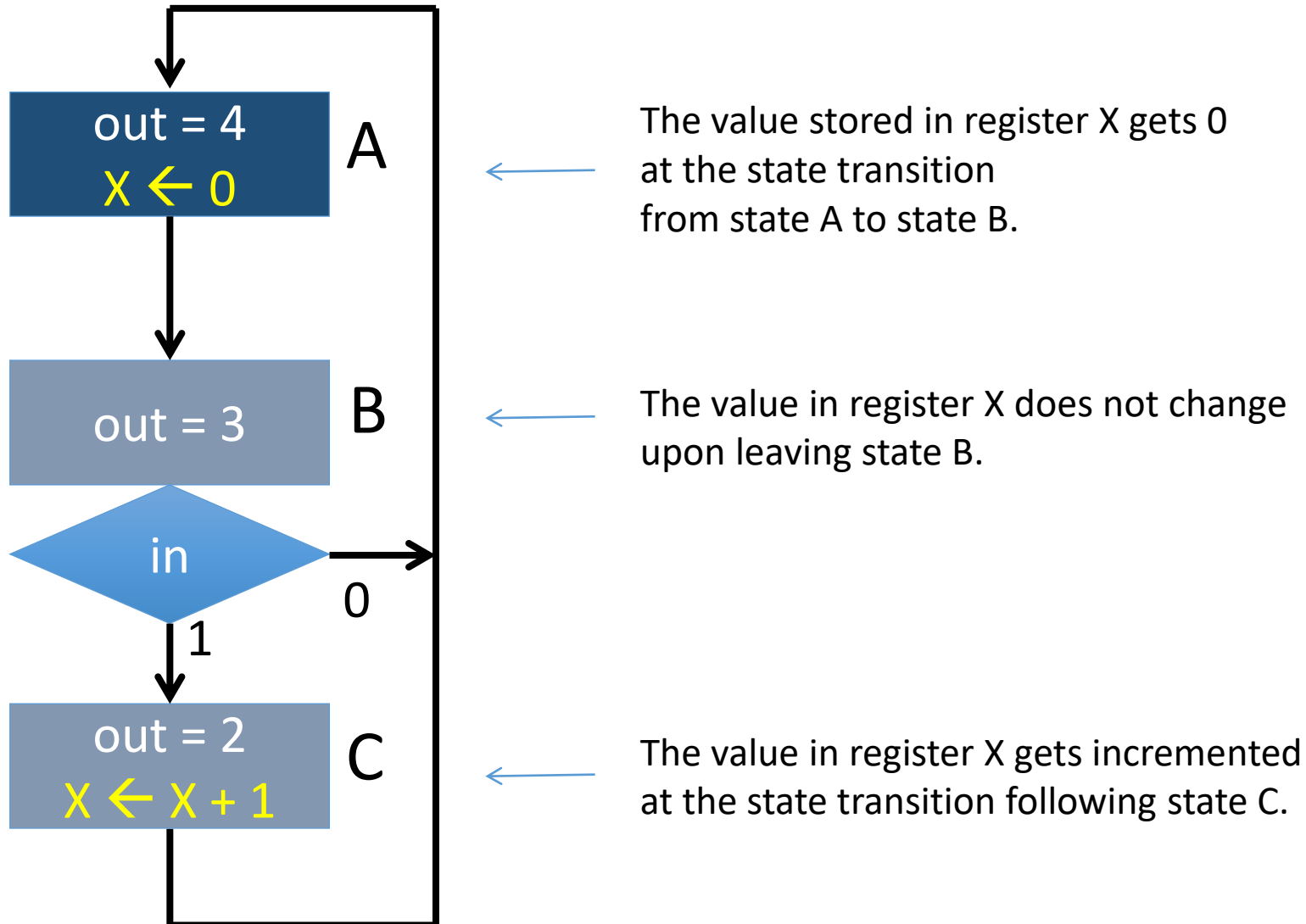ASM diagram with two register-transfer statements




Timing diagram

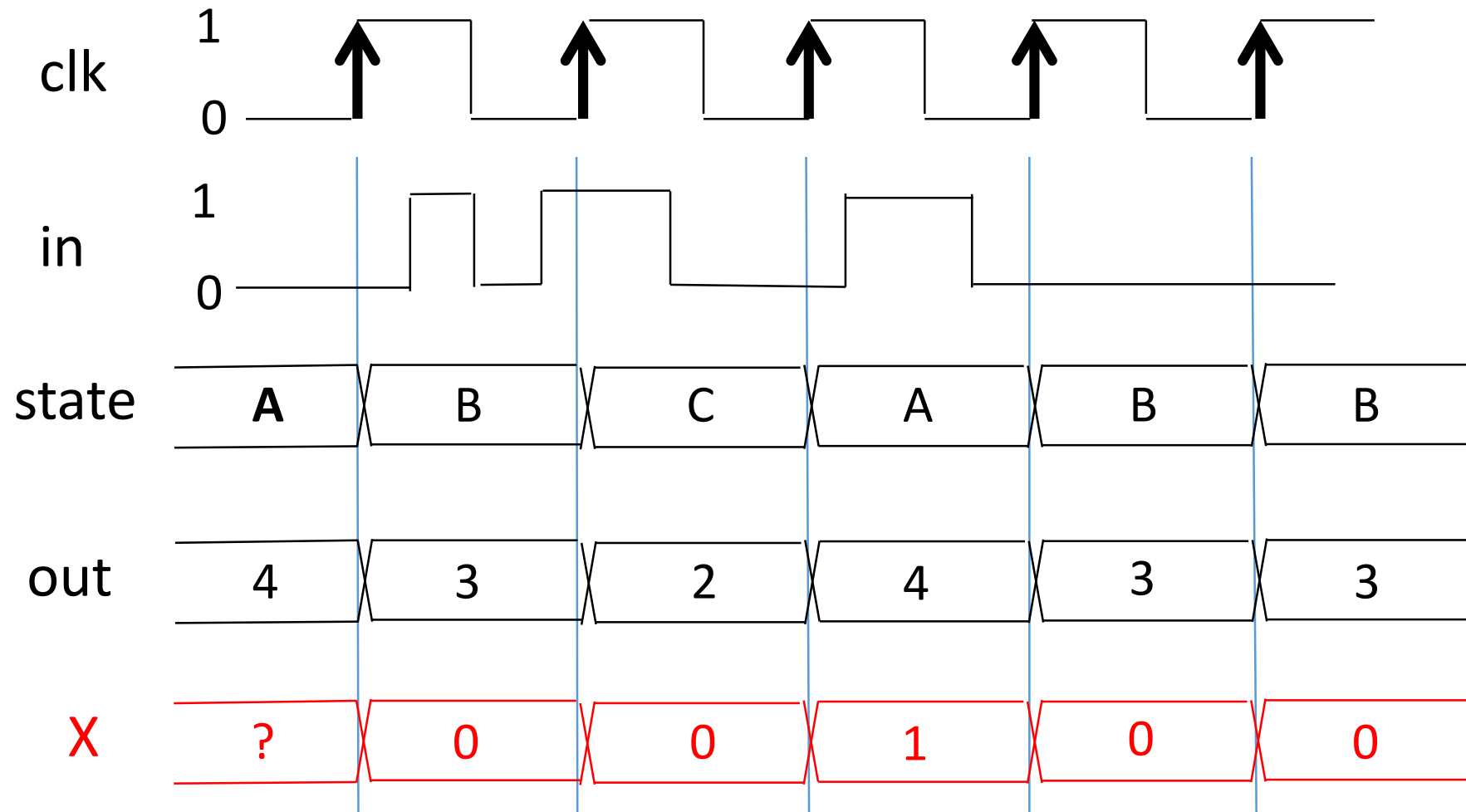

“=” versus “←”

- With the equal sign (“=”) we denote that the output of the FSM has a certain value during a particular state.
- With the left-arrow (“←”) we denote a register-transfer statement: The register value left of the arrow changes to whatever is defined right of the arrow upon the next active (= rising) edge of clock.

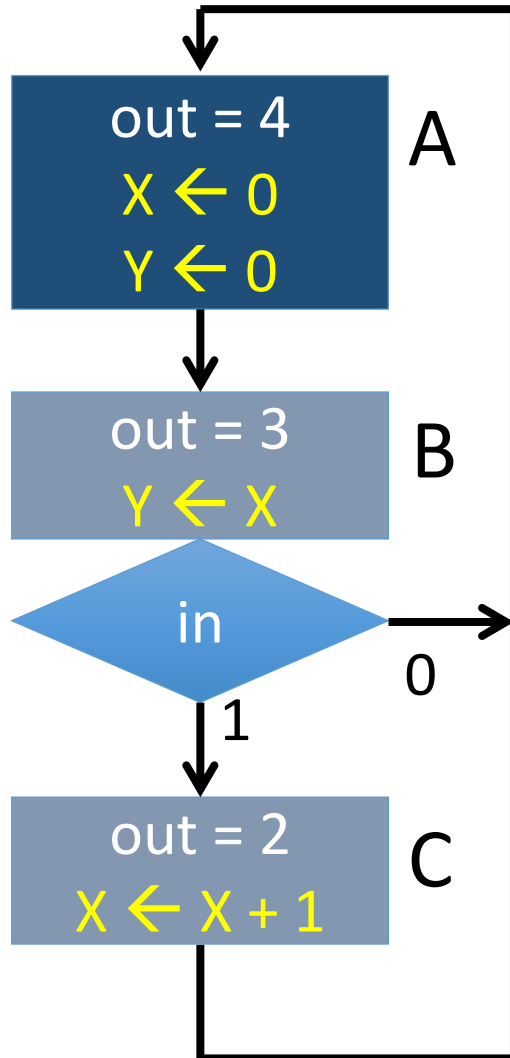Several register-transfer statements can be specified within one state




The values stored in register X and register Y become 0 at the state transition from state A to state B.

The value in register X does not change upon leaving state B. The value stored in register Y gets the value of register X upon leaving state B.

The value in register X gets incremented at the state transition following state C.

 Several register-transfer statements can be specified within one state






The values stored in register X and register Y become 0 at the state transition from state A to state B.

The value in register X does not change upon leaving state B. The value stored in register Y gets the value of register X upon leaving state B.

The value in register X gets incremented at the state transition following state C. Register Y gets the “old” value from X; i.e. the value before X gets incremented.

Separating Control and Data Path

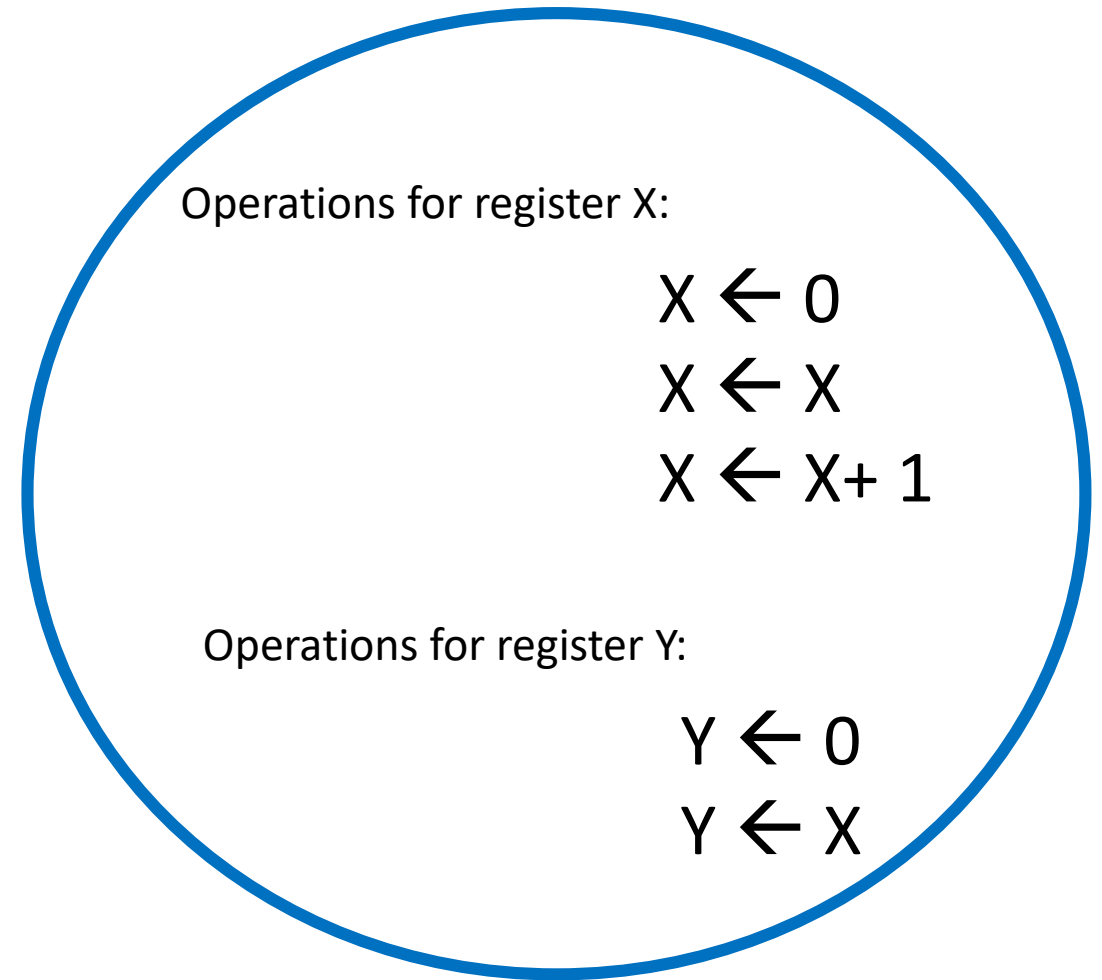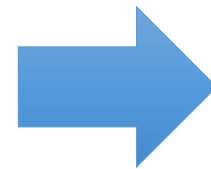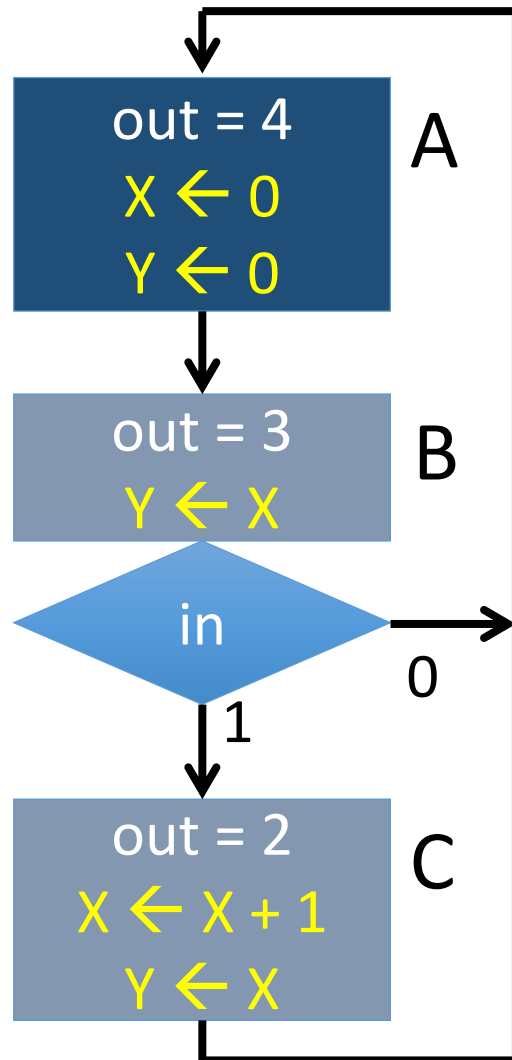Register-Transfer Statements Define the Data Path



These are the actions that our system is able to perform on
The data registers X and Y

Control Unit

- State machine generating control signals for the data path



“Piano Player”


Data Path

- Contains all functional units and registers related to data processing
- Receives control signals to perform operations on the data.
- Provides status signals to the control-related data to the control unit






“Piano”

Music

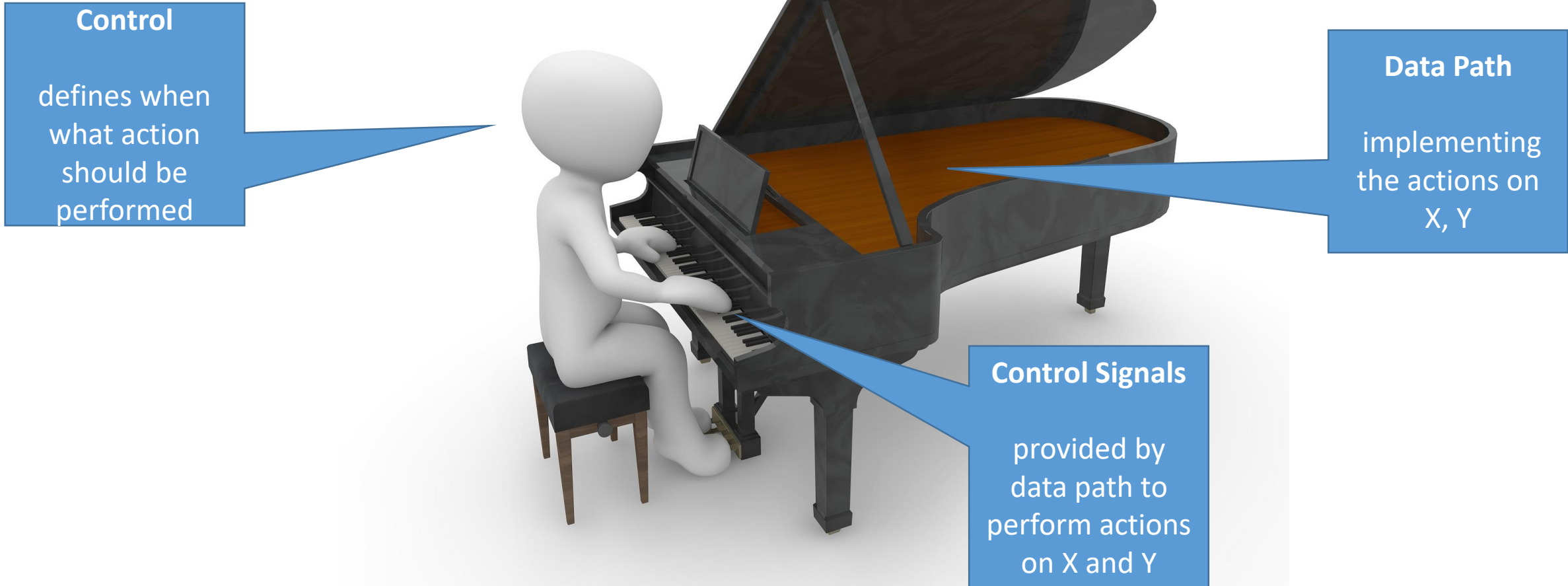

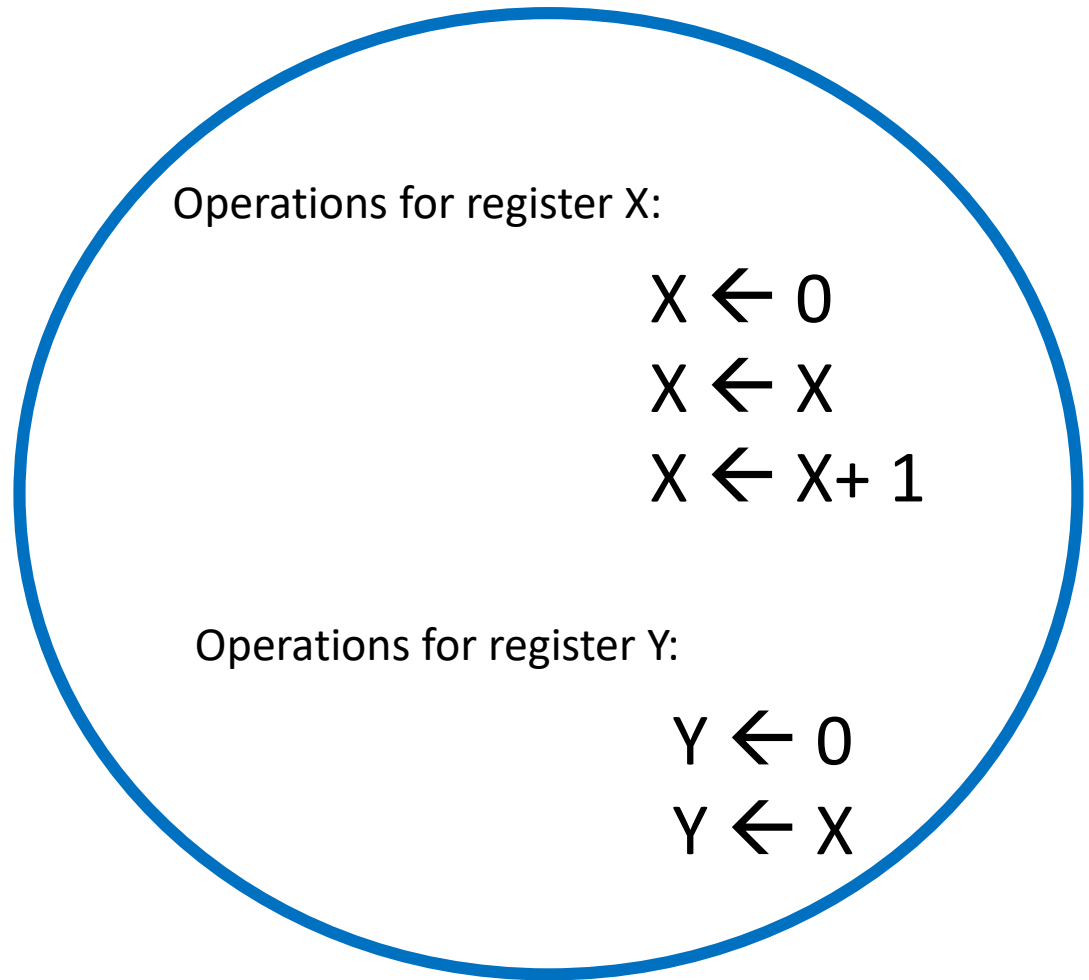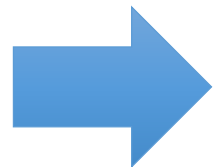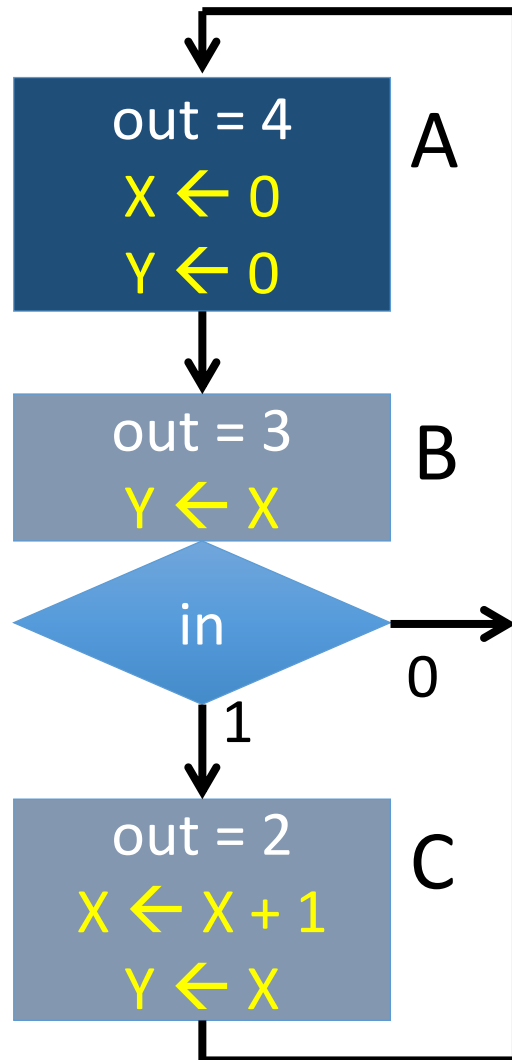Register-Transfer Statements Define the Data Path



These are the operations that our data path implements

Operations for register X

Case 0: $X \leftarrow X$

Case 1: $X \leftarrow X + 1$

Case 2: $X \leftarrow 0$

We need to distinguish
between 3 cases.

→ A one bit control signal is not enough. We need two control signals.

The neighborhood of register X


clrx	incx	action
0	0	$X \leftarrow X$
0	1	$X \leftarrow X + 1$
1	0	$X \leftarrow 0$

We use binary notation
and name the two binary
select variables.

The neighborhood of register X

clr _x	inc _x	action
0	0	$X \leftarrow X$
0	1	$X \leftarrow X + 1$
1	0	$X \leftarrow 0$

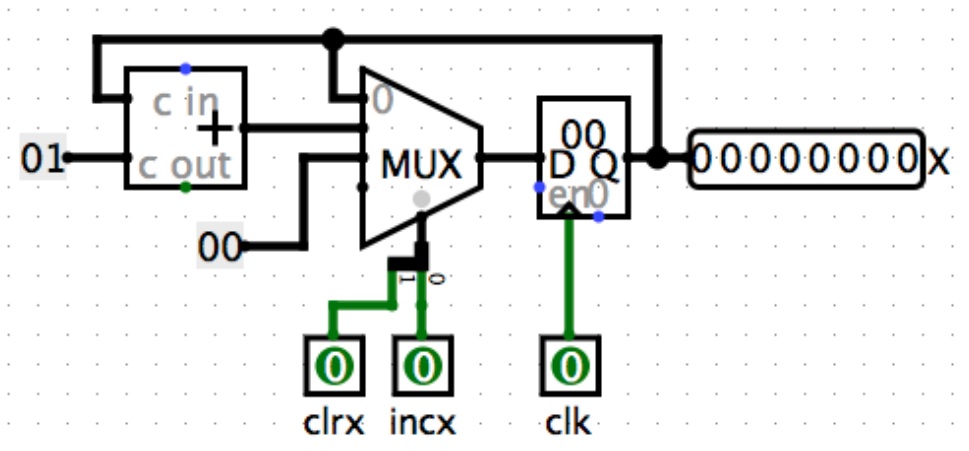
With Logisim we can model the neighborhood of Register and also simulate.




The neighborhood of register Y

clry	ldy	action
0	0	$Y \leftarrow Y$
0	1	$Y \leftarrow X$
1	0	$Y \leftarrow 0$

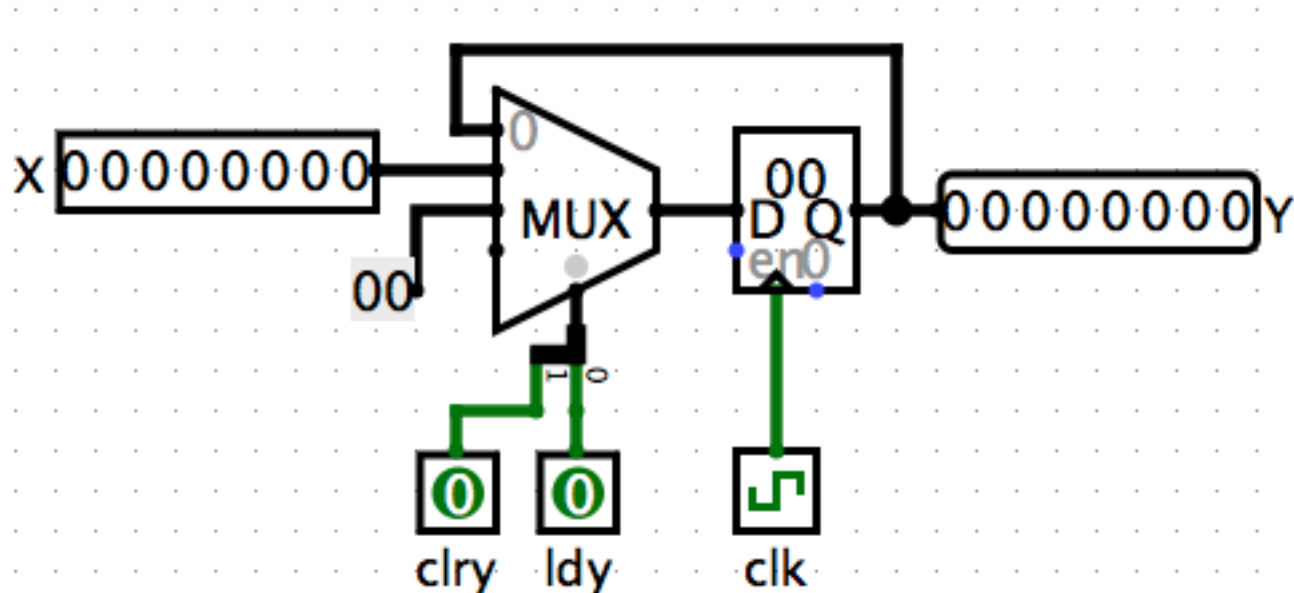In a similar way, we can model the neighborhood of Y.



The datapath

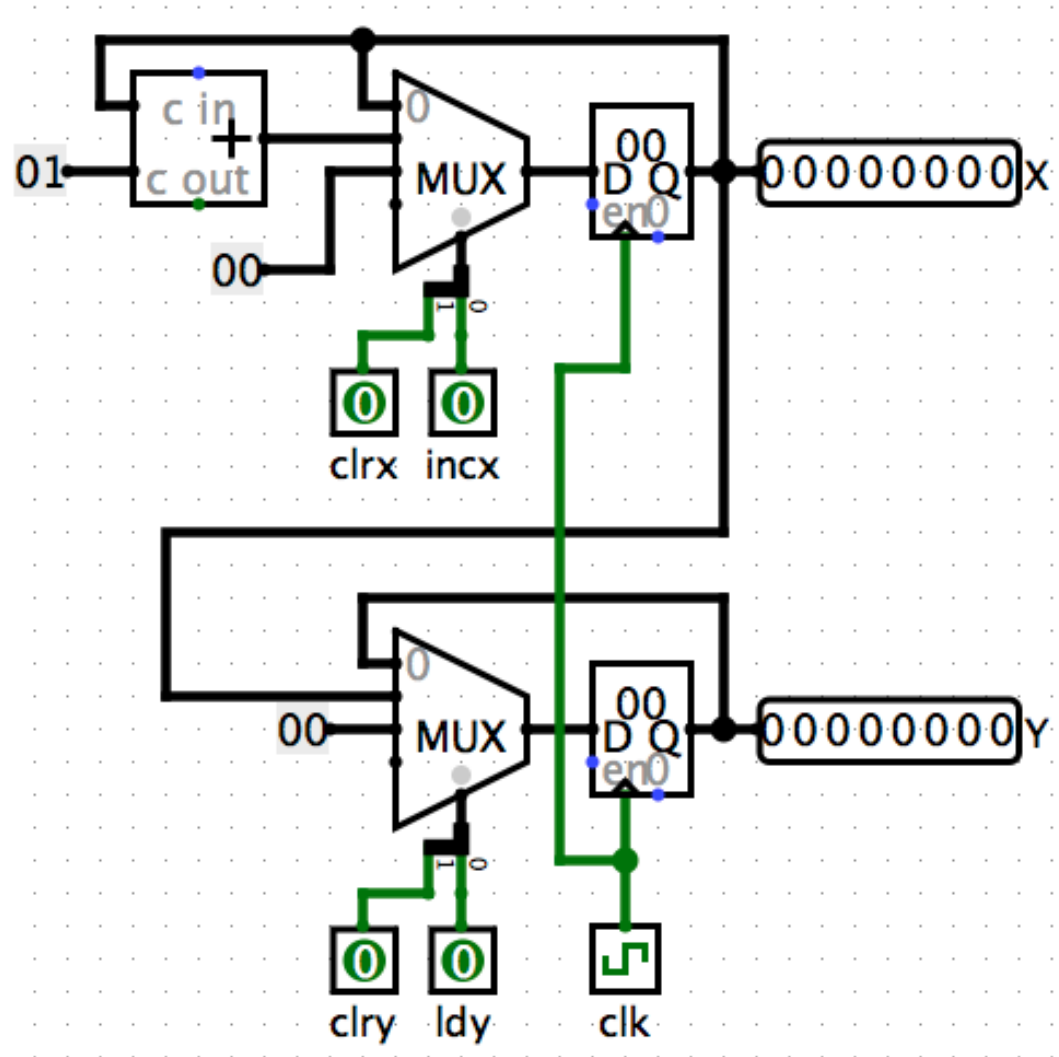


We combine the two neighborhoods.

Note that both neighborhoods are Moore machines.


The Moore machine for X has 2 inputs: *clr x* and *inc x*. Since we have chosen an 8-bit register for X, we have 256 possible states. The output function is the identity function.

The connection of the two is again a Moore machine. Thus, The datapath is a Moore machine.



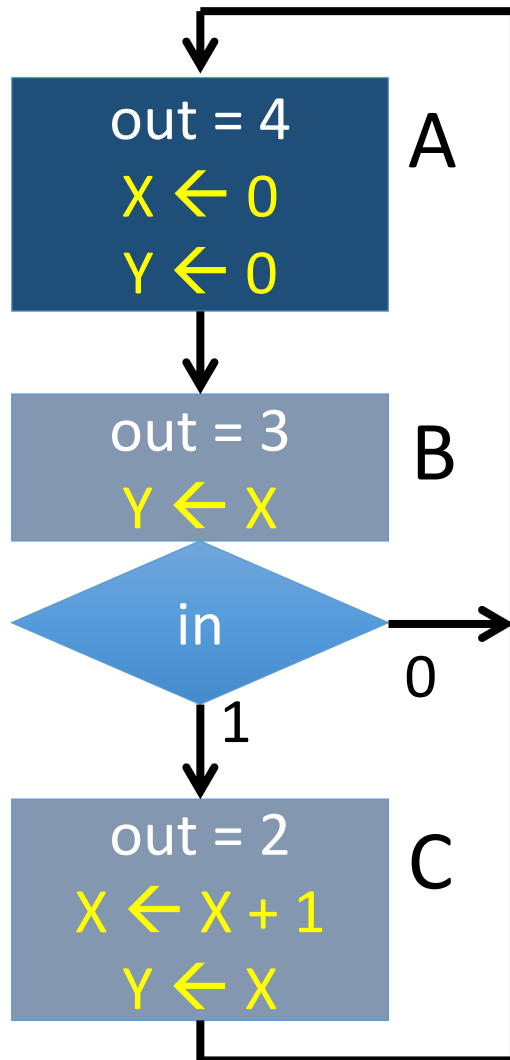
Register-transfer statements define the data path





Datapath:

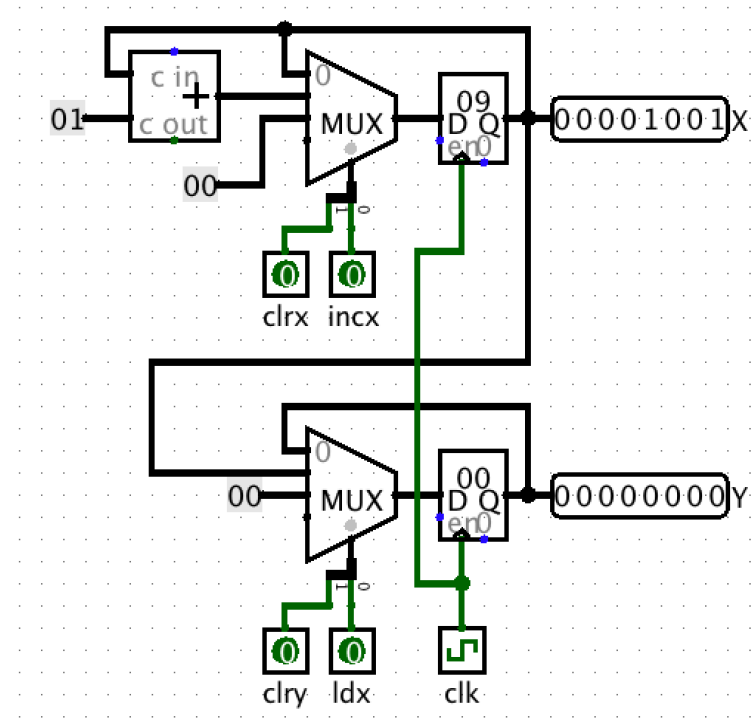

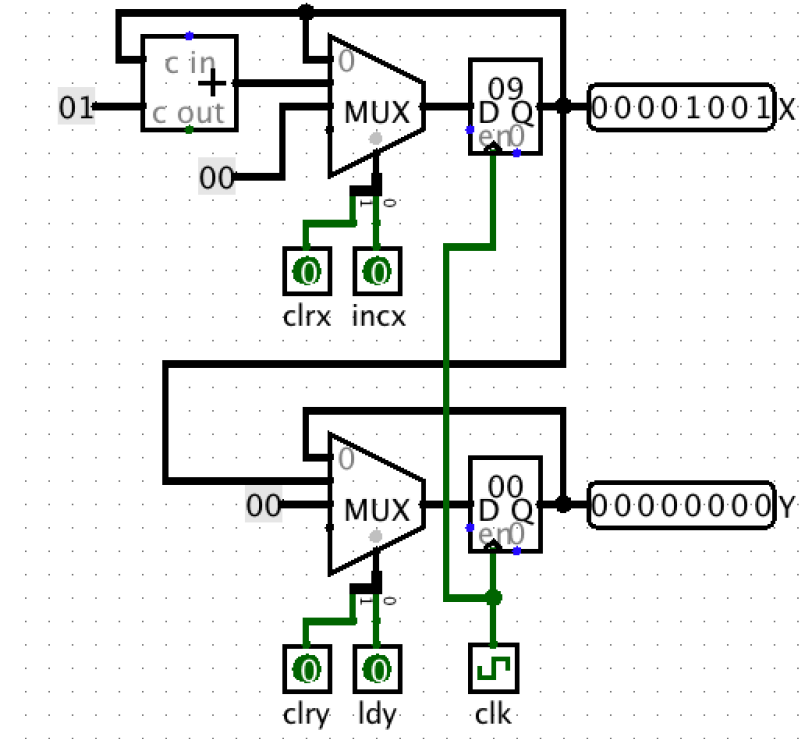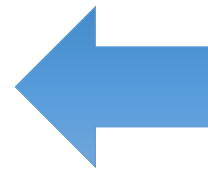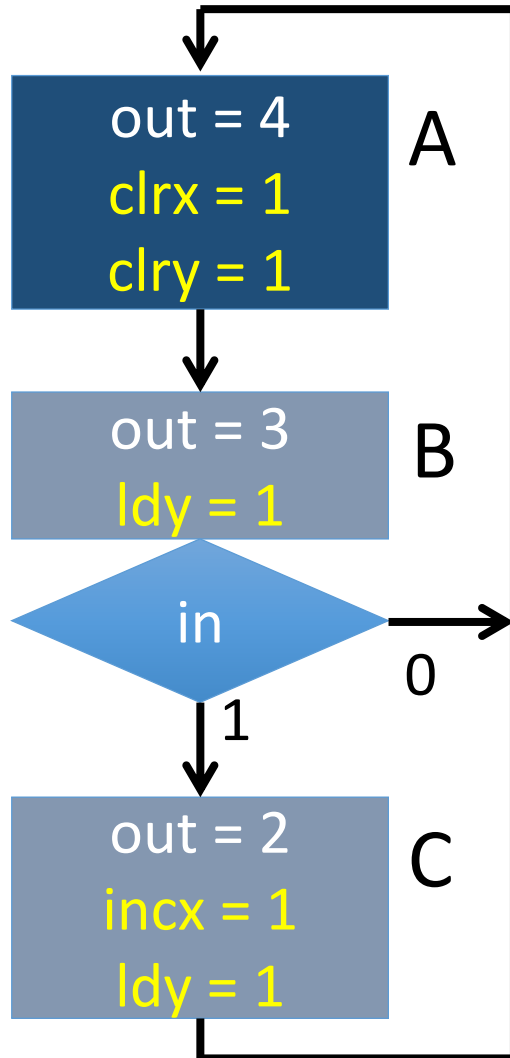The control logic needs to provide the control signals



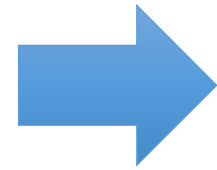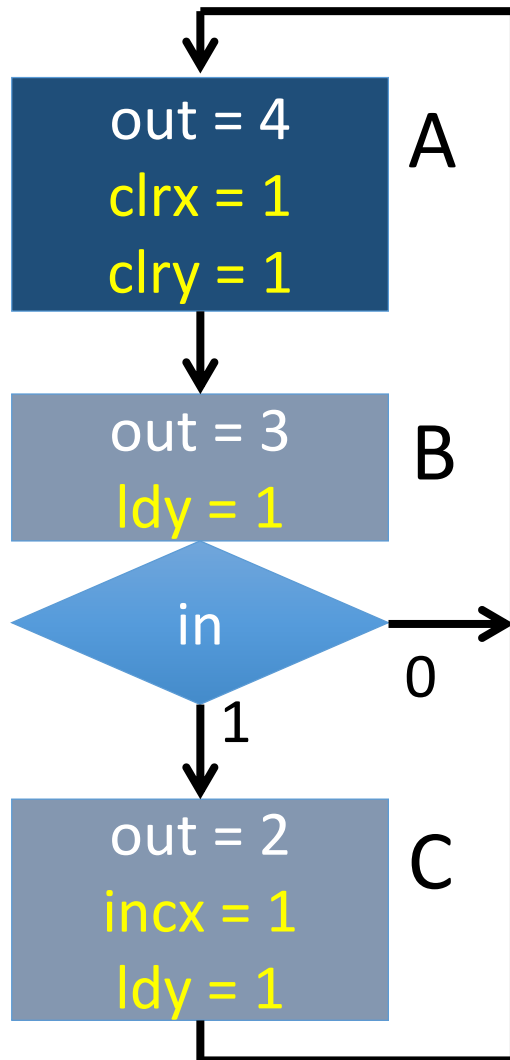Truth table of output logic of controller




state	clrx	incx	clry	ldy	out
0 0	1	0	1	0	100
0 1	0	0	0	1	011
1 0	0	1	0	1	010

A 00
B 01
C 10



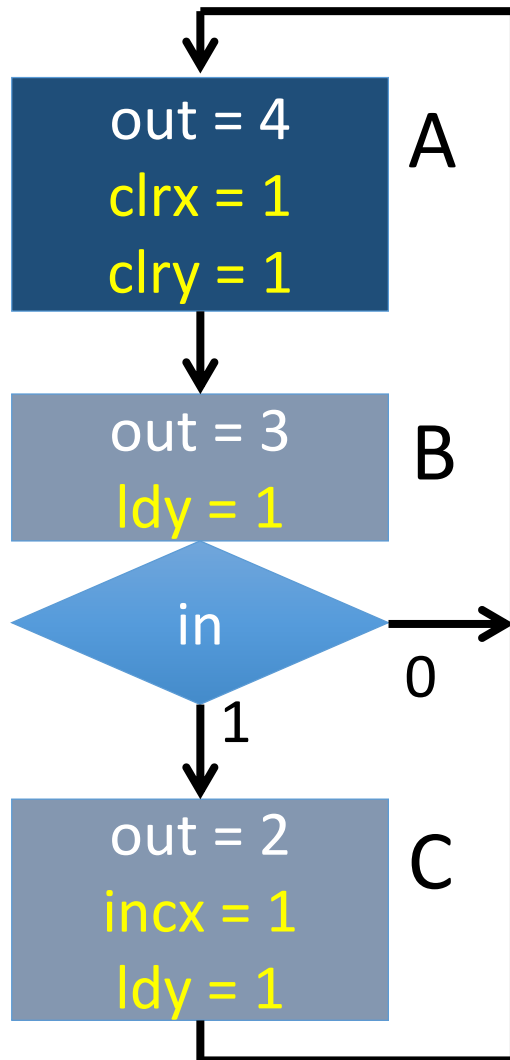
Truth table of next-state logic of controller



state	clrx	incx	clry	ldy	out
0 0	1	0	1	0	100
0 1	0	0	0	1	011
1 0	0	1	0	1	010

state	in	next_state
A	0	B
A	1	B
B	0	A
B	1	C
C	0	A
C	1	A

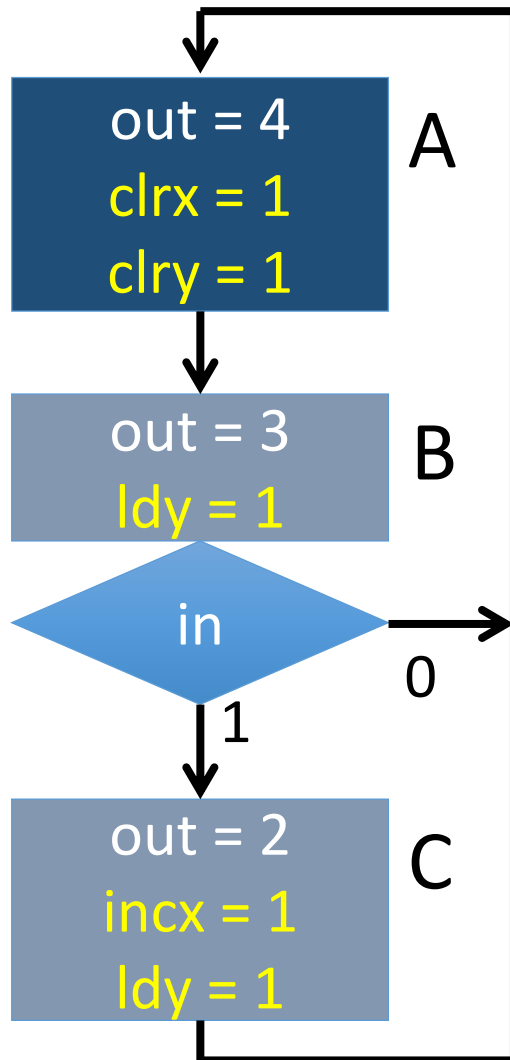Truth table of next-state logic of controller




s1	s0	clrx	incx	clry	ldy	out
0	0	1	0	1	0	100
0	1	0	0	0	1	011
1	0	0	1	0	1	010
1	1	x	x	x	x	xxx

A 00
B 01
C 10


s1	s0	in	ns1	ns0
0	0	0	0	1
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	x	x
1	1	1	x	x

From truth table to implementation

outl:

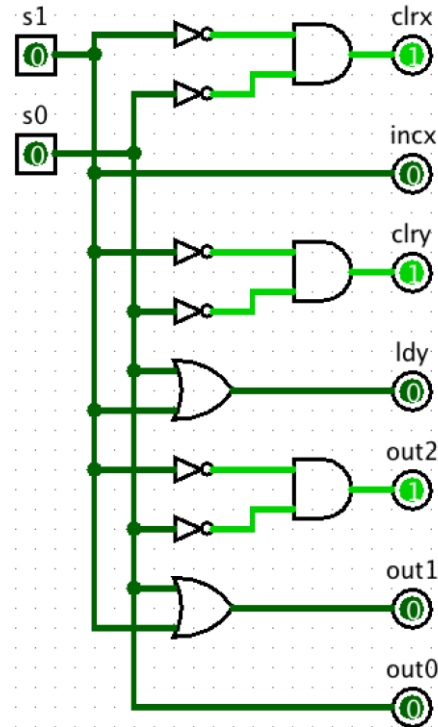


ns1:

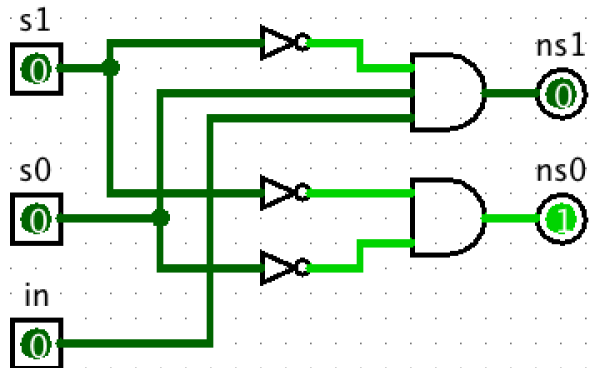

s1	s0	clrx	incx	clry	ldy	out
0	0	1	0	1	0	100
0	1	0	0	0	1	011
1	0	0	1	0	1	010
1	1	x	x	x	x	xxx

s1	s0	in	ns1	ns0
0	0	0	0	1
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	x	x
1	1	1	x	x

The controller and the data path

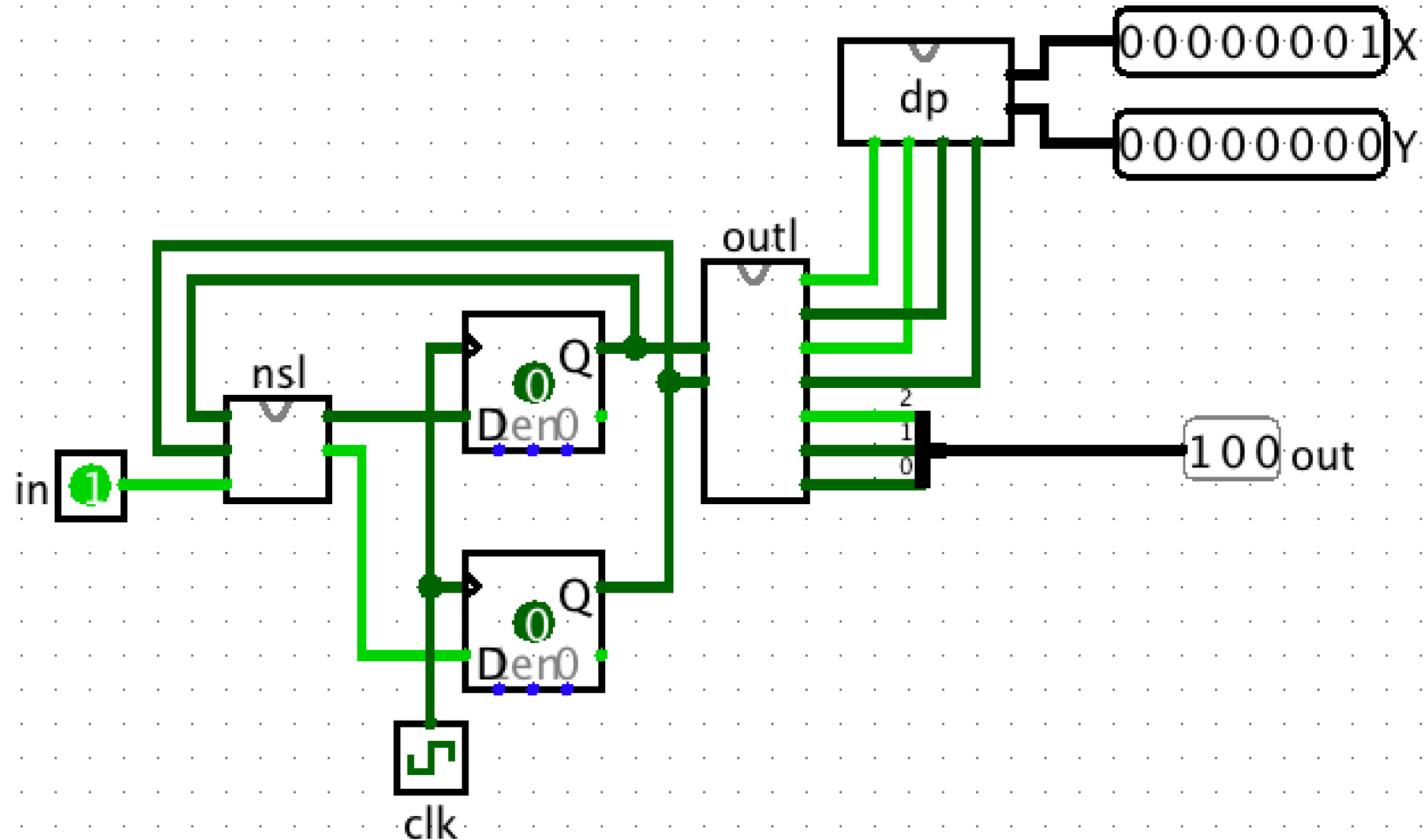

SystemVerilog

(Watch the tutorials for the practicals for details)

SystemVerilog coding style

- Suffix `_o` for module outputs, `_i` for module inputs
- Register variables with suffix `_p` for previous and `_n` for next value
- Array range with `[MSB:LSB]`, like e.g. `[31:0]`
- Clocked processes use non-blocking (`<=`) others use blocking assignments (`=`)
- Clocked processes only update registers, everything else has to be done in combinational blocks
- Filename corresponds to module name: module `MyDesign` in file `mydesign.sv`
- Module instantiation always with named assignments (`.A(C)`)
- **With significant implications beyond style:**
 - Always use default assignments (e.g. `state_n = state_p`)
 - Always use default branches (`default:`) in case statements
 - If you do not assign the output of a combinational block for all input conditions, latches are created for data storage!

Overview of Coding Guidelines

```
always_ff @(posedge clk_i or posedge reset_i)
```


Use Non-Blocking Assignments

```
a_p <= a_n;
```

```
Always_comb
```

Use Blocking Assignments

```
a = b;
```

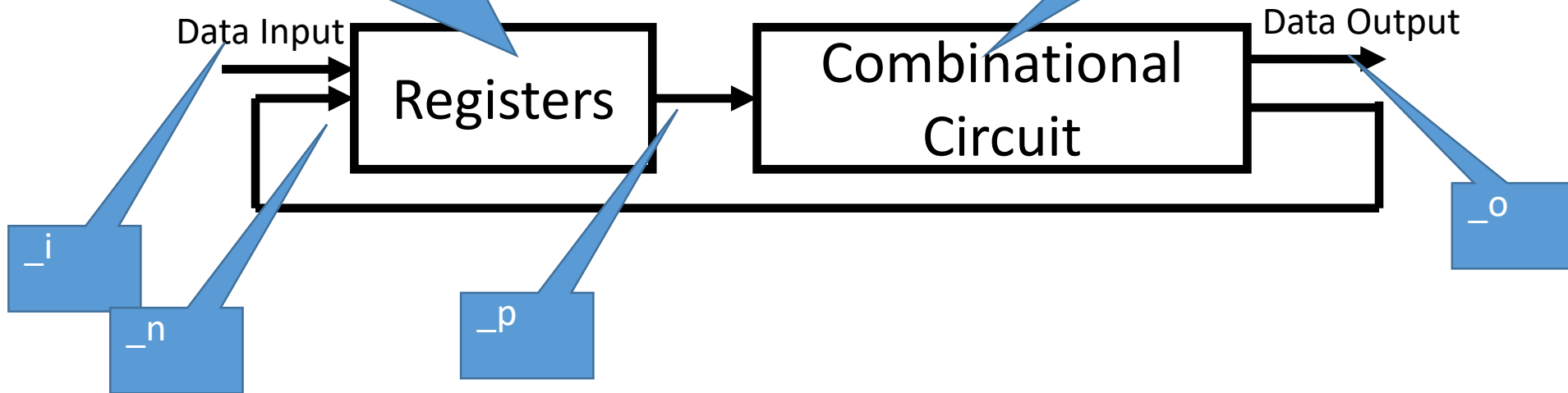


Essence of Moore Machines (Verilog)

`always_comb`

Use Blocking Assignments
`a = b;`

`always_ff @(posedge clk_i or posedge reset_i)`

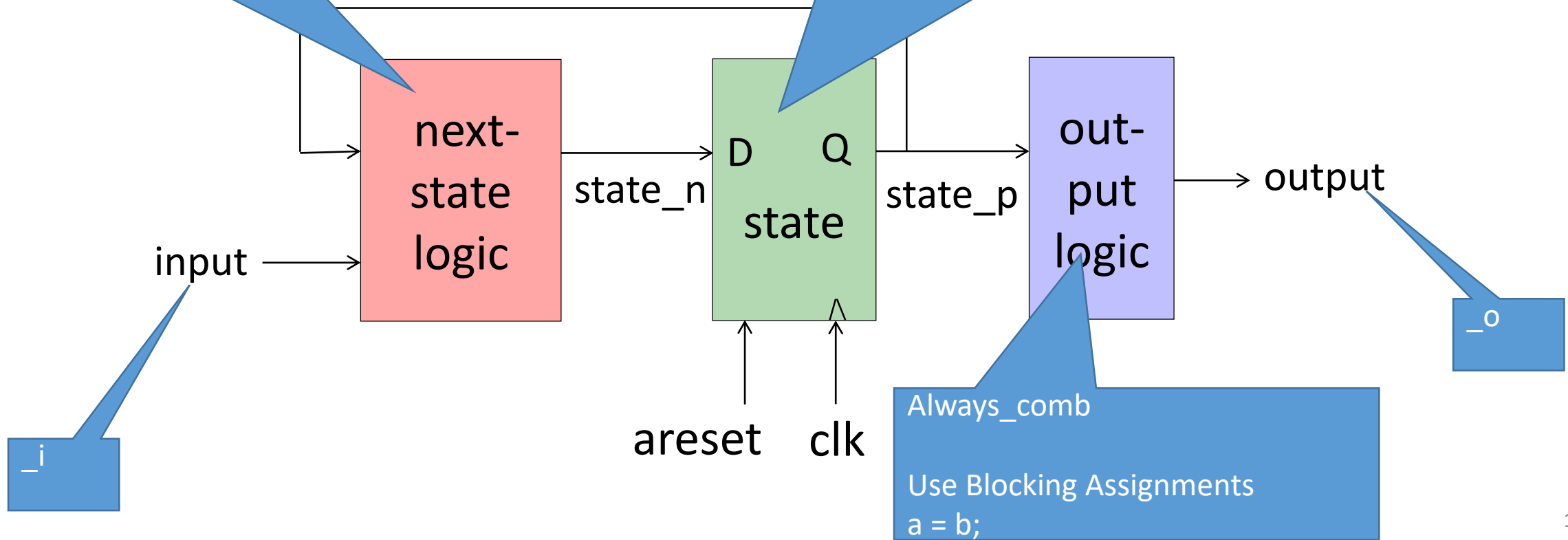Use Non-Blocking Assignments
`state_p <= state_n;`



`Always_comb`

Use Blocking Assignments
`a = b;`

SystemVerilog Examples

- All FSMs of this lecture are available in SystemVerilog as well