

Architecture of FPGAs

Meinhard Kissich

October 22, 2021

Agenda

- Introduction
- Overview
- Configurable Logic Blocks (CLBs)
- (CLB) Slices
- Interconnect Resources
- SelectIO Resource
- FPGA Configuration
- Other Resources

Introduction

What is the presentation about:

- Introductory overview of FPGA resources
- Purpose of resources
- Pointers where to continue reading (**Xilinx User Guides!**)

What is the presentation **not** about:

- Deep insight
- Hands-on


Overview



Zybo Z7 Board Reference Manual

Revised February 21, 2018
This manual applies to the Zybo Z7 rev. B

Figure 1: Zybo Z7 reference [1, p. 1].

 

ZYNQ Processor

- 667 MHz dual-core Cortex-A9 processor
- DDR3L memory controller with 8 DMA channels and 4 High Performance AXI3 Slave ports
- High-bandwidth peripheral controllers: 1G Ethernet, USB 2.0, SDIO
- Low-bandwidth peripheral controllers: SPI, UART, CAN, I2C
- Programmable from JTAG, Quad-SPI flash, and microSD card
- Programmable logic equivalent to **Artix-7 FPGA**

Figure 2: Zybo Z7 specs [1, p. 3].

- Spartan-7: low cost, low power
- Artix-7: low power, high throughput
- Kintex-7: best price-performance
- Virtex-7: highest system performance

Same CLBs in all (7-series) FPGA families [3]

Big Picture


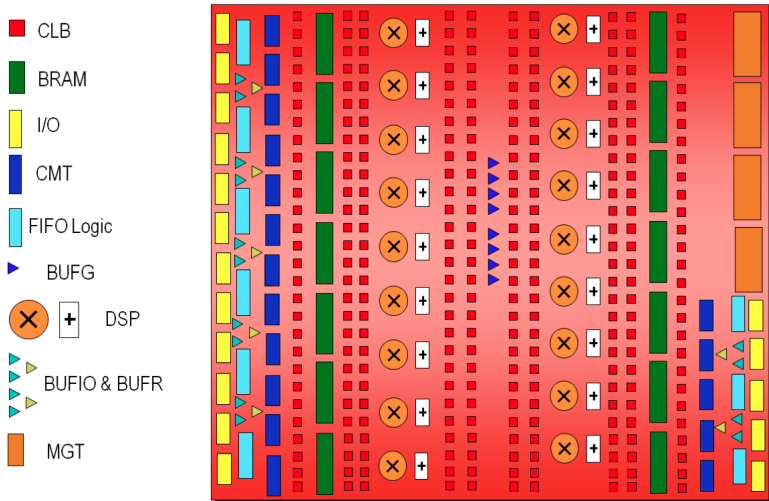


Figure 3: Overview 7 series (ASMBL) architecture [2, p. 9].

Configurable Logic Block (CLB)

Configurable Logic Block

 

- CLBs arranged in columns (ASMBL)
- Connected to switch matrix
- Contains a pair of slices
- No direct connection, each slice organized as a column
- $2 \times$ SLICEL or SLICEL + SLICEM

Figure 4: CLB and slices [3, p. 9].

CLB Slices

- 4×6 -input LUTs
(or 8×5 -input)
(= *logic-function generators*)
- $8 \times$ flip-flops (storage unit)
- Multiplexers
- Arithmetic carry logic

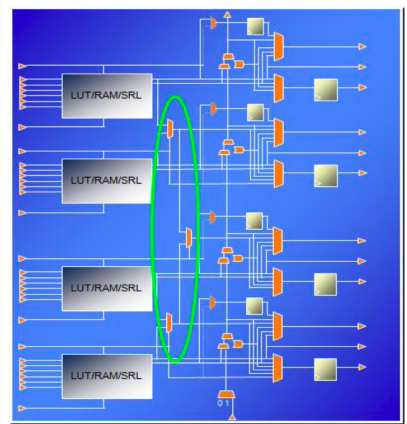


Figure 5: Slice details [2, p. 15].

Look-Up Table

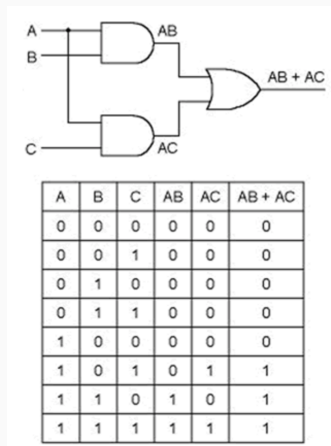


Figure 6: Boolean functions with LUTs [4].

Look-Up Table

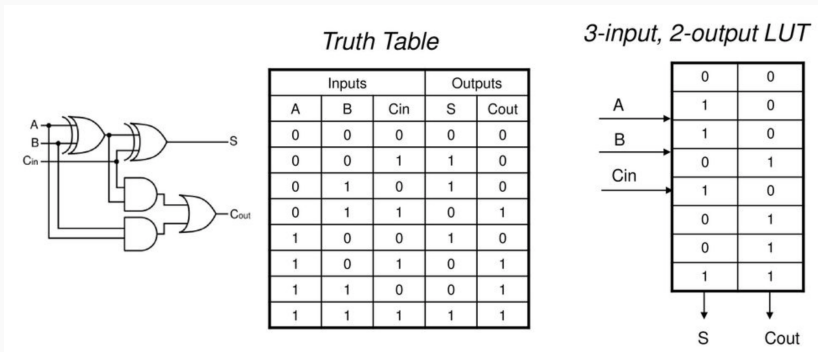


Figure 7: Boolean functions with LUTs [4].

Look-Up Table

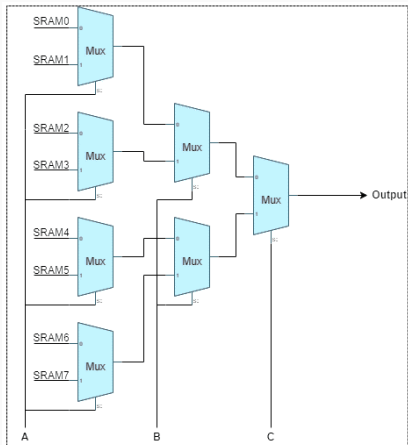


Figure 8: Realization of LUTs [5].

Types of Slices

- $\approx 2/3$: SLICEL logic slices
- $\approx 1/3$: SLICEM logic slices, LUTs also be used as either:
 - Distributed 64×1 RAM
 - 32-bit shift register (SRL32)
 - 2×16 -bit shift registers (SRL16)

Row Architecture

- Coordinate system numbering
- $X_$ column position (different within CLB)
- $Y_$ row position (same within CLB)

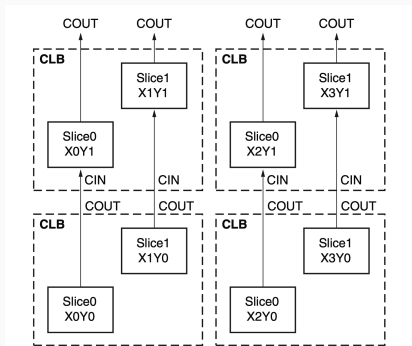


Figure 9: CLB slices [3, p. 17]

Slices in Detail

- 6 inputs (A1 - A6)
- 2 outputs (O5, O6)
- ... for each LUT (A, B, C, D)
- Can build
 - any 6-input boolean function
 - $2 \times$ 5-input boolean functions (common inputs)
 - $2 \times$ arbitrarily boolean functions with $\{2, 3\}$ inputs or less
- Propagation delay independent of function

Multiplexer

- 3 multiplexer (F7AMUX, F7BMUX, F8MUX)
- F7AMUX 7-input function from LUTs A, B
- F7BMUX 7-input function from LUTs C, D
- F8MUX 8-input function from all LUTs
- Functions with more inputs? Multiple slices

Storage Elements

- 8 storage elements
- 4 × D-FF (edge) or latch (level)
 - Latch: transparent with CLK is low
- 4 × only D-FF by LUT (05) or slide inputs (only when others are D-FF)
- Control Signals (CLK, CE, SR) shared within slice

Distributed RAM (only SLICEM)

- LUTs can be used as synchronous RAM (DRAM)
- Various options

RAM	Description	Primitive	Number of LUTs
32 x 1S	Single port	RAM32X1S	1
32 x 1D	Dual port	RAM32X1D	2
32 x 2Q	Quad port	RAM32M	4
32 x 6SDP	Simple dual port	RAM32M	4
64 x 1S	Single port	RAM64X1S	1
64 x 1D	Dual port	RAM64X1D	2
64 x 1Q	Quad port	RAM64M	4
64 x 3SDP	Simple dual port	RAM64M	4
128 x 1S	Single port	RAM128X1S	2
128 x 1D	Dual port	RAM128X1D	4
256 x 1S	Single port	RAM256X1S	4

Figure 10: Options for DRAM [3, p. 24].

Shift Register (only SLICEM)

- LUT configurable as 32-bit shift register w/o using FF
- Each LUT can delay data 1-32 clock cycles
- Cascade for larger shift register
- $4 \times \text{LUT} = 128\text{-bit shift register}$
- Longer SHR: multiple slices (CLBs)

Interconnect Resources

Interconnect Resources

- Transparent to designers
- Selected types are under user control (e.g., clocking)
- Programmable network of signal pathways
- Connections between: IOBs, CLBs, DSP Slices, BRAM, ...
- CLBs connect to switch matrix
- Connect to general-routing resource
- Vertically / horizontally between CLB rows and columns

Interconnect Resources

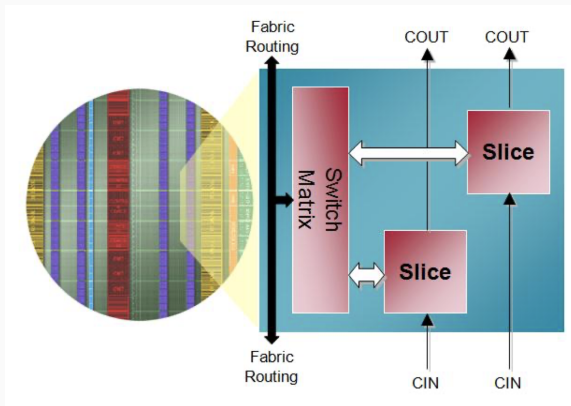


Figure 11: Switch matrix [p. 11, 2].

Interconnect Resources

 


Figure 12: Logic fabric and interconnects [6, p. 23].

SSI (some Virtex-7)

- *Stacked Silicon Interconnect (SSI)*
- In some Virtex-7 devices
- Summarized: a lot of super fast connection to connect super logic regions (SLRs)
- See *CLB User Guide* for more information

SelectIO Resource

- Organized in *banks*
- High performance (HP) banks
 - High-speed memory
 - High-speed chip-to-chip
 - Only up to 1.8V
- High range (HR) banks
 - Wider range of I/O standards
 - Up to 3.3V

I/O Standards

Feature	HP I/O Banks	HR I/O Banks
3.3V I/O standards ⁽¹⁾	N/A	Supported
2.5V I/O standards ⁽¹⁾	N/A	Supported
1.8V I/O standards ⁽¹⁾	Supported	Supported
1.5V I/O standards ⁽¹⁾	Supported	Supported
1.35V I/O standards ⁽¹⁾	Supported	Supported
1.2V I/O standards ⁽¹⁾	Supported	Supported
LVDS signaling	Supported ⁽²⁾	Supported
24 mA drive option for LVCMOS18 and LVTTTL outputs	N/A	Supported
V _{CCAUX_IO} supply rail	Supported	N/A
Digitally-controlled impedance (DCI) and DCI cascading	Supported	N/A
Internal V _{REF}	Supported	Supported

Figure 13: I/O standards, subset [7, p. 13].

- 1 bank = 50 IOBs
 - Pins at edges: single-ended
 - Other 48 pins: single-ended or differential
- input / output / 3-state
- Number of banks defined by device size (pin count)

I/O Block

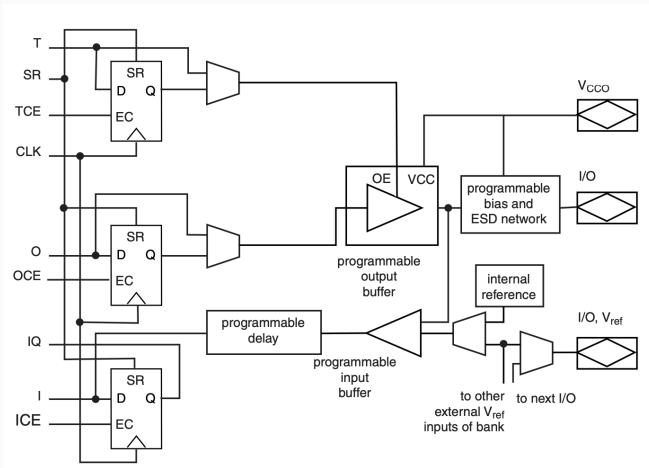


Figure 14: I/O block of Spartan-II [8, p. 140].

I/O Block Components

The usage can be summarized as:

- right side: handling of I/O standards, reference voltage
- left side: buffers, one for I/O/Three-State, FF or latch
- programmable delay: compensate variations in hold time on input path

FPGA Configuration

- FPGA needs to be configured (volatile)
- Data stored in *CMOS Configuration Latches* (CCL)
- Reprogrammed unlimited number of times
- Different configuration options
 - Master-mode: CLK driven by FPGA
 - (e.g., to load from SPI flash)
 - Slave-mode: FPGA uses CLK input
 - JTAG
- Bitstream length depends on device
 - 7S6 (smallest Spartan): 4,310,752 bits (min 8Mb)
 - 7VH870T (biggest Virtex): 294,006,336 bits (min 512Mb)

Configuring a 7-series device

 


Figure 15: Device power-up [9, p. 85].

Other Resources

RAMB36 Block RAM

- $2 \times 18 \text{ Kb}$ or $1 \times 36 \text{ Kb}$
- Various configuration options
 - $64\text{K} \times 1$ (with adjacent)
 - $32\text{K} \times 1$
 - $16\text{K} \times 2$
 - ...
- Synchronous r/w, 2 ports independent
- Data can be initialized by bitstream
- Many, many more configurations

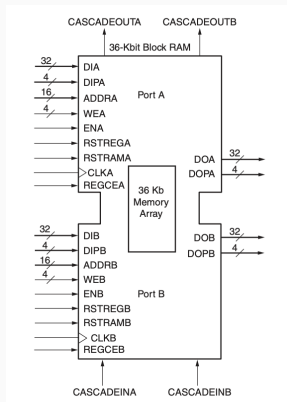


Figure 16: RAMB36 [10, p. 16].

- Hardware is great for DSP
- DSP with CLBs is expensive
- Many dedicated, full-custom, low-power DSP slices

DSP48E1 Slices

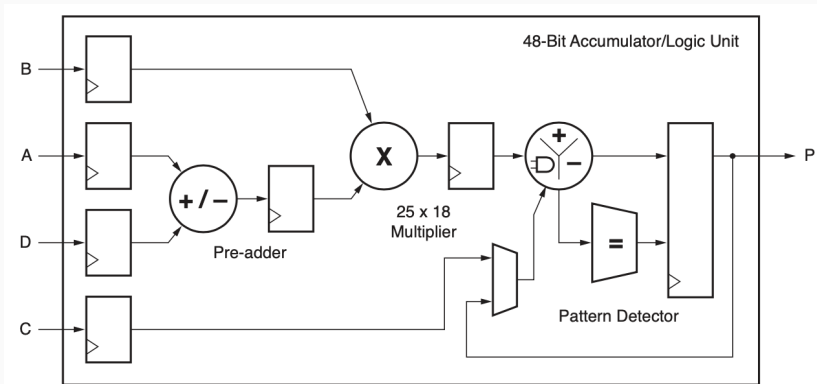


Figure 17: DSP48E1 [11, p. 9].

- 25×18 two's complement multiplier
- 48-bit accumulator (opt. sync. up/down counter)
- Pre-adder (for symmetrical filter applications)
- SIMD arithmetic unit (2×24 -bit, 4×12 -bit)
- Logic unit (any of 10 logic functions of 2 operands)
- Pattern detector (rounding, 96-bit-wide logic function with LU)
- See *7 Series DSP48E1 Slice User Guide* for more details

- Clock Management Tiles (CMT) provide frequency synthesis, deskew, jitter filter
- Clock tree to distribute clock signal
- CMTs contain
 - Mixed-Mode Clock Manager (MMCM)
 - Phase-Locked Loop (PLL)
- FPGA divided into clock regions
- More information: *Clocking Resource User Guide*

Thank You For Your Attention

Do you have any Questions?

- [1] Digilent. *Zybo Z7 Board Reference Manual*.
https://digilent.com/reference/_media/reference/programmable-logic/zybo-z7/zybo-z7_rm.pdf. Online; accessed 06 October, 2021.
- [2] Xilinx. *7-Series Architecture Overview*. http://xilinx.eetrend.com/files-eetrend-xilinx/forum/201509/9204-20390-7_series_architecture_overview.pdf. Online; accessed 07 October, 2021.
- [3] Xilinx. *7 Series FPGAs Configurable Logic Block. User Guide*.
https://www.xilinx.com/support/documentation/user_guides/ug474_7Series_CLB.pdf. Online; Version September 27, 2016.

- [4] *How to execute the Boolean Algebra in a Look-up Table.*
[https://fpgabeginner.com/
how-to-do-executing-the-boolean-algebra-in-a-look-up-table](https://fpgabeginner.com/how-to-do-executing-the-boolean-algebra-in-a-look-up-table)
Online; accessed 22 October, 2021.
- [5] *The Ultimate Guide to FPGA Architecture.*
[https://hardwarebee.com/
the-ultimate-guide-to-fpga-architecture/](https://hardwarebee.com/the-ultimate-guide-to-fpga-architecture/). Online;
accessed 22 October, 2021.
- [6] Crockett, Louise H. et al *The Zynq Book*
<http://www.zynqbook.com>

- [7] Xilinx. *7 Series FPGAs SelectIO Resources. User Guide.*
https://www.xilinx.com/support/documentation/user_guides/ug471_7Series_SelectIO.pdf. Online; Version May 8, 2018.
- [8] *FPGA Fabrics.*
https://ptgmedia.pearsoncmg.com/images/0131424610/samplechapter/0131424610_ch03.pdf. Online; accessed 22 October, 2021.
- [9] Xilinx. *7 Series FPGAs Configuration Resources. User Guide.*
https://www.xilinx.com/support/documentation/user_guides/ug470_7Series_Config.pdf. Online; Version August 20, 2018.

- [10] Xilinx. *7 Series FPGAs Memory Resources. User Guide.*
https://www.xilinx.com/support/documentation/user_guides/ug473_7Series_Memory_Resources.pdf. Online; Version July 3, 2019.
- [11] Xilinx. *7 Series DSP48E1 Slice. User Guide.*
https://www.xilinx.com/support/documentation/user_guides/ug479_7Series_DSP48E1.pdf. Online; Version March 27, 2018.
- [12] Bajaj, Ronak and Fahmy, Suhaib. *Mapping for maximum performance on FPGA DSP blocks* https://www.researchgate.net/publication/282398023_Mapping_for_maximum_performance_on_FPGA_DSP_blocks