

Verilog HDL Review

October 10, 2022


Ahmet Can Mert

ahmet.mert@iaik.tugraz.at



Hardware Description Language (HDL): Overview of a Digital System

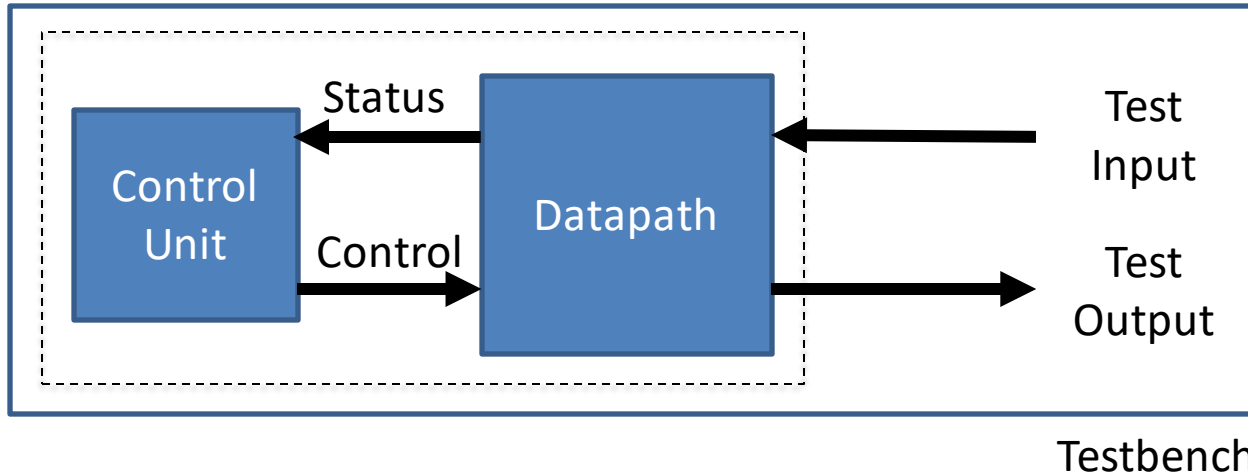- Datapath
 - Performs data processing
- Control Unit (Finite State Machine)
 - Generates control signals to control the datapath
- Testbench
 - Used to verify the functional correctness of the design (for simulation)





Hardware Description Language (HDL): Definition

- It is **NOT** a programming language.
- It is used to describe any digital circuit.
 - i.e., you can describe circuit elements and connections between them.
- Many languages available for RTL Modeling: VHDL, Verilog, SystemVerilog
 - **Verilog** is simple and similar to C
 - Verilog has more than half of the world digital design market
 - Many free resources are available:
 - <http://www.asic-world.com/verilog/veritut.html>
 - <https://www.chipverify.com/verilog/>

Hardware Description Language (HDL): Logic and Memory

  - Register Transfer Level: An abstract level used to describe the operation of synchronous digital circuits.
 - Logic Functions (computation)
 - Any combinatorial computation
 - Memory (update)
 - Flip-Flop: edge sensitive
 - Latch: level sensitive (WE WILL NOT USE)



Verilog Operators

- Logical, arithmetic and conditional operators

Syntax	Operation
~	Bit-wise negation
&	AND
!&	NAND
	OR
~	NOR
^	XOR
^~ or ~^	XNOR

i.e.,

```
c = ~a;
```

```
c = a & b;
```

Syntax	Operation
+	Addition
-	Subtraction
*	Multiplication
/	Division
%	Modulo
<<	Left shift
>>	Right shift

i.e.,

```
c = a + b;
```

```
c = a >> 2;
```

Syntax	Operation
==	Equality
!=	Inequality
<	Less than
<=	Less than or equal
>	Greater than
>=	Greater than or equal

i.e.,

```
c = (a==b) ? 1 : 0;
```

Verilog Operators

- Operator precedence is important.

Verilog Operator	Name	Functional Group
[]	bit-select or part-select	
()	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
===	case equality	equality
!==	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
~^ or ^~	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

* Table from: <https://class.ece.uw.edu/cadta/verilog/operators.html>

Verilog Operators

- Operator precedence is important.

Verilog Operator	Name	Functional Group
[]	bit-select or part-select	
()	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
===	case equality	equality
!==	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
~^ or ^~	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

`c0 = a + b << 2;`

<code>a = 4, b = 1</code>
<code>c0 = (5 << 2) = 20</code>

Verilog Operators

- Operator precedence is important.

Verilog Operator	Name	Functional Group
[]	bit-select or part-select	
()	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
===	case equality	equality
!==	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
~^ or ^~	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

```
c0 = a + b << 2;
```

<pre>a = 4, b = 1 c0 = (5 << 2) = 20</pre>
--

```
c1 = a + (b << 2);
```

<pre>a = 4, b = 1 c1 = 4 + (1<<2) = 8</pre>

Verilog Operators - Example

- Using + operator to design an adder
 - 4-bit inputs and 5-bit output



- { } operator is used to concatenate signals
 - Carry is 1-bit
 - Sum is 4-bit

{Carry, Sum} = A + B;

- { { } } operator is used to repeat a signal
 - Repeating Carry[0] bit four times

{Carry[0], Carry[0], Carry[0], Carry[0]} --> {4{Carry[0]}}

Language Element - Literals

- Literals are constant numbers (in binary, octal, decimal and hexadecimal).
- Literals as represented as:

<size>' <signed><radix>value

Language Element - Literals

- Literals are constant numbers (in binary, octal, decimal and hexadecimal).
- Literals as represented as:

<size>'<signed><radix>value

- e.g., A = 16' d12987;
 - 16 indicates the bit size of the signal
 - d indicates decimal representation is used.
 - b or B -> binary
 - o or O -> octal
 - d or D -> decimal
 - h or H -> hexadecimal
 - No s after ' shows it is unsigned
- e.g., B = 20;
 - If bit size, sign and radix are not specified, default representation is 32-bit unsigned decimal

Language Element - Literals

- Literals are constant numbers (in binary, octal, decimal and hexadecimal).
- Literals as represented as:

<size>'<signed><radix>value

- e.g., A = 16' d12987;
 - 16 indicates the bit size of the signal
 - d indicates decimal representation is used.
 - b or B -> binary
 - o or O -> octal
 - d or D -> decimal
 - h or H -> hexadecimal
 - No s after ' shows it is unsigned
- e.g., B = 20;
 - If bit size, sign and radix are not specified, default representation is 32-bit unsigned decimal.

Language Elements – Data Types

- Bus definition
 - n-bit data type declaration
 - `reg [n-1:0] a;`
 - `wire [n-1:0] a;`
 - Part selection:

```
reg [31:0] a,b;  
wire [16:0] sum;  
assign sum = a[15:0]+ b[15:0];
```

Language Elements – Data Types

- Bus definition
 - n-bit data type declaration
 - `reg [n-1:0] a;`
 - `wire [n-1:0] a;`
 - Part selection:

```
reg [31:0] a,b;  
wire [16:0] sum;  
assign sum = a[15:0]+ b[15:0];
```

- Verilog is case-sensitive
 - `reg [3:0] Rega, RegA;`
- Net/Variable names cannot start with a number
 - `reg [3:0] 2num;` ❌
 - `reg [3:0] num2;`

Language Elements – Module and ports

- Verilog module declaration starts with `module` and ends with `endmodule`.

```
module module_name (<port list>;  
  
    // Module content  
  
endmodule
```

- Module ports (by default, ports are considered as type `wire`):
 - `input`
 - `output`
 - `inout`

Language Elements – Module and ports

- Example:

```
module add_unit (a,b,c);  
  
input [3:0] a,b;  
output [4:0] c;  
  
assign c = a+b;  
  
endmodule
```

```
module add_unit (input [3:0] a,b,  
                output [4:0] c);  
  
assign c = a+b;  
  
endmodule
```


Language Elements – Statements

- Statements are used to drive nets
 - There are two different methods to define Statements:
 - `assign`
Combinational (Blocking: =)
 - `always`
Combinational (Blocking: =)
Sequential (Non-blocking: <=)

Language Elements – `assign` Statement

- It is used to drive `output` and `wire` types. It is used to define combinational circuit parts.
- Order of `assign` statements is not important.
- When a variable at the RHS of assign statement changes, LHS is re-evaluated.

Language Elements – `assign` Statement

- It is used to drive `output` and `wire` types. It is used to define combinational circuit parts.
- Order of `assign` statements is not important.
- When a variable at the RHS of assign statement changes, LHS is re-evaluated.

```
module Module_1 (A, B, C, D, E);  
  
    input [3:0]  A, B, C;  
    output [11:0] D, E;  
  
    wire [4:0] t1, t2, t3;  
  
    assign t1 = A + B;  
    assign t2 = A - B;  
    assign t3 = (C << 1);  
    assign D = (t1 * t2) + t3;  
    assign E = A * C;  
  
endmodule
```

Language Elements – assign Statement

- It is used to drive `output` and `wire` types. It is used to define combinational circuit parts.
- Order of `assign` statements is not important.
- When a variable at the RHS of assign statement changes, LHS is re-evaluated.

```
module Module_1 (A, B, C, D, E);  
  
    input [3:0] A, B, C;  
    output [11:0] D, E;  
  
    wire [4:0] t1, t2, t3;  
  
    assign t1 = A + B;  
    assign t2 = A - B;  
    assign t3 = (C << 1);  
    assign D = (t1 * t2) + t3;  
    assign E = A * C;  
  
endmodule
```

- When `A` changes, the new values of `t1`, `t2` and `E` are computed concurrently

Language Elements – assign Statement

- It is used to drive `output` and `wire` types. It is used to define combinational circuit parts.
- Order of `assign` statements is not important.
- When a variable at the RHS of assign statement changes, LHS is re-evaluated.

```
module Module_1 (A, B, C, D, E);  
  
    input [3:0] A, B, C;  
    output [11:0] D, E;  
  
    wire [4:0] t1, t2, t3;  
  
    assign t1 = A + B;  
    assign t2 = A - B;  
    assign t3 = (C << 1);  
    assign D = (t1 * t2) + t3;  
    assign E = A * C;  
  
endmodule
```

- When A changes, the new values of t1, t2 and E are computed concurrently
- Since t1 and t2 are updated, D is re-evaluated

Language Elements – assign Statement

- It is used to drive `output` and `wire` types. It is used to define combinational circuit parts.
- Order of `assign` statements is not important.
- When a variable at the RHS of assign statement changes, LHS is re-evaluated.


```
module Module_1 (A, B, C, D, E);  
  
    input [3:0] A, B, C;  
    output [11:0] D, E;  
  
    wire [4:0] t1, t2, t3;  
  
    assign t1 = A + B;  
    assign t2 = A - B;  
    assign t3 = (C << 1);  
    assign D = (t1 * t2) + t3;  
    assign E = A * C;  
  
endmodule
```

- When A changes, the new values of t1, t2 and E are computed concurrently
- Since t1 and t2 are updated, D is re-evaluated
- D does not update any net

Language Elements – `assign` Statement

- No combinatorial loops
 
```
wire [7:0] b;  
assign b = b + 1;
```



- No combinatorial loops between signals in a clock cycle

Language Elements – *always* Statement

- It is used to drive *reg* types. It is used to define both combinational and sequential parts.
- A **sensitivity list** is defined for each *always* block.
 - It has signals that trigger the execution of the logic defined in *always* block
- Syntax:

```
always @(sensitivity list)
begin
    <your logic>
end
```

Clock-sensitive synchronous design

```
always @(posedge clk)
begin
    <your logic>
end
```

Combinational design

```
always @(*)
begin
    <your logic>
end
```


Language Elements - Conditional Assignments

- Three ways to do conditional assignment.
- Method1: `if/else if/else`


```
always @ (*)
begin
    if (S==1'b0)
        Y = I0;
    else
        Y = I1;
end
```

- Method2: `case/endcase`

```
always @ (*)
begin
    case (S)
        1'b0: Y = I0;
        1'b1: Y = I1;
    endcase
end
```

- Method3:
 
```
always @ (*)
begin
    Y = (S) ? I1 : I0;
end
```




Language Elements - Conditional Assignments

- Three ways to do conditional assignment.
- Method1: `if/else if/else`

```
always @ (*)
begin
    if (S==1'b0)
        Y = I0;
    else
        Y = I1;
end
```

 For combinational circuits,
never use incomplete
conditional assignments!



- Method2: `case/endcase`

```
always @ (*)
begin
    case (S)
        1'b0: Y = I0;
        1'b1: Y = I1;
    endcase
end
```

- Method3:



```
always @ (*)
begin
    Y = (S) ? I1 : I0;
end
```

A Sample Design: Full Adder

- `module/endmodule` is used to define the design
- A unique name must be given to each design in a project

```
module Full_Adder
```

```
endmodule
```

 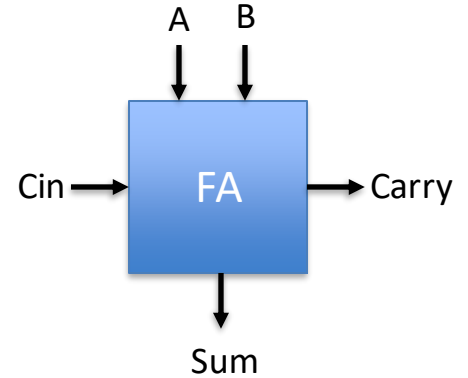

A Sample Design: Full Adder


- All I/Os must be defined in argument list. Order of the list is not important
- The polarity of the ports (`input` or `output`) must be defined at the beginning.

```
module Full_Adder (A, B, Cin, Sum, Carry);
```

```
    input A, B, Cin;
```

```
    output Sum, Carry;
```


```
endmodule
```

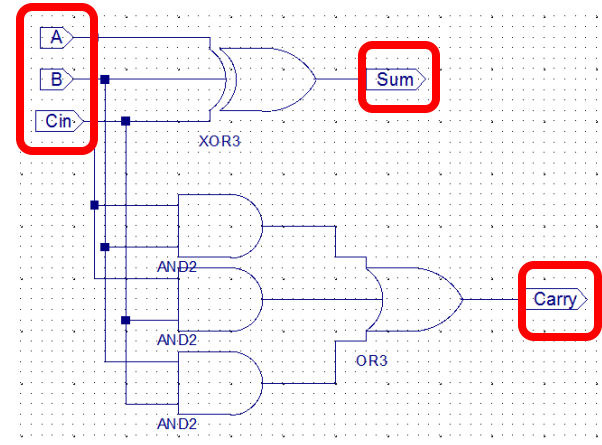

A Sample Design: Full Adder

- There may be some interconnections between gates
- Gates are connected with nets which are defined as `wire`

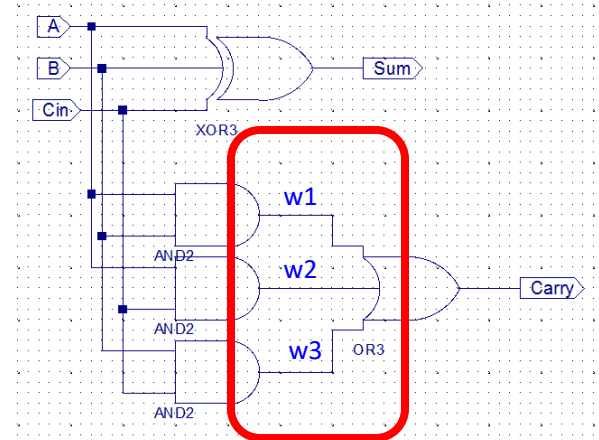
```
module Full_Adder (A, B, Cin, Sum, Carry);  
  
    input A, B, Cin;  
    output Sum, Carry;  
  
    wire w1, w2, w3;  
  
endmodule
```



A Sample Design: Full Adder

- After the module is created and all I/Os and nets are defined, the interconnections may be defined.

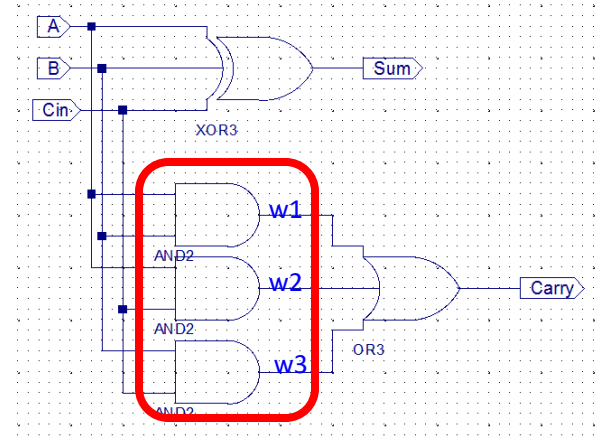
```
module Full_Adder (A, B, Cin, Sum, Carry);  
  
    input A, B, Cin;  
    output Sum, Carry;  
  
    wire w1, w2, w3;  
  
    assign w1 = A & B;  
    assign w2 = A & Cin;  
    assign w3 = B & Cin;  
  
endmodule
```



A Sample Design: Full Adder

- After the module is created and all I/Os and nets are defined, the interconnections may be defined.


```
module Full_Adder (A, B, Cin, Sum, Carry);  
  
    input A, B, Cin;  
    output Sum, Carry;  
  
    wire w1, w2, w3;  
  
    assign w1 = A & B;  
    assign w2 = A & Cin;  
    assign w3 = B & Cin;  
    assign Carry = w1 | w2 | w3;  
    assign Sum = A ^ B ^ Cin;  
  
endmodule
```

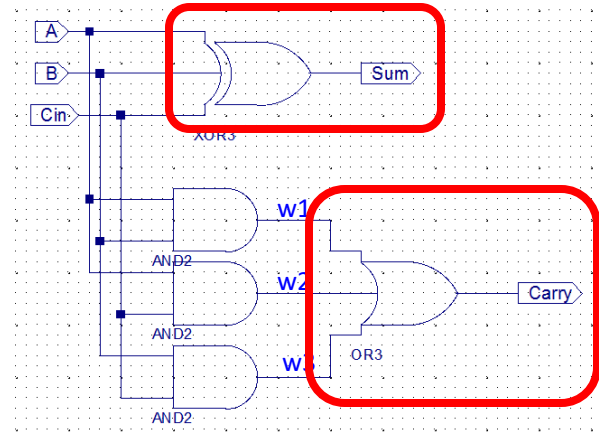

A Sample Design: Full Adder


- All interconnections do not have to be defined separately.
- `//` (line comment) or `/* */` (block comment) may be used to add comments.

```
module Full_Adder (A, B, Cin, Sum, Carry);  
  
    input A, B, Cin; //inputs  
    output Sum, Carry; /*outputs*/  
  
    assign Carry = (A & B) | (A & Cin) | (B & Cin);  
    assign Sum = A ^ B ^ Cin;  
  
endmodule
```

 


A Sample Design: 3-bit Ripple Carry Adder

 - Hierarchical Design
 - A module may be used as a sub-module of another module.



A Sample Design: 3-bit Ripple Carry Adder

 - Hierarchical Design
 - A module may be used as a sub-module of another module.



```
module RCA3 (A, B, Cin, S, Carry);
    input [2:0] A, B;
    input Cin;
    output [2:0] S;
    output Carry;
    wire C_0, C_1;

    Full_Adder FA0 (A[0], B[0], Cin, S[0], C_0);
    Full_Adder FA1 (.A(A[1]), .B(B[1]), .Cin(C_0), .S(S[1]), .Carry(C_1));
    Full_Adder FA2 (.S(S[2]), .B(B[2]), .Cin(C_1), .Carry(Carry), .A(A[2]));
endmodule
```

A Sample Design: 3-bit Ripple Carry Adder

- Module Instantiation
 - Firstly, **the name of module**, which is instantiated, is specified.
 - Then, **a unique name** is given to each module.

```
Full_Adder FA0 (<ports>);
```

A Sample Design: 3-bit Ripple Carry Adder

- Module Instantiation
 - Firstly, **the name of module**, which is instantiated, is specified.
 - Then, **a unique name** is given to each module.

```
Full_Adder FA0 (<ports>);
```

- Finally, I/O connections of the module are defined. There are two methods:

A Sample Design: 3-bit Ripple Carry Adder

- Module Instantiation
 - Firstly, **the name of module**, which is instantiated, is specified.
 - Then, **a unique name** is given to each module.

```
Full_Adder FA0 (<ports>);
```

- Finally, I/O connections of the module are defined. There are two methods:
 - Method1: Signal names are written inside the parenthesis. Signals have to be written in the same order of submodule argument list.

```
Full_Adder FA0 (A[0], B[0], Cin, S[0], C_0);
```

A Sample Design: 3-bit Ripple Carry Adder

- Module Instantiation

- Firstly, **the name of module**, which is instantiated, is specified.
- Then, **a unique name** is given to each module.

```
Full_Adder FA0 (<ports>);
```

- Finally, I/O connections of the module are defined. There are two methods:

- Method1: Signal names are written inside the parenthesis. Signals have to be written in the same order of submodule port list.

```
Full_Adder FA0 (A[0], B[0], Cin, S[0], C_0);
```

- Method2: Signals and ports are connected explicitly. Order of the signals is not important in this method.

```
Full_Adder FA0 (.A(A[0]), .B(B[0]), .Cin(Cin), .S(S[0]),  
.Carry(C_0));
```

Language Element – Generate Block

- A generate block is used to instantiate a module multiple times
 - It must be coded in a module

```
genvar i;  
  
generate  
    for (i=0; i<N; i=i+1)  
    begin  
        <module instantiation>  
    end  
endgenerate
```

Language Element – Generate Block

- C



```
for(int i=0; i<4; i++) {  
    s = Full_Addder(...);  
}
```

- Verilog

```
genvar i;  
generate  
    for(i=0; i<4; i=i+1) begin  
        Full_Addder fa(...);  
    end  
endgenerate
```


Language Element – Generate Block



- Example: 4-bit Carry Save Adder

  

Language Element – Generate Block

  - Example: 4-bit Carry Save Adder

```
module CSA4 (X, Y, Z, P);  
    input [3:0] X, Y, Z;  
    output [5:0] P;  
    wire [3:0] C, S;  
  
    genvar i;  
    generate  
        for (i=0; i<4; i=i+1) begin  
            Full_Adder fa(X[i], Y[i], Z[i], S[i], C[i]);  
        end  
    endgenerate  
  
    assign P = S + (C << 1);  
endmodule
```



Language Element – Parameter

- Parameters are constants that allow a module to be re-used with different specifications

```
parameter PARAMETER_NAME = <value>;
```

Language Element – Parameter

- Parameters are constants that allow a module to be re-used with different specifications

```
parameter PARAMETER_NAME = <value>;
```

- Example:

```
parameter N = 8;  
  
wire [N-1:0] a,b;  
wire [N:0] c;  
  
assign c = a+b;
```

Language Element – Parameter

- Example: Parameterized module

```
module CSA #(parameter N=4) (X, Y, Z, P);
    input  [N-1:0] X, Y, Z;
    output [N+1:0] P;
    wire  [N-1:0] C, S;

    genvar i;
    generate
        for(i=0; i<N; i=i+1) begin
            Full_Adder fa(X[i], Y[i], Z[i], S[i], C[i]);
        end
    endgenerate

    assign P = S + (C << 1);
endmodule
```

Language Element – Parameter

- Example: Parameterized module

```
module CSA #(parameter N=4) (X, Y, Z, P);
    input  [N-1:0] X, Y, Z;
    output [N+1:0] P;
    wire  [N-1:0] C, S;

    genvar i;
    generate
        for(i=0; i<N; i=i+1) begin
            Full_Adder fa(X[i], Y[i], Z[i], S[i], C[i]);
        end
    endgenerate

    assign P = S + (C << 1);
endmodule
```

- How to instantiate a parameterized module?

```
CSA #(.N(8)) unit(X,Y,Z,P);
```

Combinational Design vs Sequential Design

- Combinational design
 - Logic computation
- Sequential design
 - Logic computation + Memory element

Combinatorial

Example1:

```
wire a,b,c;  
assign a = b+c;
```

Example2:

```
wire b,c;  
reg a;  
always @(*)  
    a <= b+c;
```

Sequential


```
wire b,c;  
reg a;  
always @(posedge clk)  
    a <= b+c;
```

Flip flop

Not a flip
flop!


Sequential Design

 - Sequential circuits have memory elements and logic computation
 - Flip-flops + Combinatorial part




Sequential Design

 - Sequential circuits have memory elements and logic computation
 - Flip-flops + Combinatorial part




 - Flip-flop outputs change (updated) at only edge of trigger signal
 - Clock
 - Positive clock edge (posedge)
 - Negative clock edge (negedge)




Sequential Design

 - Sequential circuits have memory elements and logic computation
 - Flip-flops + Combinatorial part



 
- Flip-flop outputs change (updated) at only edge of trigger signal
 - Clock
 - Positive clock edge (posedge)
 - Negative clock edge (negedge)
 - Reset (optional)
 - Dependent to clock (**synchronous**)
 - Independent from clock (**asynchronous**)



Sequential Design – Flip-Flops

- Result is only available after clock's posedge/negedge transition

 
```
always @ (posedge CLK)
begin
    r <= r_in;
end
```



Sequential Design – Flip-Flops

- Result is only available after clock's posedge/negedge transition
 
```
always @ (posedge CLK)
begin
    r <= r_in;
end
```



D flip-flop with synchronous reset


```
always @ (posedge CLK)
begin
    if (RST)
        r <= 0;
    else
        r <= r_in;
end
```

D flip-flop with asynchronous reset

```
always @ (posedge CLK or posedge RST)
begin
    if (RST)
        r <= 0;
    else
        r <= r_in;
end
```

Sequential Design – Reset

 - Some sequential elements require a reset signal to initialize the circuit with a known state/value




Sequential Design – Reset

- Some sequential elements require a reset signal to initialize the circuit with a known state/value

```
module mymod(clk, rst, in, out);  
    input clk, rst;  
    input [7:0] in;  
    output [7:0] out;  
    reg[7:0] v;
```


```
endmodule
```

 

Sequential Design – Reset


- Some sequential elements require a reset signal to initialize the circuit with a known state/value
 
```
module mymod(clk, rst, in, out);  
    input clk, rst;  
    input [7:0] in;  
    output [7:0] out;  
    reg[7:0] v;  
  
    always @(posedge clk)  
    begin  
        if (rst)  
            v <= in;  
        else  
            v <= (v<<1) + 1;  
        end  
  
        assign out = v;  
  
endmodule
```




Control Unit (FSM) with Datapath

 - **Basic idea:** Control Unit and datapath exist as separate circuits.
- **Control Unit:**
 - Controls the data flow
 - An easy way to make a control unit: Finite State Machine (FSM)
- **Datapath:**
 - Performs data processing operations



Design with FSM and Datapath Example – A pattern detection circuit

 - A pattern detection circuit
 - A circuit takes 1-bit input and outputs "1" when the last 3-bits that it takes are "110". Otherwise, it outputs "0".



Design with FSM and Datapath Example – A pattern detection circuit

```
module PD(input  clk, reset, bit_i,
          output bit_o);

    reg [1:0] next_state;
    reg [1:0] curr_state;
    reg bit_o;

    parameter ST_0  = 2'd0,
    parameter ST_1  = 2'd1;
    parameter ST_11 = 2'd2;

    //State register
    always@(posedge clk)
    begin
        if(reset)
            curr_state <= ST_0;
        else
            curr_state <= next_state;
    end
end
```

Design with FSM and Datapath Example – A pattern detection circuit


```
//Next state logic
always@(*) begin
    case (curr_state)
        ST_0 : next_state = (bit_i == 1) ? ST_1 : ST_0;
        ST_1 : next_state = (bit_i == 1) ? ST_11 : ST_0;
        ST_11: next_state = (bit_i == 1) ? ST_11 : ST_0;
        default: next_state = ST_0;
    endcase
end

// output logic
always@(posedge clk) begin
    if(reset)
        bit_o <= 0;
    else
        bit_o <= (curr_state == ST_11 && bit_i == 0) ? 1 : 0;
    end
end

endmodule
```

Verilog Testbench

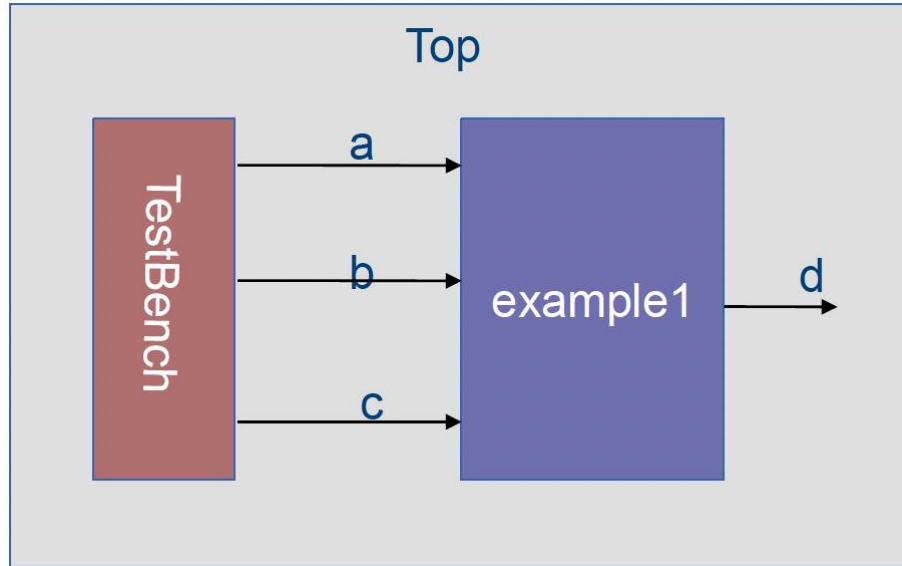- Used to simulate design and test its functional correctness.
- Simulation is much faster than testing/debugging on actual hardware.



Verilog Testbench

- How to generate a testbench for your combinatorial design module?
 1. Create a new module for testbench (tb)
 2. Create a `reg` for each input of your design in tb
 3. Create a `wire` for each output of your design in tb
 4. Create clock (if your design has a clock)
 5. Instantiate your design in tb
 6. Connect `regs` and `wires` to your design in tb
 7. Give inputs to your input
 8. Observe/verify outputs
- Let's look at the pattern detector example.

```
module PD(input  clk, reset, bit_i,  
          output bit_o);
```

Verilog Testbench – Steps for writing testbench

1. Create a new module for testbench (tb)

```
`timescale 1ns/1ps  
  
module PD_tb();
```

```
...
```

```
...
```

```
endmodule
```

Verilog Testbench – Steps for writing testbench

2. Create a `reg` for each input of your design in tb

```
`timescale 1ns/1ps  
  
module PD_tb();  
  
reg clk, reset, bit_i;
```

...

...

```
endmodule
```

Verilog Testbench – Steps for writing testbench

3. Create a `wire` for each output of your design in tb

```
`timescale 1ns/1ps  
  
module PD_tb();  
  
reg clk, reset, bit_i;  
wire bit_o;  
  
...
```

```
...
```

```
endmodule
```


Verilog Testbench – Steps for writing testbench

4. Create a clock

```
`timescale 1ns/1ps

module PD_tb();

reg clk, reset, bit_i;
wire bit_o;

always #5 clk = ~clk;

...
```

...

```
endmodule
```

Verilog Testbench – Steps for writing testbench

5+6. Instantiate your design in tb + Connect `regs` and `wires` to your design in tb

```
`timescale 1ns/1ps

module PD_tb();

reg clk, reset, bit_i;
wire bit_o;

always #5 clk = ~clk;

PD dut(clk,reset,bit_i,bit_o);

...
```

```
...
```

```
endmodule
```

Verilog Testbench – Steps for writing testbench

7+8. Give inputs to your design and observe outputs

```
`timescale 1ns/1ps

module PD_tb();

reg clk, reset, bit_i;
wire bit_o;

always #5 clk = ~clk;

PD dut(clk,reset,bit_i,bit_o);

...
```

```
...
initial begin
    // initialize all to 0
    clk=0; reset=1; bit_i=0;
    #20; // wait for 20 ns
    reset=0;
    #10; // wait for 10 ns
    bit_i=1; #20;
    bit_i=0; #20;
end


endmodule
```

Verilog Testbench – Steps for writing testbench

7+8. Give inputs to your design and observe outputs

```
`timescale 1ns/1ps
```

```
module PD_tb();
```

 

```
PD dut(clk,reset,bit_i,bit_o);
```

```
...
```

```
...
```

```
initial begin
```

```
    // initialize all to 0
```

```
    clk=0; reset=1; bit_i=0;
```

```
    #20; // wait for 20 ns
```

```
    reset=0;
```

```
    #10; // wait for 10 ns
```

```
    bit_i=1; #20;
```

```
    bit_i=0; #20;
```

```
end
```

```
endmodule
```

Common Mistakes/Bad Practices – Latches

- Latches easily cause timing problems:
 - In simulation: latches give correct results.,
 - On hardware: they almost always cause wrong results.
 - The tool throws warning when detecting latches in your design.

Example 1:

Latches

```
reg b;  
always @(*)  
begin  
    if (condition)  
        b <= b_in1;  
end;
```

Not Solved!

```
reg b;  
always @(*)  
begin  
    if (condition)  
        b <= b_in1;  
    else  
        b <= b;  
end;
```

Common Mistakes/Bad Practices – Latches

- Latches easily cause timing problems:
 - In simulation: latches give correct results.,
 - On hardware: they almost always cause wrong results.
 - The tool throws warning when detecting latches in your design.

Example 1:

Latches

```
reg b;  
always @(*)  
begin  
    if (condition)  
        b <= b_in1;  
end;
```

Solved

```
reg b;  
always @(*)  
begin  
    if (condition)  
        b <= b_in1;  
    else  
        b <= 0;  
end;
```

Common Mistakes/Bad Practices – Latches

- Latches easily cause timing problems:
 - In simulation: latches give correct results.,
 - On hardware: they almost always cause wrong results.
 - The tool throws warning when detecting latches in your design.

Example 2:

Latches

```
reg a;
always @(*)
begin
    case (condition)
        0: a <= a_in;
    endcase;
end;
```

Fixed

```
reg a;
always @(*)
begin
    case (condition)
        0: a <= a_in;
        default: a <= 0;
    endcase;
end;
```

Common Mistakes/Bad Practices – Multi-driven Nets

- Multi-driven nets

```
reg state;
reg [7:0] a,b;

always @(posedge clk)
begin
  if (state==0)
    a <= 1;
  else
    a <= 2; ←
  end;
end

always @(posedge clk)
begin
  if (state==0)
    b <= 1;
  else
    b <= 2;
    a <= 1; ←
  end;
end;
```

Tip: Multiple always blocks simplifies your design.

Be careful!


Never assign the same “reg” in two different always blocks.

Why? Always blocks run in parallel.

Common Mistakes/Bad Practices – Combinatorial Loops

- Combinatorial loops
 
```
wire [7:0] b;  
assign b = b + 1;
```



- No combinatorial loops between signals in a clock cycle

Common Mistakes/Bad Practices – Mixed Control Unit and Datapath

- Never use the same always block for control unit and datapath

BAD

```
reg state;
reg [7:0] R1, R2;

always @(posedge clk) begin
    state <= state ^ 1;
    if (state==0)
        R1 <= R2 + 1;
    else
        R1 <= R2 << 2;
end
```

- Advantages:
 - Easier to maintain and read code
 - Likely to lead to better critical path
 - Easier for tool to synthesize

GOOD

```
reg state;
reg[7:0] r;

always @(*) begin
    if (state==0)
        R1 <= R2 + 1;
    else
        R1 <= R2 << 2;
end

always @(posedge clk)
begin
    state <= state ^ 1;
end;
```